



حقيبة تعليمية

بغنوان: Electrical Engineering Fundamentals

إعداد

أ.م.د محمود حمزة محمد

2023 - 2022



Introduction:

Electrical engineering is an engineering discipline concerned with the study, design, and application of equipment, devices, and systems which use electricity, electronics, and electromagnetism. It emerged as an identifiable occupation in the latter half of the 19th century after commercialization of the electric telegraph, the telephone, and electrical power generation.



الصفحة	الموضوع	م
26	POWERS OF TEN	1
32	Current and Voltage	2
38	Series Circuits:	3
43	VOLTAGE DIVIDER RULE:	4
49	Parallel Circuits:	5
56	CURRENT DIVIDER RULE:	6
60	Open and Short Circuits:	7
63	Series-Parallel Networks:	8
71	Kirchoff's Laws	9
76	Current Sources in Parallel	10
83	Source Conversions	11
91	Nodal Analysis	12
96	Superposition Theorem	13
103	Thevenin's Theorem	14
112	Norton's Theorem	15
120	Maximum Power Transfer Theorem	16
125	Magnetic Circuits	17
131	Sinusoidal Alternating Waveforms	18
138	GENERAL FORMAT FOR THE SINUSOIDAL VOLTAGE OR CURRENT	19
142	PHASE RELATIONS	20
146	AVERAGE VALUE (mean)	21
152	EFFECTIVE (rms) VALUES	22
156	RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURREN	23
164	COMPLEX NUMBERS	24
171	MATHEMATICAL OPERATIONS WITH COMPLEX NUMBERS	25



الصفحة	الموضوع	م
178	IMPEDANCE AND THE PHASOR DIAGRAM	26
185	SERIES CONFIGURATION	27
195	PARALLEL ac NETWORKS	28
204	Series-Parallel ac Networks	29
208	Methods of Analysis (ac)	30
211	Power (ac)	31
212	APPARENT POWER	32



وصف المقرر الدراسي

يوفر وصف المقرر هذا إيجازاً مقتضياً لأهم خصائص المقرر ومخرجات التعلم المتوقعة من الطالب تحقيقها ميرهنأ عما إذا كان قد حقق الاستفادة القصوى من فرص التعلم المتاحة. ولا بد من الربط بينها وبين وصف البرنامج؛

1. المؤسسة التعليمية	كلية الرشيد الجامعة
2. القسم العلمي / المركز	هندسة تقنيات الحاسوب
3. اسم / رمز المقرر	أسس الهندسة الكهربائية
4. أشكال الحضور المتاحة	اسبوعي
5. الفصل / السنة	فصلين دراسيين / السنة الدراسية الاولى
6. عدد الساعات الدراسية (الكلي)	90 ساعة
7. تاريخ إعداد هذا الوصف	2022-8-14
8. أهداف المقرر	
الهدف من هذه المقرر إعطاء الطالب معلومات اساسية عن عناصر الدوائر الكهربائية و النظريات التي تستخدم في تحليل الدوائر الكهربائية وتطبيقها عمليا.	

10. مخرجات المقرر وطرائق التعليم والتعلم والتقييم

أ- الأهداف المعرفية : اذا اتم الطالب هذا المقرر بنجاح فإنه يكون قادرا على ان:

- 1- يتعرف على الرموز والمختصرات والوحدات والعناصر التي تستخدم في الدوائر الكهربائية.
- 2- يميز بين دوائر التوالي والتوازي وطريقة نقل مصادر الطاقة بينهما.
- 3- يحسب الجهد والتيار والطاقة في دوائر التيار المستمر التي تحتوي على مقاومات, مصادر تيار , مصادر جهد و مصادر جهد و تيار غير مستقلة ودوائر التيار المتناوب التي تحتوي على المحاثّة والمتسعة .
- 4- يستخدم الطرق والنظريات لتحليل الدوائر الكهربائية .
- 5- يحسب القدرة المستهلكة بالدائرة و القدرة المستمدة من المصدر و اقصى قدرة منقولة الى الحمولة.
- 6- يتعرف على انواع موجات دوائر التيار المتناوب وطريقة توليدها والعناصر التي تستخدم في هذه الدوائر.
- 7- يطبق النظريات التي تستخدم في تحليل دوائر التيار المستمر على دوائر التيار المتناوب.
- 8- يتعرف على اجهزة القياس.
- 9- يتدرب على استخدام الاجهزة الكهربائية المختبرية للقياسات المختلفة.

: اذا اتم الطالب هذا المقرر بنجاح فإنه يكون قادرا على ان:

- 1ب – يصمم التجارب العملية وإجراءها وتحليل البيانات وتفسيرها التي تحقق الجانب النظري.
- 2ب – يكتسب مهارة استخدام اجهزة القياس الكهربائي المختلفة.
- 3ب – يحدد مشاكل الدوائر الكهربائية.
- 4ب- يتمكن من العلوم الرياضية والأساسية والهندسية الضرورية لإجراء تحليل وتصميم نظم الهندسة الكهربائية والالكترونية.

طرائق التعليم والتعلم

- المحاضرات النظرية (الحصول على أ 1- أ 9 من الفقرة 9) .
- التطبيق العملي في المختبر لمفردات المنهاج (الحصول على ب 1 - ب 4 من الفقرة 9) .
- أستخدام اجهزة القياس المختبرية.
- الحوارات والمناقشات خلال المحاضرات النظرية والعملية (الحصول على أ 1- أ 2 من الفقرة 9).
- الاستعانة ببعض المباديء الهندسية العامة والتي تصب بتحليل وتصميم المشكلة الهندسية بالاضافة الى الاستعانة بالقوانين والقواعد الخاصة بالهندسة الكهربائية وذلك لتعيين مكن المشكلة وحلها.

طرائق التقييم

- الامتحانات النظرية الدورية والفصلية للتحقق من أ 1 - أ 9 من الفقرة 9.
- الامتحانات العملية الدورية والفصلية للتحقق من ب 1 - ب 4 من الفقرة 9.
- الاختبارات القصيرة (Quizzes).
- الحوارات والنقاشات الصفية للتحقق من أ 1- أ 2 من الفقرة 9 .

ج- الأهداف الوجدانية والقيمية : اذا اتم الطالب هذا المقرر بنجاح فإنه يكون قادرا على ان:

- ج1- يدرك مطلوبات مهنة الهندسة والمسؤولية الأخلاقية.
- ج2- يستوعب تأثير الحلول الهندسية على الأنشطة الاقتصادية والبيئية والسياق المجتمعي.
- ج3- يدرك الحاجة إلى التعلم مدى الحياة والقدرة على الانخراط فيه.

طرائق التعليم والتعلم

للوصول الى ج1-ج3 يتم عن طريق :

- المحاضرات النظرية.
- المحاضرات العملية والتطبيق العملي في المختبر.
- المناقشات الجماعية.

طرائق التقييم

للتحقق من ج 1 - ج3 من الفقرة 9 يتم عن طريق :

- الامتحانات النظرية الدورية والفصلية
- الامتحانات العملية الدورية والفصلية
- التقارير

د - المهارات العامة والتأهيلية المنقولة (المهارات الأخرى المتعلقة بقابلية التوظيف والتطور الشخصي).

د1- تحديد وصياغة وحل المشاكل الهندسية.

د2- تصميم التجارب واجراءها وتحليل البيانات وتفسيرها.

د3- استخدام التقنيات والمهارات الهندسية الحديثة والأدوات اللازمة لممارسة مهنة الهندسة.

طرائق التعليم والتعلم

للوصول الى د 1 - د 3 يتم الاستفادة من تناول مشكلة هندسية عملية تخص هندسة الدوائر الكهربائية ويطلب بكتابتها على شكل تقرير و عرض نتائجه ضمن فترة زمنية محددة.

طرائق التقييم

الاستفادة من طريقة تقييم الفقرة ج من الفقرة 9 .

10. بنية المقرر					
الأسبوع	الساعات	مخرجات التعلم المطلوبة	اسم الوحدة / أو الموضوع	طريقة التعليم	طريقة التقييم
1	T1+2	ان يكون الدارس قادرا على ان يفهم اساسيات الدوائر الكهربائية	Symbols And Abbreviations, Units, Electric Circuit & It's Element.	عرض نظري بالاستعانة ببعض المبادئ الهندسية العامة	اختبار تحصيلي +واجب صفي
2	T1+2	ان يفهم اساسيات الدوائر الكهربائية	The Direct Current Network. Kirchoff's Laws & Their Use In Network Analysis.		
3	T1+2	ان يكون الدارس قادرا على ان يميز بين دوائر التوالي والتوازي	Series Circuits, Parallel Circuits, Series-Parallel Circuits , Open and Short Circuits, Source Transformation	عرض نظري بالاستعانة بالمخططات التوضيحية	اختبار تحصيلي +واجب صفي
4	T 1+2	ان يميز بين دوائر التوالي والتوازي	Conversion Of Delta To Star Connection And Vice Versa.		اختبار تحصيلي +واجب صفي
5	T 1+2	ان يكون الدارس قادرا على ان يستخدم نظريات تحليل الدوائر الكهربائية	Nodal Voltage Method	عرض نظري بالاستعانة بالمعادلات والقواعد الخاصة بالدوائر الكهربائية	اختبار تحصيلي +واجب صفي
6	T1+2	ان يستخدم نظريات تحليل الدوائر الكهربائية	Loop (mesh)Current Method.		
7	T1+2	ان يستخدم نظريات تحليل الدوائر الكهربائية	Superposition Method.		



اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمعادلات والقواعد الخاصة بالدوائر الكهربائية	Thevenin's Theorem	ان يكون الدارس قادرا على	T1+2	8
اختبار تحصيلي +واجب صفي		Norton's Theorem	ان يستخدم نظريات تحليل الدوائر الكهربائية للتيار المستمر	T1+2	9
اختبار تحصيلي +واجب صفي		Maximum Power Transfer Theorem		T1+2	10
اختبار تحصيلي +واجب صفي		Reciprocity Theorem		T1+2	11
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمخططات التوضيحية	The Alternating Current Network Types of Alternating Waveforms, Generation of Alternating Current, and Definitions related to Alternating Waveforms.		T1+2	12
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالقوانين والمخططات التوضيحية	The Mean Values of Current and Voltage	ان يكون الدارس قادرا على ان يفهم اساسيات دوائر التيار المتناوب	T1+2	13
اختبار تحصيلي +واجب صفي		The Effective Vales of Current and Voltage		T1+2	14
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالقوانين والمخططات التوضيحية	Circuit Elements in the Phasor Domain		T1+2	15
اختبار تحصيلي +واجب صفي		The Vector Diagram		T1+2	16
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالقوانين والمخططات التوضيحية	Reviews for Complex Numbers and there mathematical operations th		T1+2	17
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمعادلات والقواعد الخاصة بالدوائر الكهربائية	Series and Parallel Ac Circuits	ان يكون الدارس قادرا على ان يتعرف على دوائر التوالي والتوازي للتيار المتناوب وتطبيق القوانين الحسابية	T1+2	18
اختبار تحصيلي +واجب صفي		The Instantaneous Power and Mean Power of AC, Reactive and Apparent Power		T1+2	19
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمعادلات والقواعد الخاصة بالدوائر الكهربائية	Using Kirchhoff's law's to solve AC circuits	ان يكون الدارس قادرا على ان يستخدم نظريات تحليل الدوائر الكهربائية للتيار المتناوب	T1+2	20
اختبار تحصيلي +واجب صفي		Using Loop's method to solve AC circuits		T1+2	21
اختبار تحصيلي +واجب صفي		Using Superposition's method to solve AC circuits		T1+2	22
اختبار تحصيلي +واجب صفي		Using Thevenin's theorem to solve AC circuits		T1+2	23



اختبار تحصيلي +واجب صفي		Using Norton's theorem to solve AC circuits		T1+2	24
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمخططات التوضيحية	3- Phase Current, 3- Phase System, Y- Connection Delta Connection.	ان يكون الدارس قادرا على فهم	T1+2	25
اختبار تحصيلي +واجب صفي		Solving 3-phase networks with balanced loads, Solving 3-phase networks with unbalanced loads	اساسيات الدوائر ذات ثلاثية الطور	T1+2	26
اختبار تحصيلي +واجب صفي	عرض نظري بالاستعانة بالمعادلات والقواعد الخاصة بالدوائر الكهرومغناطيسية	Electromagnetism, Permanent and artificial Magnets, The Magnetic Field, The flux density , The magnetic reluctance , The permeability , The mmf , The magnetic force , The electromagnetic circuits.	ان يكون الدارس قادرا على فهم	T1+2	27
اختبار تحصيلي +واجب صفي		The implementation of B-H curves for solving electromagnetic circuits	اساسيات الدوائر الكهرومغنا طيسية	T1+2	28
اختبار تحصيلي +واجب صفي		Transformers , The hysteresis losses , The eddy current losses		T1+2	29
اختبار تحصيلي +واجب صفي		Direct Current Machines, Direct Current Generators, Asynchronous And Synchronous Machines.		T1+2	30



10. البنية التحتية	
*Boylestad, R. L. " Introductory Circuit Analysis", 4th Edition, Charles E. Merill Publishers.	1- الكتب المقررة المطلوبة
*Alexander C. K. and Sadiku M. N. "Fundamentals of Electric Circuits", McGraw- Hill Companies. *Alexander C. K. and Sadiku M. N. " Circuit Analysis, Theory and Practice", 2nd Edition, Robbins & Miller. *B.L Theraja, " A Text Book of Electrical Technology" ,4th Edition.	2- المراجع الرئيسية (المصادر)
	ا- الكتب والمراجع التي يوصى بها (المجلات العلمية , التقارير ,) (
"Electrical Circuit Fundamental", http://www.electronics-tutorials.ws	ب - المراجع الالكترونية, مواقع الانترنت



HIGHER EDUCATION PERFORMANCE REVIEW: PROGRAMME REVIEW

COURSE SPECIFICATION

This Course Specification provides a concise summary of the main features of the course and the learning outcomes that a typical student might reasonably be expected to achieve and demonstrate if he/she takes full advantage of the learning opportunities that are provided. It should be cross-referenced with the programme specification.

1. Teaching Institution	Al-Rasheed University College
2. University Department/Centre	computer technology engineering
3. Course title/code	basics of electrical engineering
4. Programme(s) to which it contributes	Use of different electrical measuring devices
5. Modes of Attendance offered	weekly
6. Semester/Year	Two semesters / first academic year
7. Number of hours tuition (total)	hours 90
8. Date of production/revision of this specification	14/4/2022
9. Aims of the Course instructions is to give the student information about electrical .circuits, electrical circuits, and theories that are used in electrical circuits and	



10. Learning Outcomes, Teaching ,Learning and Assessment Methode

A- Knowledge and Understanding: If the student successfully completes this course, he will be able to:

A1- Recognize the symbols, abbreviations, units and elements that are used in electrical circuits.

A2- Distinguish between series and parallel circuits and the way energy sources are transferred between them.

A3- Calculates voltage, current and power in DC circuits that contain resistors, current sources, voltage sources, non-independent voltage and current sources, and alternating current circuits containing inductance and capacitance

A4- Uses methods and theories to analyze electrical circuits

A5- Calculates the power consumed in the circuit, the power derived from the source, and the maximum power transferred to the load

A6- Recognize the types of waves in alternating current circuits, the method of generating them, and the elements that are used in these circuits

A7- Apply the theories that are used in the analysis of DC circuits to AC circuits

A8- Familiarize yourself with measuring devices

A 9- He is trained in the use of electrical laboratory equipment for different measurements.

B. Course specific objectives. If the student successfully completes this course, he will be able to:

B1 - designs and conducts practical experiments, and analyzes and interprets data .that achieve the theoretical aspect

.B2 - Acquire the skill of using different electrical measuring devices

.B3 - Identifies electrical circuit problems

.B4- Be able to master the mathematical, basic and engineering sciences necessary to analyze and design electrical and electronic engineering systems.



Teaching and Learning Methods

- Theoretical lectures (getting A-1 A9 from paragraph 9).
- Practical application in the lab of the curriculum vocabulary (obtaining B1 - B4 from paragraph (9)).
- Use of laboratory equipment.
- Dialogues and discussions during theoretical and practical lectures (get A-1a2 from paragraph 9).
- Using some general engineering principles, which are intended to analyze and design the engineering problem, in addition to using the laws and rules of electrical engineering in order to identify the location of the problem and its solution .

Assessment methods

- Periodic and quarterly theoretical exams to verify A-1 A9 of Paragraph 9.
- Periodic and quarterly practical exams to verify B1 - B4 of Paragraph 9.
- Quizzes.
- Classroom discussions and discussions to verify A-1a2 of Paragraph 9.



C. Thinking Skills : If the student successfully completes this course, he will be able to:

C1- He understands the requirements of the engineering profession and ethical responsibility.

C2- Understand the impact of engineering solutions on economic and environmental activities and the societal context.

C3- Recognize the need for lifelong learning and the ability to engage in it.

Teaching and Learning Methods

To reach C1-C3 is through

- Theoretical lectures.
- Practical lectures and practical application in the laboratory.
- Group discussions

Assessment methods

Verification of C 1 - C 3 of Paragraph 9 is done by:

- Regular and quarterly theory exams
- Regular and quarterly practical exams
- Reports



D. General and Transferable Skills (other skills relevant to employability and personal development)

D1- Defining, formulating and solving engineering problems.

D2- Design and conduct experiments, and analyze and interpret data.

D3 - Using modern engineering techniques and skills and tools necessary to practice the engineering profession.

Teaching and learning methods

To get to D1 - D3, it is benefited from addressing a practical engineering problem related to electrical circuit engineering, and it is required to write it in the form of a report and present its results within a specified period of time.

Evaluation methods

Take advantage of the method of evaluation of paragraph C of paragraph 9.

11. Course Structure					
Week	Hours	ILOs	Unit/Module or Topic Title	Teaching Method	Assessment Method
1	T1+2	To be able to understand the basics of electrical circuits	Symbols And Abbreviations, Units, Electric Circuit & It's Element.	theoretical presentation Using some general engineering principles	Achievement test class homework +
2	T1+2		The Direct Current Network. Kirchoff's Laws & Their Use In Network Analysis.		Achievement test class homework +
3	T1+2	The student should be able to distinguish between series and parallel circuits	Series Circuits, Parallel Circuits, Series-Parallel Circuits , Open and Short Circuits, Source Transformation	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
4	T1+2		Conversion Of Delta To Star Connection And Vice Versa.		Achievement test class homework +
5	T1+2	The student should be able to use the theories of electrical circuit analysis	Nodal Voltage Method	theoretical presentation with the help of With equations and rules for electrical circuits	Achievement test class homework +
6	T1+2		Loop (mesh)Current Method.		Achievement test class homework +
7	T1+2		Superposition Method.		Achievement test class homework +
8	T1+2	The student should be able to use the theories of DC circuit analysis	Thevenin's Theorem	theoretical presentation with the help of With equations and rules for electrical circuits	Achievement test class homework +
9	T1+2		Norton's Theorem		Achievement test class homework +
10	T1+2		Maximum Power Transfer Theorem		Achievement test class homework +
11	T1+2		Reciprocity Theorem		Achievement test class homework +



12	T1+2	To be able to understand the basics of alternating current circuits	The Alternating Current Network Types of Alternating Waveforms, Generation of Alternating Current, and Definitions related to Alternating Waveforms.	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
13	T1+2		The Mean Values of Current and Voltage	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
14	T1+2		The Effective Vales of Current and Voltage	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
15	T1+2		Circuit Elements in the Phasor Domain	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
16	T1+2		The Vector Diagram	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
17	T1+2		Reviews for Complex Numbers and there mathematical operations th	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
18	T1+2		The student should be able to identify the series and parallel circuits of alternating current and apply arithmetic laws	Series and Parallel Ac Circuits	theoretical presentation with the help of With equations and rules for electrical circuits
19	T1+2	The Instantaneous Power and Mean Power of AC, Reactive and Apparent Power		Achievement test class homework +	



20	T1+2	The student should be able to use theories electrical circuit analysis	Using Kirchoff's law's to solve AC circuits	theoretical presentation with the help of With equations and rules for electrical circuits	Achievement test class homework +
21	T1+2		Using Loop's method to solve AC circuits		Achievement test class homework +
22	T1+2		Using Superposition's method to solve AC circuits		Achievement test class homework +
23	T1+2		Using Thevenin's theorem to solve AC circuits		Achievement test class homework +
24	T1+2	The student should be able to use theories AC circuit analysis	Using Norton's theorem to solve AC circuits	theoretical presentation with the help of With equations and rules for electrical circuits	Achievement test class homework +
25	T1+2	The student should be able to understand the basics of three-phase circuits	3- Phase Current, 3-Phase System, Y-Connection Delta Connection.	theoretical presentation with the help of by schematics illustration	Achievement test class homework +
26	T1+2	The student should be able to understand the basics of three-phase circuits	Solving 3-phase networks with balanced loads, Solving 3-phase networks with unbalanced loads	theoretical presentation with the help of With equations and rules for electromagnetic circuits	Achievement test class homework +
27	T1+2	To be able to understand the basics of electromagnetic circuits	Electromagnetism, Permanent and artificial Magnets, The Magnetic Field, The flux density , The magnetic reluctance , The permeability , The mmf , The magnetic force , The electromagnetic circuits.		Achievement test class homework +



28	T1+2	To be able to understand the basics of electromagnetic circuits	The implementation of B-H curves for solving electromagnetic circuits	theoretical presentation with the help of With equations and rules for electromagnetic circuits	Achievement test class homework +
29	T1+2		Transformers , The hysteresis losses , The eddy current losses		Achievement test class homework +
30	T1+2		Direct Current Machines, Direct Current Generators, Asynchronous And Synchronous Machines.		Achievement test class homework +



12. Infrastructure	
Required reading: · CORE TEXTS · COURSE MATERIALS · OTHER	*Boylestad, R. L. " Introductory Circuit Analysis", 4th Edition, Charles E. Merill Publishers.
Special requirements (include for example workshops, periodicals, IT software, websites)	Alexander C. K. and Sadiku M. N. "Fundamentals of Electric Circuits McGraw- Hill Companies. *Alexander C. K. and Sadiku M. N. " Circuit Analysis, Theory and Practice", 2nd Edition, Robbins & Miller. B.L Theraja, " A Text Book of Electrical Technology" th Edition.
Community-based facilities (include for example, guest Lectures , internship , field studies)	

13. Admissions	
Pre-requisites	
Minimum number of students	
Maximum number of students	



إرشادات للطلبة

- الرغبة والحماس للتعليم
- كن مشاركاً في جميع الأنشطة
- احترم أفكار المدرس وزملاء
- أنقد أفكار المدرس وزملاء بأدب إن كانت هناك حاجة.
- احرص على استثمار الوقت
- تقبل الدور الذي يسند إليك في المجموعة
- حفز أفراد مجموعتك في المشاركة في النشاطات
- احرص على بناء علاقات طيبة مع المدرس وزملاء أثناء المحاضرة
- احرص على ما تعلمته في المحاضرة وطبقه في الميدان .
- ركز ذهنك بالتعليم و احرص على التطبيق المباشر
- تغلق الموبايل قبل الشروع بالمحاضرة



الوحدة الأولى - الزمن: 90 دقيقة

أهداف المحاضرة الأولى:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على القوانين المهمة التي يستفاد منها الطالب

موضوعات

الأساليب والأنشطة والوسائل التعليمية

م	الأساليب والأنشطة التدريسية	الوسائل التدريسية
1	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام

خطة إجراءات تنفيذ المحاضرة الأولى



الزمن بالدقيقة	الإجراءات	المحاضرة	الوحدة
90 دقيقة	الترحيب بالطلبة والتعارف معهم التعريف بالبرنامج وأهدافه وأهميته	الأولى	الأولى

Electrical Circuits



POWERS OF TEN

$$\begin{aligned} 1 &= 10^0 & 1/10 &= 0.1 = 10^{-1} \\ 10 &= 10^1 & 1/100 &= 0.01 = 10^{-2} \\ 100 &= 10^2 & 1/1000 &= 0.001 = 10^{-3} \\ 1000 &= 10^3 & 1/10,000 &= 0.0001 = 10^{-4} \end{aligned}$$

$$10,000.0 = 1 \underbrace{0,000}_{1\ 2\ 3\ 4} = 10^{+4}$$

$$0.00001 = 0 \underbrace{.00001}_{5\ 4\ 3\ 2\ 1} = 10^{-5}$$

$$\frac{1}{10^n} = 10^{-n} \quad \frac{1}{10^{-n}} = 10^n$$

EXAMPLE:

a. $\frac{1}{1000} = \frac{1}{10^{+3}} = 10^{-3}$

b. $\frac{1}{0.00001} = \frac{1}{10^{-5}} = 10^{+5}$

The product of powers of ten:

$$(10^n)(10^m) = 10^{(n+m)}$$

EXAMPLE

a. $(1000)(10,000) = (10^3)(10^4) = 10^{(3+4)} = 10^7$

b. $(0.00001)(100) = (10^{-5})(10^2) = 10^{(-5+2)} = 10^{-3}$

The division of powers of ten:

$$\frac{10^n}{10^m} = 10^{(n-m)}$$



EXAMPLE

a. $\frac{100,000}{100} = \frac{10^5}{10^2} = 10^{(5-2)} = 10^3$

b. $\frac{1000}{0.0001} = \frac{10^3}{10^{-4}} = 10^{(3-(-4))} = 10^{(3+4)} = 10^7$

The power of powers of ten:

$$(10^n)^m = 10^{(nm)}$$

EXAMPLE

a. $(100)^4 = (10^2)^4 = 10^{(2)(4)} = 10^8$

b. $(1000)^{-2} = (10^3)^{-2} = 10^{(3)(-2)} = 10^{-6}$

c. $(0.01)^{-3} = (10^{-2})^{-3} = 10^{(-2)(-3)} = 10^6$

Basic Arithmetic Operations

1- Addition and Subtraction

$$A \times 10^n \pm B \times 10^n = (A \pm B) \times 10^n$$

EXAMPLE

a. $6300 + 75,000 = (6.3)(1000) + (75)(1000)$
 $= 6.3 \times 10^3 + 75 \times 10^3$
 $= (6.3 + 75) \times 10^3$
 $= 81.3 \times 10^3$

b. $0.00096 - 0.000086 = (96)(0.00001) - (8.6)(0.00001)$
 $= 96 \times 10^{-5} - 8.6 \times 10^{-5}$
 $= (96 - 8.6) \times 10^{-5}$
 $= 87.4 \times 10^{-5}$

2- Multiplication



$$(A \times 10^n)(B \times 10^m) = (A)(B) \times 10^{n+m}$$

EXAMPLE

a. $(0.0002)(0.000007) = [(2)(0.0001)][(7)(0.000001)]$
 $= (2 \times 10^{-4})(7 \times 10^{-6})$
 $= (2)(7) \times (10^{-4})(10^{-6})$
 $= 14 \times 10^{-10}$

b. $(340,000)(0.00061) = (3.4 \times 10^5)(61 \times 10^{-5})$
 $= (3.4)(61) \times (10^5)(10^{-5})$
 $= 207.4 \times 10^0$
 $= 207.4$

3- Division

$$\frac{A \times 10^n}{B \times 10^m} = \frac{A}{B} \times 10^{n-m}$$

EXAMPLE

a. $\frac{0.00047}{0.002} = \frac{47 \times 10^{-5}}{2 \times 10^{-3}} = \left(\frac{47}{2}\right) \times \left(\frac{10^{-5}}{10^{-3}}\right)$
 $= 23.5 \times 10^{-2}$

b. $\frac{690,000}{0.00000013} = \frac{69 \times 10^4}{13 \times 10^{-8}} = \left(\frac{69}{13}\right) \times \left(\frac{10^4}{10^{-8}}\right)$
 $= 5.31 \times 10^{12}$

4- Powers

$$(A \times 10^n)^m = A^m \times 10^{nm}$$

EXAMPLE



a. $(0.00003)^3 = (3 \times 10^{-5})^3 = (3)^3 \times (10^{-5})^3$
 $= 27 \times 10^{-15}$

b. $(90,800,000)^2 = (9.08 \times 10^7)^2 = (9.08)^2 \times (10^7)^2$
 $= 82.4464 \times 10^{14}$

Prefixes

Multiplication Factors	SI Prefix	SI Symbol
1 000 000 000 000 = 10^{12}	tera	T
1 000 000 000 = 10^9	giga	G
1 000 000 = 10^6	mega	M
1 000 = 10^3	kilo	k
0.001 = 10^{-3}	milli	m
0.000 001 = 10^{-6}	micro	μ
0.000 000 001 = 10^{-9}	nano	n
0.000 000 000 001 = 10^{-12}	pico	p

EXAMPLE

a. 1,000,000 ohms = 1×10^6 ohms
= 1 megohm ($M\Omega$)

b. 100,000 meters = 100×10^3 meters
= 100 kilometers (km)

c. 0.0001 second = 0.1×10^{-3} second
= 0.1 millisecond (ms)

d. 0.000001 farad = 1×10^{-6} farad
= 1 microfarad (μF)



EXAMPLE

- a. 41,200 m is equivalent to 41.2×10^3 m = 41.2 kilometers = **41.2 km**.
- b. 0.00956 J is equivalent to 9.56×10^{-3} J = 9.56 millijoules = **9.56 mJ**.
- c. 0.000768 s is equivalent to 768×10^{-6} s = 768 microseconds = **768 μ s**.
- d. $\frac{8400 \text{ m}}{0.06} = \frac{8.4 \times 10^3 \text{ m}}{6 \times 10^{-2}} = \left(\frac{8.4}{6}\right) \times \left(\frac{10^3}{10^{-2}}\right) \text{ m}$
 $= 1.4 \times 10^5 \text{ m} = 140 \times 10^3 \text{ m} = 140 \text{ kilometers} = \mathbf{140 \text{ km}}$
- e. $(0.0003)^4 \text{ s} = (3 \times 10^{-4})^4 \text{ s} = 81 \times 10^{-16} \text{ s}$
 $= 0.0081 \times 10^{-12} \text{ s} = 0.008 \text{ picosecond} = \mathbf{0.0081 \text{ ps}}$

الوحدة الثانية - الزمن: 90 دقيقة

أهداف المحاضرة الاولى:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على التيار والفولتية

موضوعات



الأساليب والأنشطة والوسائل التعليمية

الوسائل التدريبية	الأساليب والأنشطة التدريبية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	1


Current and Voltage

Charge: the electrical charge is an electrical property of atomic particles of which matter consists, measured in coulombs (C). The charge of an electron is ($-1.602 \times 10^{-19} C$).

Electrical current: is the rate of change of charge, measured in amperes (A). The current (I) is defined mathematically as:

$$I = \frac{Q}{t}$$

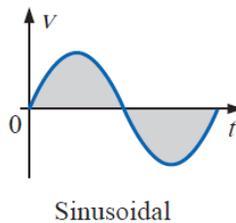- **Direct current (DC):** is the current that remains constant with time. The symbol (I) is usually used to represent such a constant current.
- **Alternating current (AC):** is a current that is varying sinusoidally with time. A time varying current is represented by the symbol (i).



Voltage: the voltage (or potential difference) is the energy required to move a unit of charge through an element, measured in volts (V).

* For the voltage **V_{ab}**, this mean that the potential of point **a** is higher than that of point **b**.

$$V_{ab} = V_a - V_b$$

Power: is the time rate of expending or absorbing energy, measured in watt (W).

$$P = \frac{w}{t}$$

Where P is the power in watt (W), w is the energy in joules (J), and t is the time in seconds (s).


The power (P) is defined mathematically as:

$$P = VI$$

$$P = \frac{V^2}{R}$$

$$P = I^2R$$

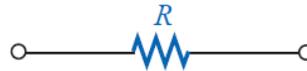Resistance: the resistance R denotes the ability of an element to resist the flow of electrical current, it is measured in Ohms (Ω).



For the material, the resistance R depends of the physical dimensions as follows:

$$R = \rho \frac{l}{A}$$

Where ρ is the receptivity of material.

Resistivity (ρ) of various materials in ohm-centimeters.

Silver	1.645×10^{-6}
Copper	1.723×10^{-6}
Gold	2.443×10^{-6}
Aluminum	2.825×10^{-6}
Tungsten	5.485×10^{-6}
Nickel	7.811×10^{-6}
Iron	12.299×10^{-6}
Tantalum	15.54×10^{-6}
Nichrome	99.72×10^{-6}
Tin oxide	250×10^{-6}
Carbon	3500×10^{-6}


EXAMPLE: Determine the resistance of 30.48 m of copper telephone wire if the diameter is 0.032 cm.

Solution:

$$A = \frac{\pi d^2}{4} = \frac{(3.1416)(0.032 \text{ cm})^2}{4} = 8.04 \times 10^{-4} \text{ cm}^2$$

$$R = \rho \frac{l}{A} = \frac{(1.723 \times 10^{-6} \Omega \cdot \text{cm})(3048 \text{ cm})}{8.04 \times 10^{-4} \text{ cm}^2} \cong 6.5 \Omega$$

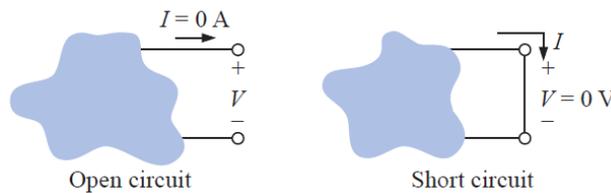- The resistance of a short circuit element is approaching **zero**.
- The resistance of an open circuit element is approaching **infinity**.



Conductance: the conductance can be explained as the ability of an element to conduct electrical current, it is measured in siemens (S).

$$G = \frac{1}{R}$$

$$G = \frac{A}{\rho l}$$

OHM'S LAW: Ohm's law states that the voltage V across a resistor is directly proportional to the current I flowing through the resistor.

$$V = IR \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

EXAMPLE: Determine the current resulting from the application of a 9-V battery across a network with a resistance of 2.2Ω .

Solution:


$$I = \frac{V}{R} = \frac{9V}{2.2\Omega} = 4.09 A$$

EXAMPLE: Calculate the resistance of a 60-W bulb if a current of 500 mA results from an applied voltage of 120 V.

Solution:

$$R = \frac{V}{I} = \frac{120}{500 \times 10^{-3}} = 240\Omega$$

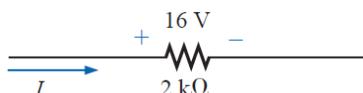
EXAMPLE: Calculate the current through the 2-k Ω resistor of Figure below if the voltage drop across it is 16 V.



Solution:

$$I = \frac{V}{R} = \frac{16 V}{2 \times 10^3 \Omega} = 8 \text{ mA}$$

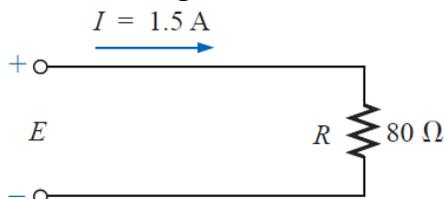EXAMPLE: Calculate the voltage that must be applied across the soldering iron of Figure below to establish a current of 1.5 A through the iron if its internal resistance is 80 Ω .



Solution:

$$E = IR = (1.5 A)(80 \Omega) = 120 V$$

EXAMPLE: What is the power dissipated by a 5 Ω resistor if the current is 4 A?

Solution:

$$P = I^2 R = (4 A)^2 (5 \Omega) = 80 W$$

EXAMPLE: Determine the current through a 5-k Ω resistor when the power dissipated by the element is 20 mW.

Solution:



$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{20 \times 10^{-3} \text{ W}}{5 \times 10^3 \Omega}} = \sqrt{4 \times 10^{-6}} = 2 \times 10^{-3} \text{ A} \\ = 2 \text{ mA}$$

الوحدة الثالثة -الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على الدوائر المتسلسلة

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

م	الأساليب والأنشطة التعليمية	الوسائل التعليمية
2	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام

Series Circuits:

Two elements are in series if

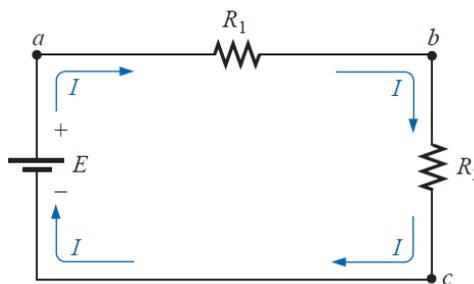1. They have only one terminal in common (i.e., one lead of one is connected to only one lead of the other).
2. The common point between the two elements is not connected to another current-carrying element.



- The current is the same through series elements, but the voltage is different.
- The total resistance of a series circuit is the sum of the resistance levels.


$$R_T = R_1 + R_2 + R_3 + \dots + R_N$$

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3, \dots, V_N = IR_N$$



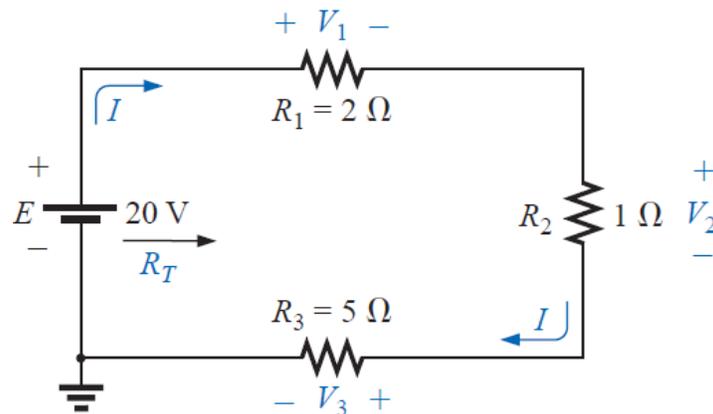EXAMPLE: for the figure below

- Find the total resistance for the series circuit.
- Calculate the source current I_s .
- Determine the voltages V_1 , V_2 , and V_3 .
- Calculate the power dissipated by R_1 , R_2 , and R_3 .
- Determine the power delivered by the source, and compare it to the sum of the power levels of part (d).



Solution:

a. $R_T = R_1 + R_2 + R_3 = 2 \Omega + 1 \Omega + 5 \Omega = 8 \Omega$


b. $I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{8 \Omega} = 2.5 \text{ A}$

c. $V_1 = IR_1 = (2.5 \text{ A})(2 \Omega) = 5 \text{ V}$
 $V_2 = IR_2 = (2.5 \text{ A})(1 \Omega) = 2.5 \text{ V}$
 $V_3 = IR_3 = (2.5 \text{ A})(5 \Omega) = 12.5 \text{ V}$

d. $P_1 = V_1 I_1 = (5 \text{ V})(2.5 \text{ A}) = 12.5 \text{ W}$
 $P_2 = I_2^2 R_2 = (2.5 \text{ A})^2 (1 \Omega) = 6.25 \text{ W}$
 $P_3 = V_3^2 / R_3 = (12.5 \text{ V})^2 / 5 \Omega = 31.25 \text{ W}$

e. $P_{\text{del}} = EI = (20 \text{ V})(2.5 \text{ A}) = 50 \text{ W}$
 $P_{\text{del}} = P_1 + P_2 + P_3$
 $50 \text{ W} = 12.5 \text{ W} + 6.25 \text{ W} + 31.25 \text{ W}$
 $50 \text{ W} = 50 \text{ W}$ (checks)

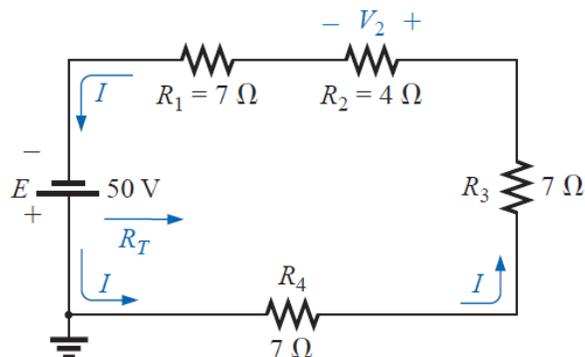EXAMPLE: Determine R_T , I , and V_2 for the circuit of Figure below.




Solution: Note the current direction as established by the battery and the polarity of the voltage drops across R_2 as determined by the current direction. Since $R_1 = R_3 = R_4$,

$$R_T = NR_1 + R_2 = (3)(7 \Omega) + 4 \Omega = 21 \Omega + 4 \Omega = 25 \Omega$$

$$I = \frac{E}{R_T} = \frac{50 \text{ V}}{25 \Omega} = 2 \text{ A}$$

$$V_2 = IR_2 = (2 \text{ A})(4 \Omega) = 8 \text{ V}$$

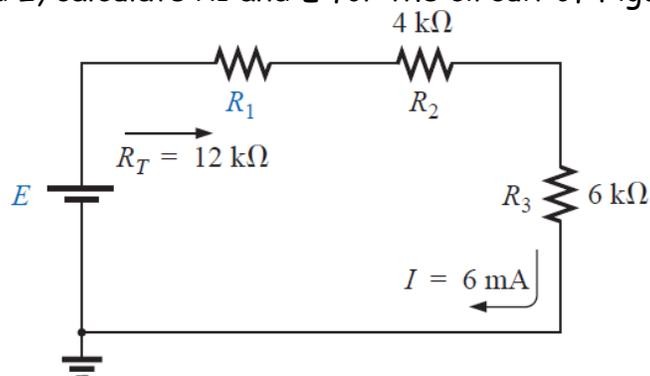EXAMPLE: Given R_T and I , calculate R_1 and E for the circuit of Figure below.



Solution:

$$R_T = R_1 + R_2 + R_3$$


$$12 \text{ k}\Omega = R_1 + 4 \text{ k}\Omega + 6 \text{ k}\Omega$$

$$R_1 = 12 \text{ k}\Omega - 10 \text{ k}\Omega = 2 \text{ k}\Omega$$


$$E = IR_T = (6 \times 10^{-3} \text{ A})(12 \times 10^3 \Omega) = 72 \text{ V}$$

Voltage Sources in Series:

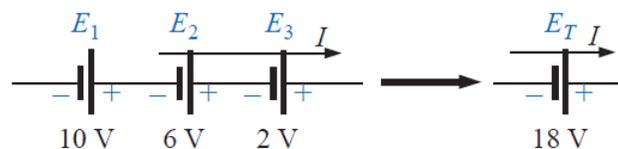Voltage sources can be connected in series as shown in figure below. The net voltage is determined simply by summing the sources with the same polarity and subtracting the total of the sources with the opposite.




(a)

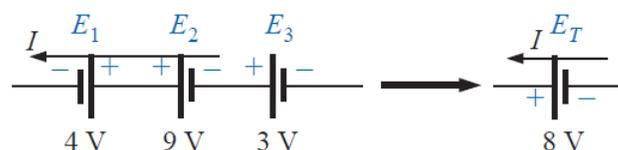

(b)

Interchanging Series Elements:

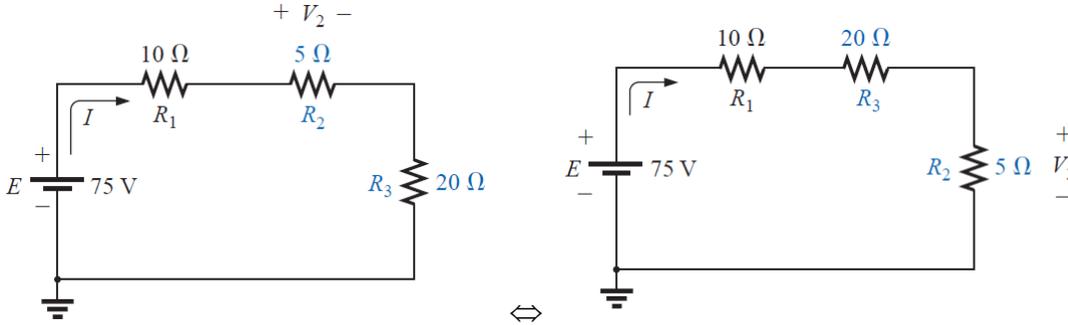The elements of a series circuit can be interchanged without affecting the total resistance, current, or power to each element.



الوحدة الرابعة - الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على قوانين الفولتية في الدوائر المتسلسلة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none"> • جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام 	<ul style="list-style-type: none"> • نشاط التعارف • محاضرة • مناقشة • سؤال وجواب 	4



VOLTAGE DIVIDER RULE:

In a series circuit,

the voltage across a resistor in a series circuit is equal to the value of that resistor times the total impressed voltage across the series elements divided by the total resistance of the series elements.


$$V_x = \frac{R_x E}{R_T}$$

Where V_x is the voltage across R_x .


For example:

$$V_1 = IR_1 = \left(\frac{E}{R_T}\right)R_1 = \frac{R_1E}{R_T}$$
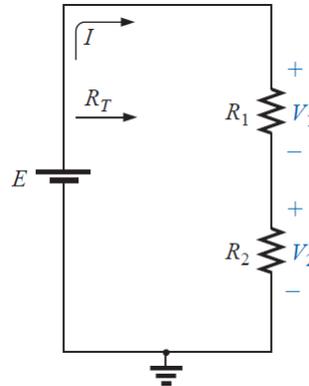
$$V_2 = IR_2 = \left(\frac{E}{R_T}\right)R_2 = \frac{R_2E}{R_T}$$



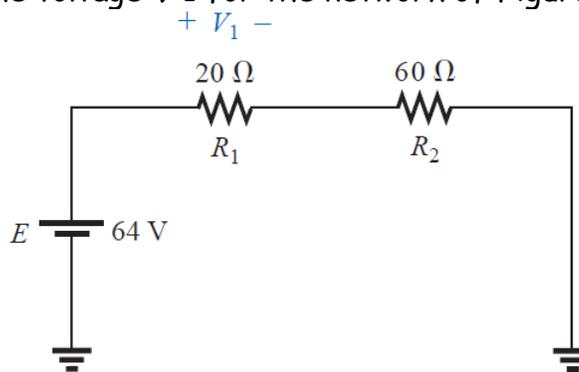
EXAMPLE: Determine the voltage V_1 for the network of Figure below.



Solution:

$$V_1 = \frac{R_1E}{R_T} = \frac{R_1E}{R_1 + R_2} = \frac{(20 \Omega)(64 \text{ V})}{20 \Omega + 60 \Omega} = \frac{1280 \text{ V}}{80} = 16 \text{ V}$$

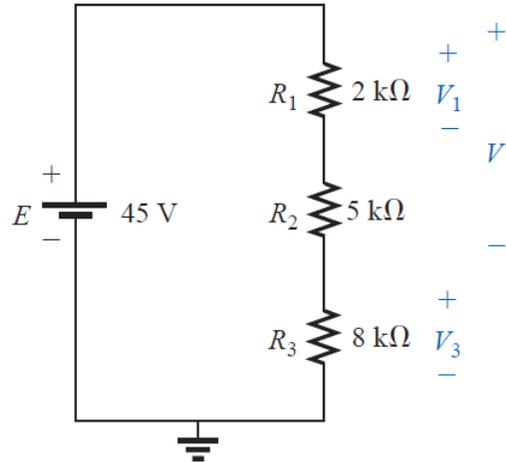EXAMPLE: Using the voltage divider rule, determine the voltages V_1 and V_3 for the series circuit of Figure below.



Solution:


$$V_1 = \frac{R_1 E}{R_T} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega}$$

$$= \frac{(2 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} = \frac{90 \text{ V}}{15} = 6 \text{ V}$$

$$V_3 = \frac{R_3 E}{R_T} = \frac{(8 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} = \frac{(8 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega}$$

$$= \frac{360 \text{ V}}{15} = 24 \text{ V}$$

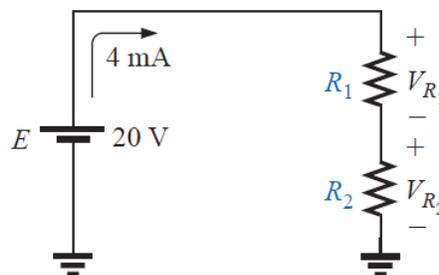EXAMPLE: Design the voltage divider of Figure below such that $V_{R1} = 4V_{R2}$.



Solution: The total resistance is defined by

$$R_T = \frac{E}{I} = \frac{20 \text{ V}}{4 \text{ mA}} = 5 \text{ k}\Omega$$

Since $V_{R_1} = 4V_{R_2}$,



$$R_1 = 4R_2$$



Thus $R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$

and $5R_2 = 5 \text{ k}\Omega$
 $R_2 = 1 \text{ k}\Omega$


and $R_1 = 4R_2 = 4 \text{ k}\Omega$

NOTATION:

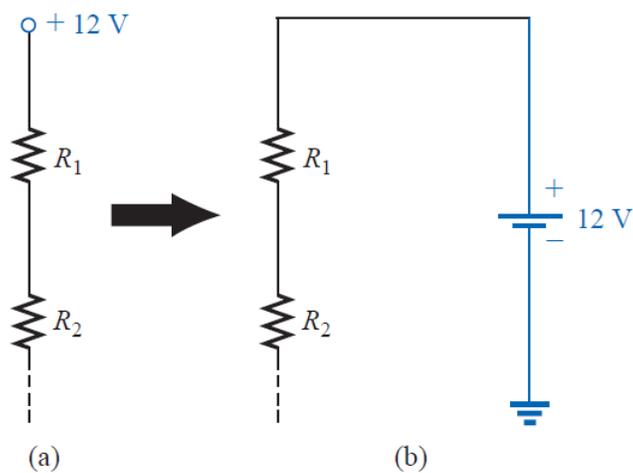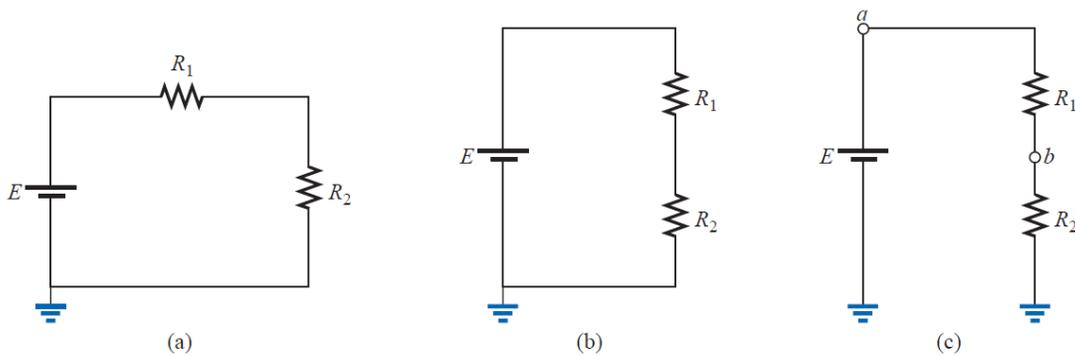

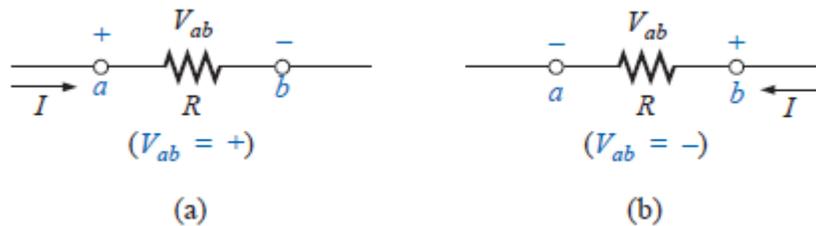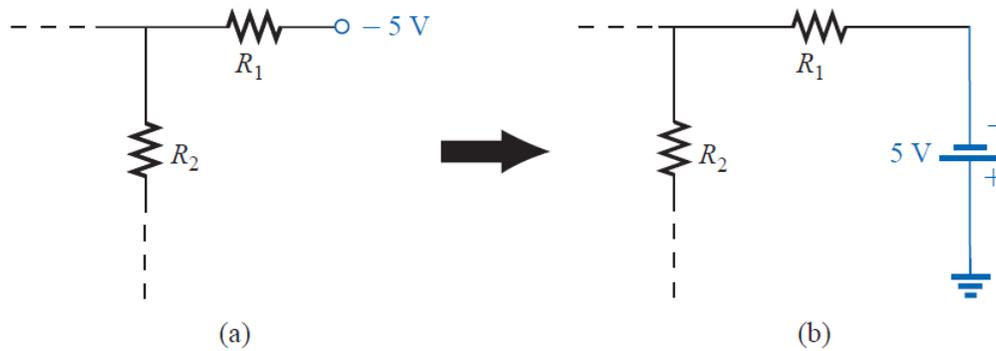

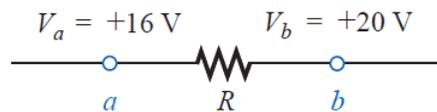
EXAMPLE: Find the voltage V_{ab} for the conditions.



Solution:

$$V_{ab} = V_a - V_b = 16\text{ V} - 20\text{ V} \\ = -4\text{ V}$$

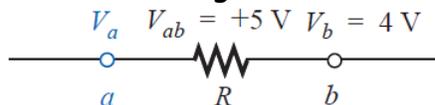EXAMPLE: Find the voltage V_a for the configuration.




Solution:

$$V_{ab} = V_a - V_b$$

$$V_a = V_{ab} + V_b = 5\text{ V} + 4\text{ V} \\ = 9\text{ V}$$



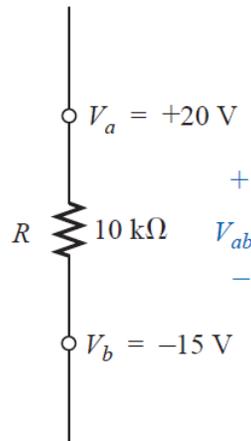EXAMPLE: Find the voltage V_{ab} for the configuration.



Solution:

$$\begin{aligned} V_{ab} &= V_a - V_b = 20 \text{ V} - (-15 \text{ V}) = 20 \text{ V} + 15 \text{ V} \\ &= 35 \text{ V} \end{aligned}$$

الوحدة الخامسة - الزمن: 90 دقيقة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على الدوائر المتوازية
موضوعات المحاضرة




امثلة

الأساليب والأنشطة والوسائل التعليمية


الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	5

Parallel Circuits:

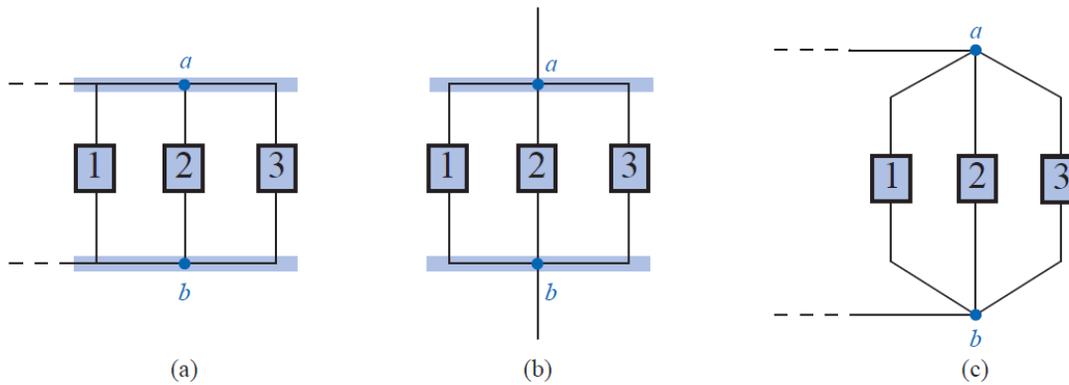Two elements, branches, or networks are in parallel if they have two points in common.



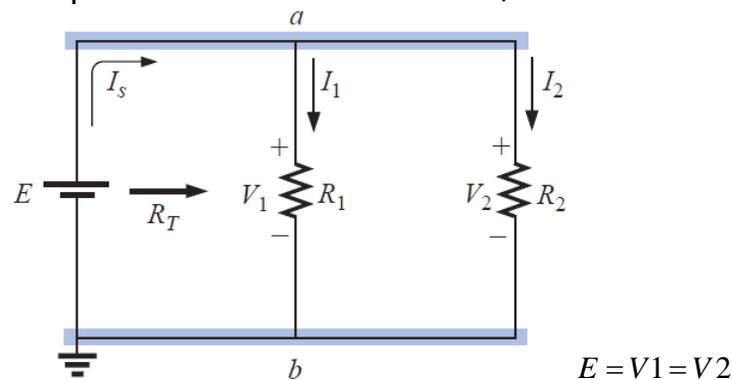
- The voltage across parallel elements is the same, but the current is different.




- For parallel elements, the total conductance is the sum of the individual conductances.
- The total resistance of parallel resistors is always less than the value of the smallest resistor.

$$G_T = G_1 + G_2 + G_3 + \dots + G_N$$
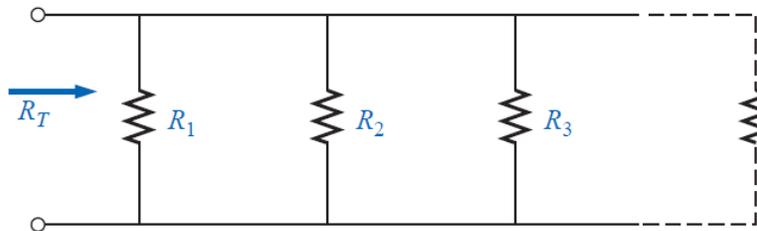
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$



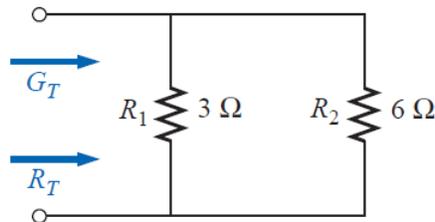EXAMPLE: Determine the total conductance and resistance for the parallel network.




Solution:

$$G_T = G_1 + G_2 = \frac{1}{3 \Omega} + \frac{1}{6 \Omega} = 0.333 \text{ S} + 0.167 \text{ S} = \mathbf{0.5 \text{ S}}$$

and
$$R_T = \frac{1}{G_T} = \frac{1}{0.5 \text{ S}} = \mathbf{2 \Omega}$$

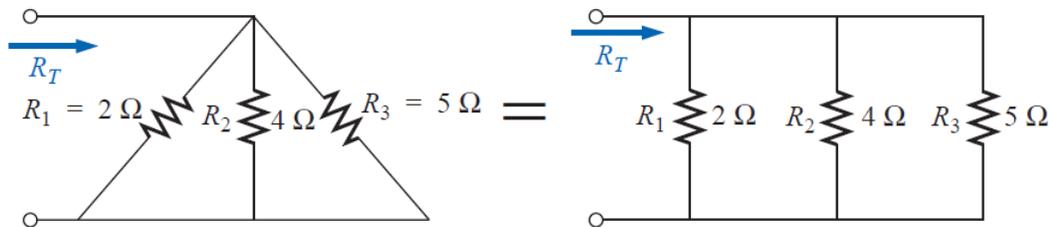EXAMPLE: Determine the total resistance for the network.



Solution:


$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{2 \Omega} + \frac{1}{4 \Omega} + \frac{1}{5 \Omega} = 0.5 \text{ S} + 0.25 \text{ S} + 0.2 \text{ S} \\ &= 0.95 \text{ S} \end{aligned}$$

and $R_T = \frac{1}{0.95 \text{ S}} = 1.053 \Omega$

* The total resistance of two parallel resistors is the product of the two divided by their sum.

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

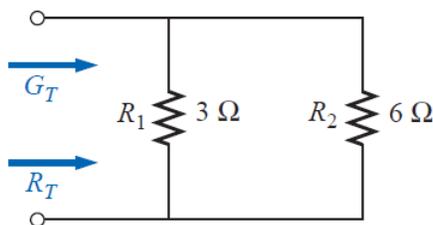
EXAMPLE: Determine the total conductance and resistance for the parallel network.



Solution:

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 6 \Omega} = \frac{18 \Omega}{9} = 2 \Omega$$

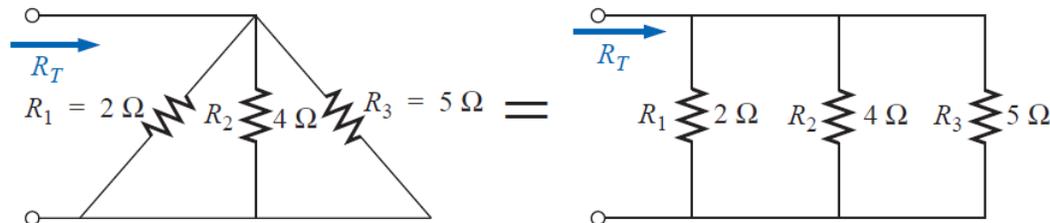EXAMPLE: Determine the total resistance for the network.




Solution:



$$R'_T = 2 \Omega \parallel 4 \Omega = \frac{(2 \Omega)(4 \Omega)}{2 \Omega + 4 \Omega} = \frac{4}{3} \Omega$$

$$R_T = R'_T \parallel 5 \Omega = \frac{\left(\frac{4}{3} \Omega\right)(5 \Omega)}{\frac{4}{3} \Omega + 5 \Omega} = 1.053 \Omega$$

EXAMPLE: For the parallel network.

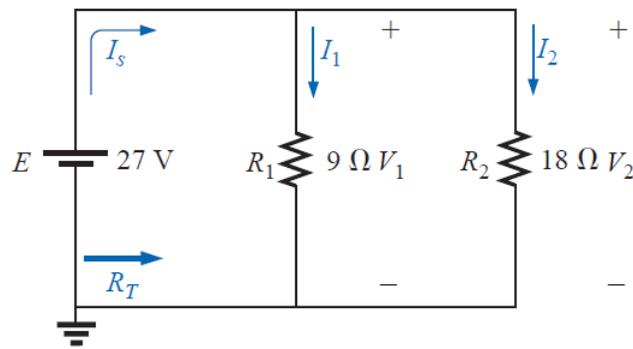

- Calculate R_T .
- Determine I_s .
- Calculate I_1 and I_2 , and demonstrate that $I_s = I_1 + I_2$.
- Determine the power to each resistive load.
- Determine the power delivered by the source, and compare it to the total power dissipated by the resistive elements.

Solution:

$$a. R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9 \Omega)(18 \Omega)}{9 \Omega + 18 \Omega} = \frac{162 \Omega}{27} = 6 \Omega$$

$$b. I_s = \frac{E}{R_T} = \frac{27 \text{ V}}{6 \Omega} = 4.5 \text{ A}$$

$$c. I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27 \text{ V}}{9 \Omega} = 3 \text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27 \text{ V}}{18 \Omega} = 1.5 \text{ A}$$

$$I_s = I_1 + I_2$$

$$4.5 \text{ A} = 3 \text{ A} + 1.5 \text{ A}$$

$$4.5 \text{ A} = 4.5 \text{ A} \quad (\text{checks})$$

$$d. P_1 = V_1 I_1 = E I_1 = (27 \text{ V})(3 \text{ A}) = 81 \text{ W}$$


$$P_2 = V_2 I_2 = E I_2 = (27 \text{ V})(1.5 \text{ A}) = 40.5 \text{ W}$$

$$e. P_s = E I_s = (27 \text{ V})(4.5 \text{ A}) = 121.5 \text{ W}$$

$$= P_1 + P_2 = 81 \text{ W} + 40.5 \text{ W} = 121.5 \text{ W}$$

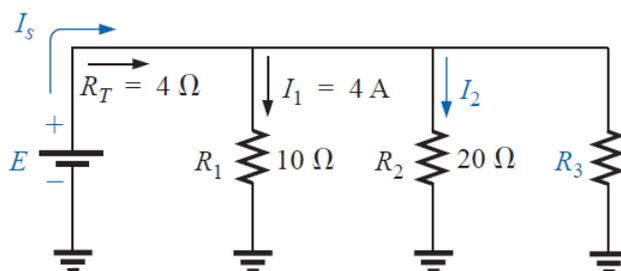EXAMPLE: Given the information provided.

- Determine R_3 .
- Calculate E .
- Find I_s .
- Find I_2 .
- Determine P_2 .



Solution:



a.
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
$$\frac{1}{4 \Omega} = \frac{1}{10 \Omega} + \frac{1}{20 \Omega} + \frac{1}{R_3}$$
$$0.25 \text{ S} = 0.1 \text{ S} + 0.05 \text{ S} + \frac{1}{R_3}$$
$$0.25 \text{ S} = 0.15 \text{ S} + \frac{1}{R_3}$$
$$\frac{1}{R_3} = 0.1 \text{ S}$$
$$R_3 = \frac{1}{0.1 \text{ S}} = \mathbf{10 \Omega}$$

b. $E = V_1 = I_1 R_1 = (4 \text{ A})(10 \Omega) = \mathbf{40 \text{ V}}$

c. $I_s = \frac{E}{R_T} = \frac{40 \text{ V}}{4 \Omega} = \mathbf{10 \text{ A}}$

d. $I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{40 \text{ V}}{20 \Omega} = \mathbf{2 \text{ A}}$

e. $P_2 = I_2^2 R_2 = (2 \text{ A})^2 (20 \Omega) = \mathbf{80 \text{ W}}$



الوحدة السادسة - الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:


التعرف على قوانين التيار
موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

م	الأساليب والأنشطة التعليمية	الوسائل التعليمية
6	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام

CURRENT DIVIDER RULE:

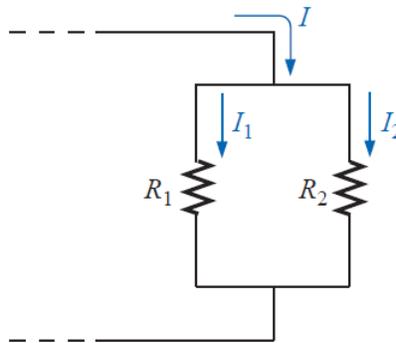- For two parallel elements of equal value, the current will divide equally.
- For parallel elements with different values, the smaller the resistance, the greater the share of input current.
- For parallel elements of different values, the current will split with a ratio equal to the inverse of their resistor values.




Note difference in subscripts.

$$I_1 = \frac{R_2 I}{R_1 + R_2}$$

$$I_2 = \frac{R_1 I}{R_1 + R_2}$$

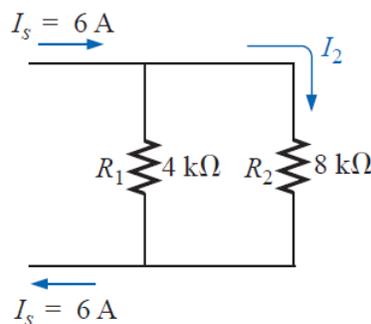EXAMPLE: Determine the current I_2 for the network using the current divider rule.




Solution:

$$I_2 = \frac{R_1 I_s}{R_1 + R_2} = \frac{(4 \text{ k}\Omega)(6 \text{ A})}{4 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{4}{12}(6 \text{ A}) = \frac{1}{3}(6 \text{ A})$$

$$= 2 \text{ A}$$

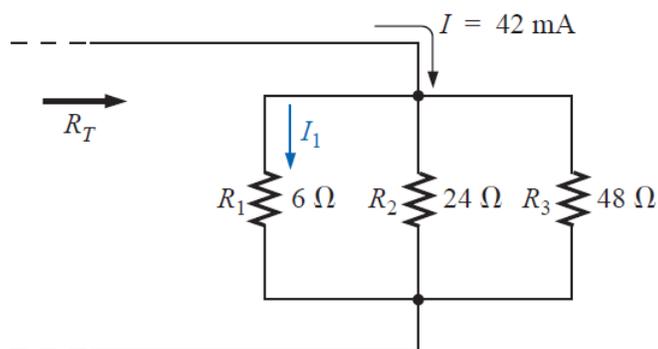EXAMPLE: Find the current I_1 for the network.




Solution:

$$24 \Omega \parallel 48 \Omega = \frac{(24 \Omega)(48 \Omega)}{24 \Omega + 48 \Omega} = 16 \Omega$$

$$I_1 = \frac{16 \Omega(42 \text{ mA})}{16 \Omega + 6 \Omega} = 30.54 \text{ mA}$$

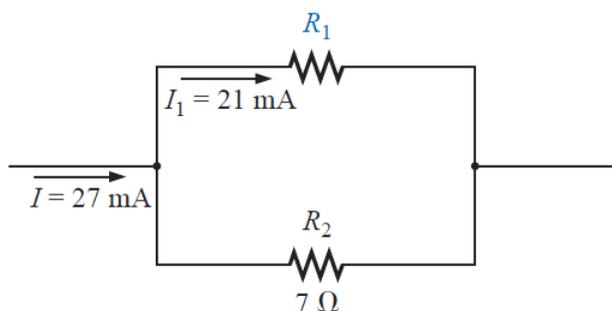EXAMPLE: Determine the resistance R_1 to effect the division of current.



Solution:

$$I_1 = \frac{R_2 I}{R_1 + R_2}$$



$$(R_1 + R_2)I_1 = R_2I$$

$$R_1I_1 + R_2I_1 = R_2I$$

$$R_1I_1 = R_2I - R_2I_1$$

$$R_1 = \frac{R_2(I - I_1)}{I_1}$$

$$R_1 = \frac{7 \Omega(27 \text{ mA} - 21 \text{ mA})}{21 \text{ mA}}$$

$$= 7 \Omega \left(\frac{6}{21} \right) = \frac{42 \Omega}{21} = 2 \Omega$$



الوحدة السابعة - الزمن: 90 دقيقة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

التعرف على الدوائر القصيرة المفتوحة


موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية


الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	7

Open and Short Circuits:

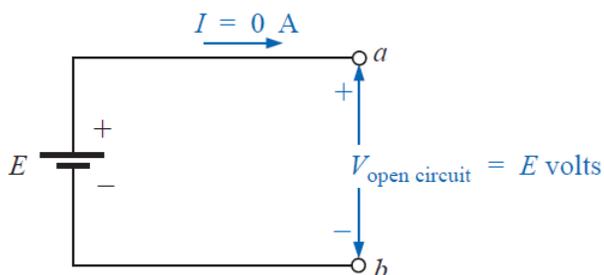
An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero amperes.



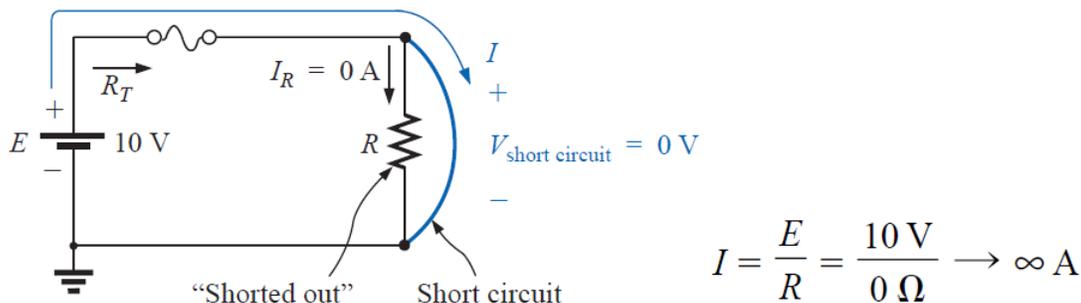A short circuit can carry a current of a level determined by the external circuit, but the potential difference (voltage) across its terminals is always zero volts.



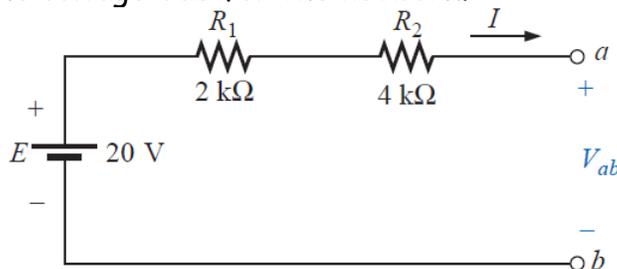
EXAMPLE: Determine the voltage V_{ab} for the network.



Solution:

$$V_{ab} = E = 20 \text{ V}$$

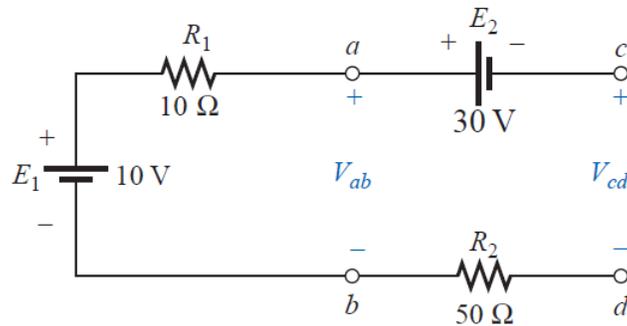EXAMPLE: Determine the voltages V_{ab} and V_{cd} for the network.




Solution:

$$V_{ab} = E_1 = 10 \text{ V}$$

$$+E_1 - E_2 - V_{cd} = 0$$

$$V_{cd} = E_1 - E_2 = 10 \text{ V} - 30 \text{ V} = -20 \text{ V}$$

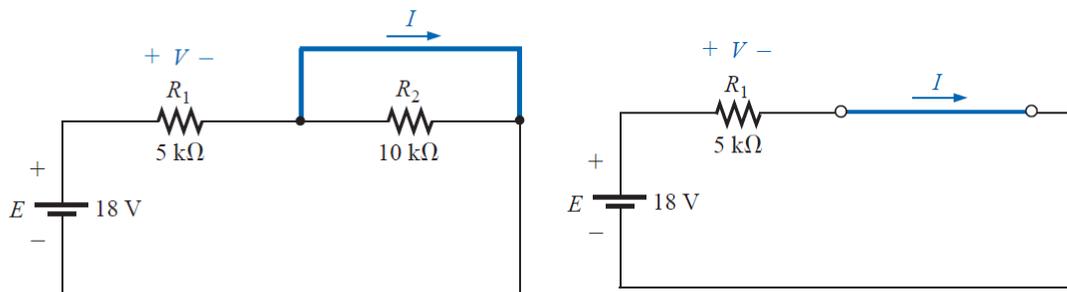EXAMPLE: Calculate the current I and the voltage V for the network.



Solution:

$$I = \frac{E}{R_1} = \frac{18 \text{ V}}{5 \text{ k}\Omega} = 3.6 \text{ mA}$$

$$V = E = 18 \text{ V}$$

الوحدة الثامنة- الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Series-parallel networks are networks that contain both series and parallel circuit configurations

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	8

Series-Parallel Networks:

Series-parallel networks are networks that contain both series and parallel circuit configurations.

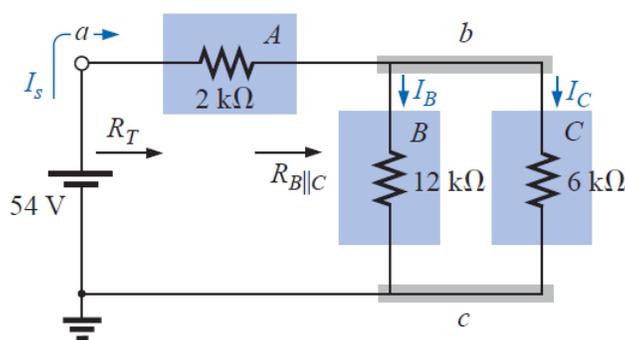
EXAMPLE: for the network find R_T , I_s , I_A , I_B , and I_C .



Solution:

$$R_{B\parallel C} = R_B \parallel R_C = \frac{(12 \text{ k}\Omega)(6 \text{ k}\Omega)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = 4 \text{ k}\Omega$$
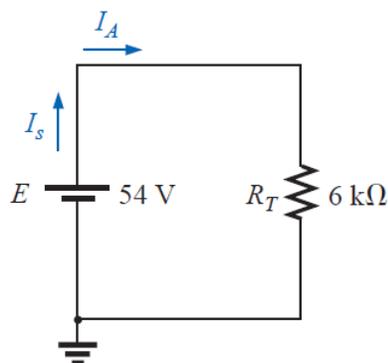
$$R_T = R_A + R_{B\parallel C} \\ = 2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega$$




$$I_s = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}\Omega} = 9 \text{ mA}$$


$$I_A = I_s = 9 \text{ mA}$$

$$I_B = \frac{6 \text{ k}\Omega(I_s)}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = \frac{6}{18} I_s = \frac{1}{3} (9 \text{ mA}) = 3 \text{ mA}$$
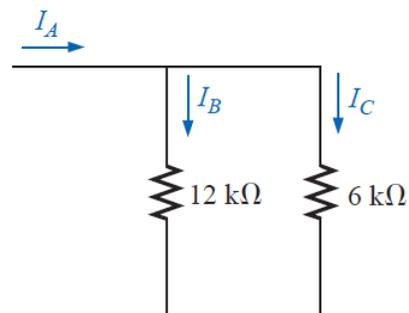
$$I_C = \frac{12 \text{ k}\Omega(I_s)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{12}{18} I_s = \frac{2}{3} (9 \text{ mA}) = 6 \text{ mA}$$



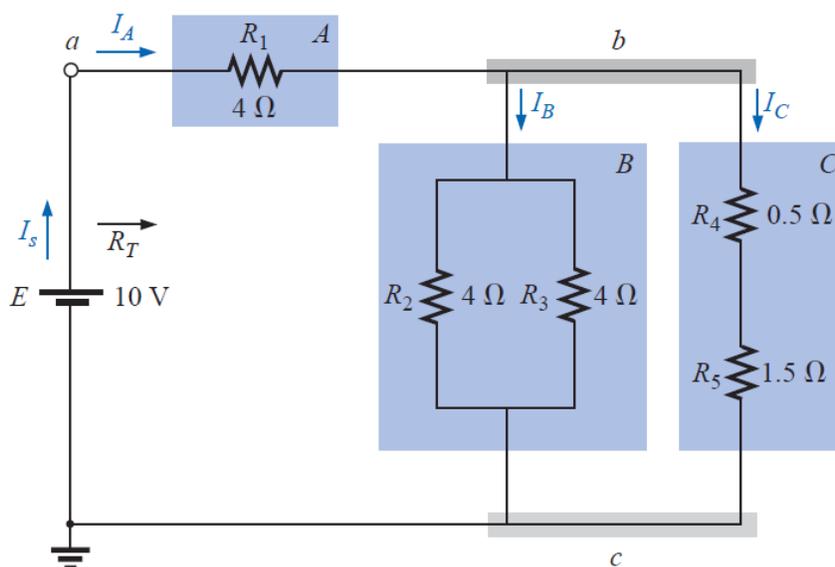EXAMPLE: for the network find the currents and voltage for each element.




Solution:

$$A: R_A = 4 \Omega$$

$$B: R_B = R_2 \parallel R_3 = R_{2\parallel 3} = \frac{R}{N} = \frac{4 \Omega}{2} = 2 \Omega$$
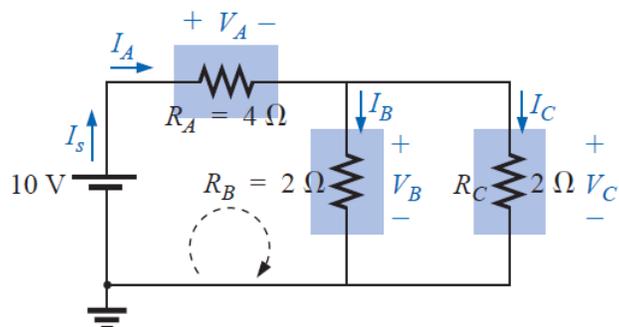
$$C: R_C = R_4 + R_5 = R_{4,5} = 0.5 \Omega + 1.5 \Omega = 2 \Omega$$



$$R_{B\parallel C} = \frac{R}{N} = \frac{2 \Omega}{2} = 1 \Omega$$

$$R_T = R_A + R_{B\parallel C} \\ = 4 \Omega + 1 \Omega = 5 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$

$$I_A = I_s = 2 \text{ A}$$

$$I_B = I_C = \frac{I_A}{2} = \frac{I_s}{2} = \frac{2 \text{ A}}{2} = 1 \text{ A}$$



$$I_{R_2} = I_{R_3} = \frac{I_B}{2} = 0.5 \text{ A}$$

$$V_A = I_A R_A = (2 \text{ A})(4 \Omega) = 8 \text{ V}$$

$$V_B = I_B R_B = (1 \text{ A})(2 \Omega) = 2 \text{ V}$$

$$V_C = V_B = 2 \text{ V}$$

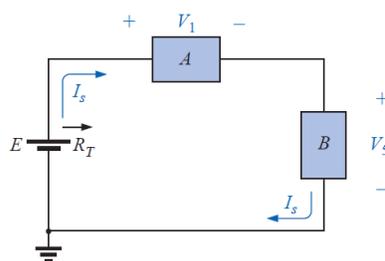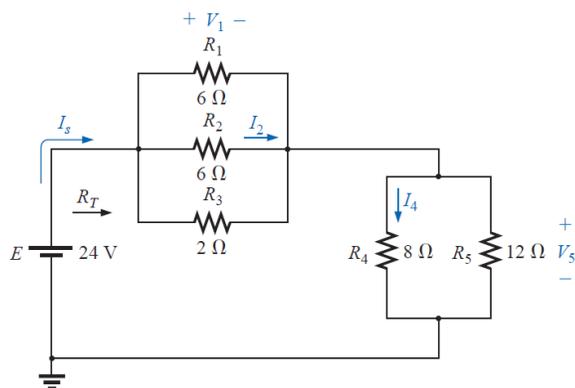EXAMPLE: for the network find the currents and voltage for each element.




Solution:

$$R_{1\parallel 2} = \frac{R}{N} = \frac{6 \Omega}{2} = 3 \Omega$$

$$R_A = R_{1\parallel 2\parallel 3} = \frac{(3 \Omega)(2 \Omega)}{3 \Omega + 2 \Omega} = \frac{6 \Omega}{5} = 1.2 \Omega$$
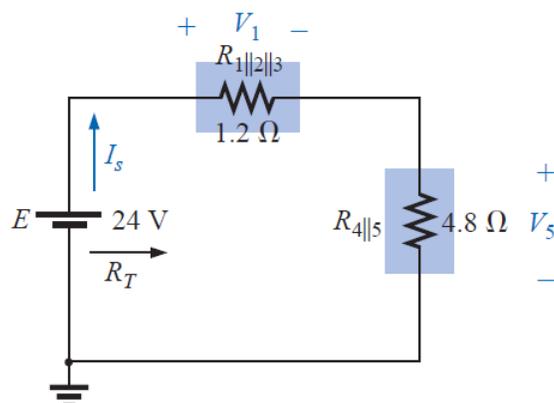
$$R_B = R_{4\parallel 5} = \frac{(8 \Omega)(12 \Omega)}{8 \Omega + 12 \Omega} = \frac{96 \Omega}{20} = 4.8 \Omega$$



$$R_T = R_{1\parallel 2\parallel 3} + R_{4\parallel 5} = 1.2 \Omega + 4.8 \Omega = 6 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{24 \text{ V}}{6 \Omega} = 4 \text{ A}$$

$$V_1 = I_s R_{1\parallel 2\parallel 3} = (4 \text{ A})(1.2 \Omega) = 4.8 \text{ V}$$


$$V_5 = I_s R_{4\parallel 5} = (4 \text{ A})(4.8 \Omega) = 19.2 \text{ V}$$

$$I_4 = \frac{V_5}{R_4} = \frac{19.2 \text{ V}}{8 \Omega} = 2.4 \text{ A}$$


$$I_2 = \frac{V_2}{R_2} = \frac{V_1}{R_2} = \frac{4.8 \text{ V}}{6 \Omega} = 0.8 \text{ A}$$

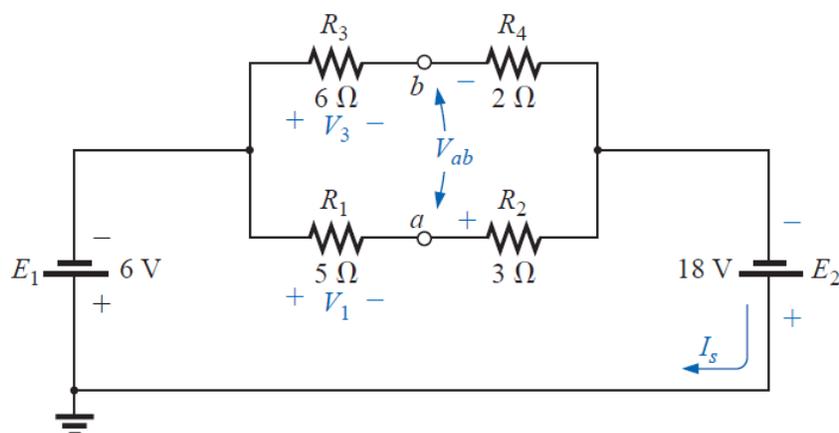EXAMPLE:

- Find the voltages V_1 , V_3 , and V_{ab} for the network.
- Calculate the source current I_s .



Solution:

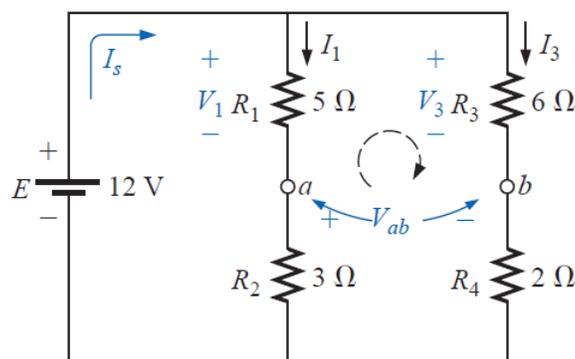

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5 \Omega)(12 \text{ V})}{5 \Omega + 3 \Omega} = \frac{60 \text{ V}}{8} = 7.5 \text{ V}$$

$$V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6 \Omega)(12 \text{ V})}{6 \Omega + 2 \Omega} = \frac{72 \text{ V}}{8} = 9 \text{ V}$$

$$+V_1 - V_3 + V_{ab} = 0$$


$$V_{ab} = V_3 - V_1 = 9 \text{ V} - 7.5 \text{ V} = 1.5 \text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{7.5 \text{ V}}{5 \Omega} = 1.5 \text{ A}$$


$$I_3 = \frac{V_3}{R_3} = \frac{9 \text{ V}}{6 \Omega} = 1.5 \text{ A}$$

$$I_s = I_1 + I_3 = 1.5 \text{ A} + 1.5 \text{ A} = 3 \text{ A}$$

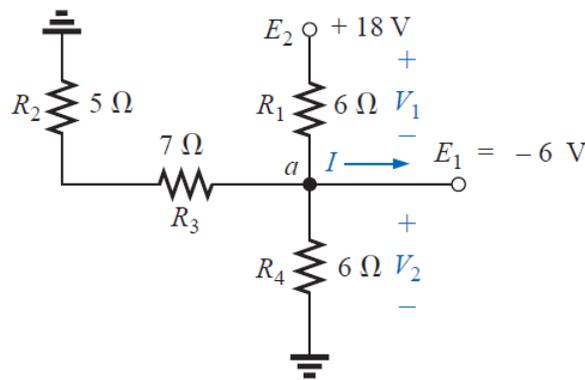EXAMPLE: For the network, determine the voltages V_1 and V_2 and the current I .



Solution:

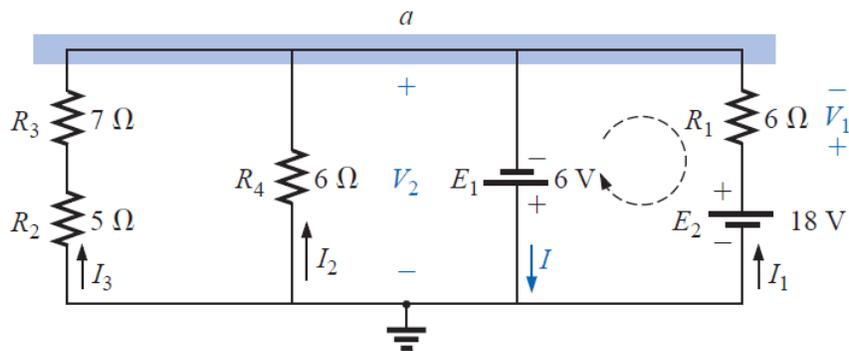

$$V_2 = -E_1 = -6 \text{ V}$$

$$-E_1 + V_1 - E_2 = 0$$

$$V_1 = E_2 + E_1 = 18 \text{ V} + 6 \text{ V} = 24 \text{ V}$$



$$\begin{aligned} I &= I_1 + I_2 + I_3 \\ &= \frac{V_1}{R_1} + \frac{E_1}{R_4} + \frac{E_1}{R_2 + R_3} \\ &= \frac{24 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{12 \Omega} \\ &= 4 \text{ A} + 1 \text{ A} + 0.5 \text{ A} \\ I &= 5.5 \text{ A} \end{aligned}$$



الوحدة التاسعة- الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

* Kirchhoff's current law (KCL) states that the algebraic sum of the currents entering and leaving an area, system, or junction is zero.

موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	9


Kirchoff's Laws

* Kirchoff's current law (KCL) states that the algebraic sum of the currents entering and leaving an area, system, or junction is zero.

Or,

* The sum of the currents entering an area, system, or junction must equal the sum of the currents leaving the area, system, or junction.

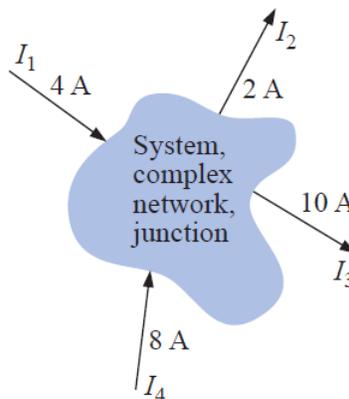
$$\Sigma I_{\text{entering}} = \Sigma I_{\text{leaving}}$$



$$\begin{aligned} I_1 + I_4 &= I_2 + I_3 \\ 4 \text{ A} + 8 \text{ A} &= 2 \text{ A} + 10 \text{ A} \\ 12 \text{ A} &= 12 \text{ A} \end{aligned}$$

* Kirchoff's voltage law (KVL) states that the algebraic sum of the potential rises and drops around a closed loop (or path) is zero.


$$\Sigma_{\text{loop}} V = 0$$

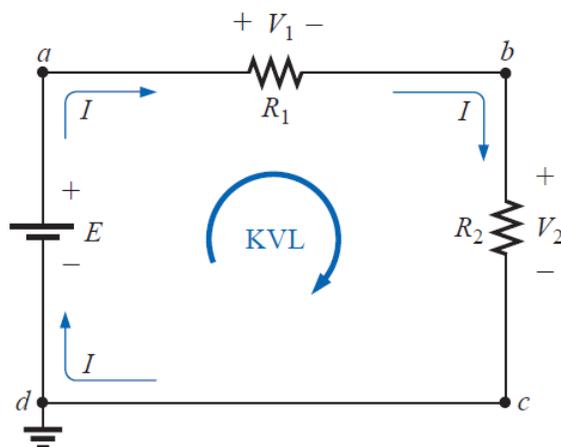

$$+E - V_1 - V_2 = 0$$

$$E = V_1 + V_2$$

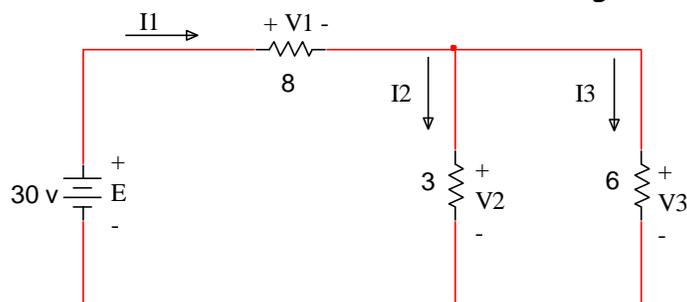EXAMPLE: using Kirchoff's laws. Find the currents and voltages in the circuit shown.



Solution:

$$E - V_1 - V_2 = 0 \quad \Rightarrow \quad 30 - V_1 - V_2 = 0$$

$$30 - 8I_1 - 3I_2 = 0 \quad \Rightarrow \quad I_1 = \frac{30 - 3I_2}{8}$$

$$V_2 - V_3 = 0 \quad \Rightarrow \quad V_2 = V_3$$

$$6I_3 = 3I_2 \quad \Rightarrow \quad I_3 = \frac{I_2}{3}$$

$$I_1 = I_2 + I_3 \quad \Rightarrow \quad I_1 - I_2 - I_3 = 0$$

By substitute I1 and I3

$$\frac{30-3I_2}{8} - I_2 - \frac{I_2}{2} = 0 \Rightarrow I_2 = 2A$$

$$I_1 = \frac{30-3I_2}{8} = \frac{30-3(2)}{8} = 3A$$


$$I_3 = \frac{I_2}{2} = \frac{2}{2} = 1A$$

$$V_1 = 8I_1 \Rightarrow V_1 = 8(3) = 24V$$

$$V_2 = 3I_2 \Rightarrow V_2 = 3(2) = 6V$$

$$V_3 = 6I_3 \Rightarrow V_3 = 6(1) = 6V$$

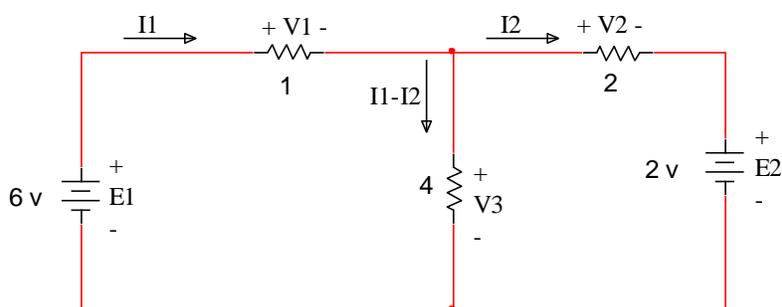EXAMPLE: using Kirchoff's laws. Find the currents and voltages in the circuit shown.



Solution:

$$I_1 + 4(I_1 - I_2) - E_1 = 0 \dots\dots\dots(1)$$

$$I_1 + 4I_1 - 4I_2 = E_1 \Rightarrow 5I_1 - 4I_2 = 6 \Rightarrow I_1 = \frac{6 + 4I_2}{5}$$

$$2I_2 + E_2 - 4(I_1 - I_2) = 0 \dots\dots\dots(2)$$

$$2I_2 - 4I_1 + 4I_2 = -E_2 \Rightarrow 6I_2 - 4I_1 = -2$$

By substitute I1

$$6I_2 - 4\left(\frac{6+4I_2}{5}\right) = -2 \Rightarrow 6I_2 - \frac{24}{5} - \frac{16I_2}{5} = -2 \Rightarrow 30I_2 - 24 - 16I_2 = -10$$

$$14I_2 = 14 \Rightarrow I_2 = \frac{14}{14} = 1A$$


$$I_1 = \frac{6+4(1)}{5} = 2A$$

$$V_1 = 1I_1 = 2V$$

$$V_2 = 2I_2 = 2(1) = 2V$$

$$V_3 = 4(I_1 - I_2) = 4(2 - 1) = 4V$$

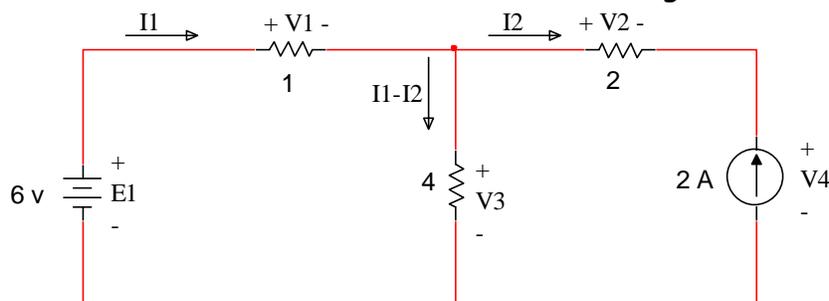EXAMPLE: using Kirchoff's lows. Find the currents and voltages in the circuit shown.



Solution:

From the circuit $I_2 = -2A$

$$I_1 + 4(I_1 - I_2) - E_1 = 0 \dots\dots\dots(1)$$

$$I_1 + 4I_1 - 4I_2 = E_1 \Rightarrow 5I_1 - 4I_2 = 6 \Rightarrow I_1 = \frac{6+4I_2}{5} = \frac{6+4(-2)}{5} = -0.4A$$

$$2I_2 + V_4 - 4(I_1 - I_2) = 0 \dots\dots\dots(2)$$

$$2I_2 - 4I_1 + 4I_2 + V_4 = 0 \Rightarrow 6I_2 - 4I_1 + V_4 = 0 \Rightarrow V_4 = 4I_1 - 6I_2 = 4(-0.4) - 6(-2) = 10.4V$$

$$V_1 = 1I_1 = -0.4V$$

$$V_2 = 2I_2 = 2(-2) = -4V$$

$$V_3 = 4(I_1 - I_2) = 4(-0.4 + 2) = 6.4V$$



الوحدة العاشرة- الزمن: 90 دقيقة

أهداف المحاضرة الثانية:

If two or more current sources are in parallel, they may all be replaced by one current source having the magnitude and direction of the resultant

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:



موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	10



Current Sources in Parallel

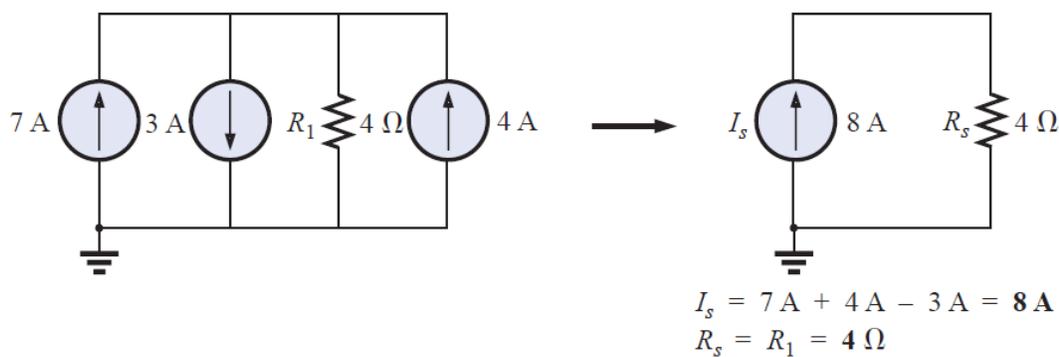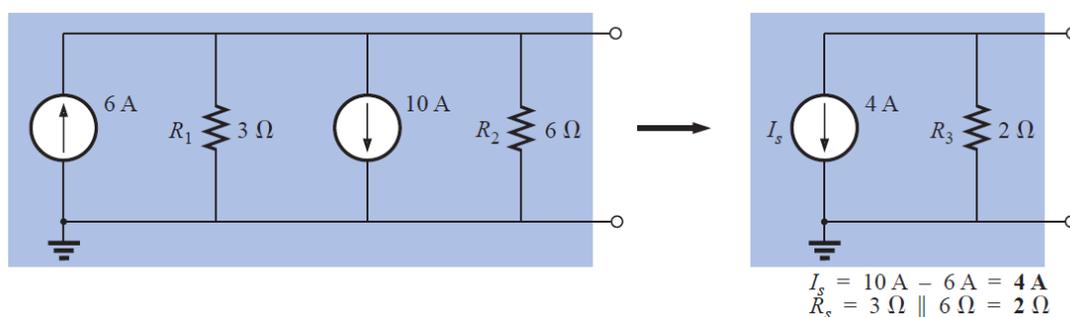If two or more current sources are in parallel, they may all be replaced by one current source having the magnitude and direction of the resultant



Y-D (T-p) and D-Y (p-T) Conversions

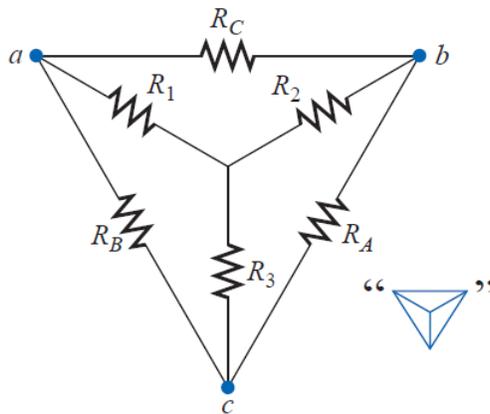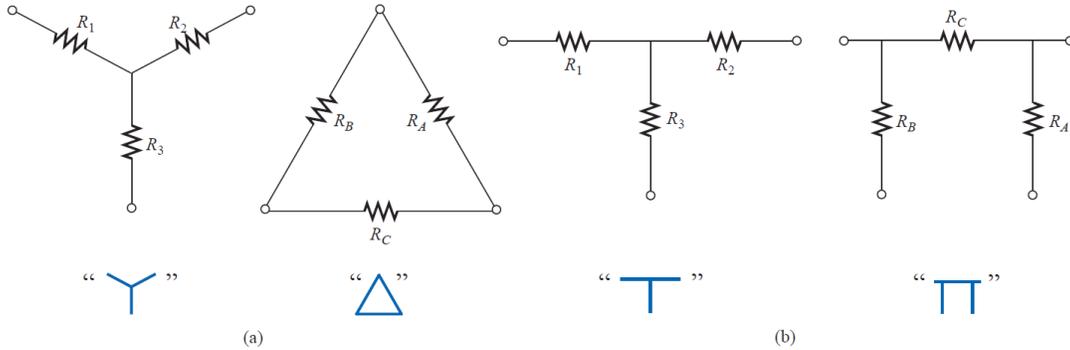Circuit configurations are often encountered in which the resistors do not appear to be in series or parallel. Under these conditions, it may be necessary to convert the circuit from one form to another.



$$\underline{\Delta \rightarrow Y}$$

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$


$$\underline{Y \rightarrow \Delta}$$

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

EXAMPLE: Convert the Δ to a Y.

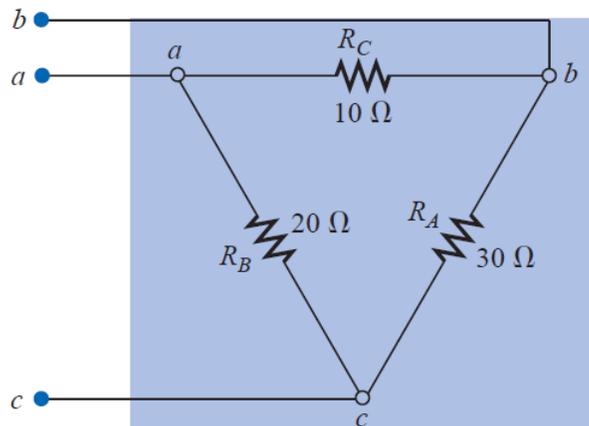


Solution:


$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(20 \Omega)(10 \Omega)}{30 \Omega + 20 \Omega + 10 \Omega} = \frac{200 \Omega}{60} = 3 \frac{1}{3} \Omega$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(30 \Omega)(10 \Omega)}{60 \Omega} = \frac{300 \Omega}{60} = 5 \Omega$$
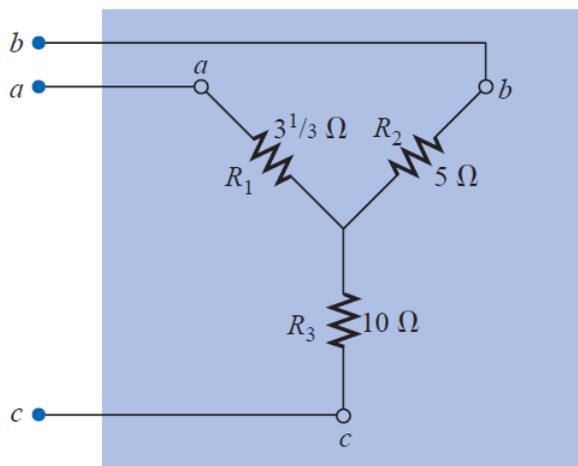
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(20 \Omega)(30 \Omega)}{60 \Omega} = \frac{600 \Omega}{60} = 10 \Omega$$



EXAMPLE: Convert the Y to a Δ .

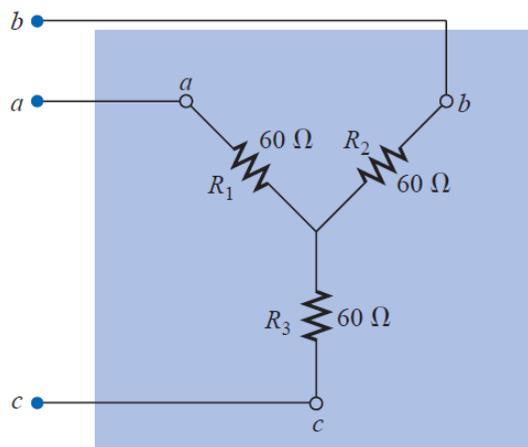


Solution:

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$


$$= \frac{(60 \Omega)(60 \Omega) + (60 \Omega)(60 \Omega) + (60 \Omega)(60 \Omega)}{60 \Omega}$$

$$= \frac{3600 \Omega + 3600 \Omega + 3600 \Omega}{60} = \frac{10,800 \Omega}{60}$$

$$R_A = 180 \Omega$$

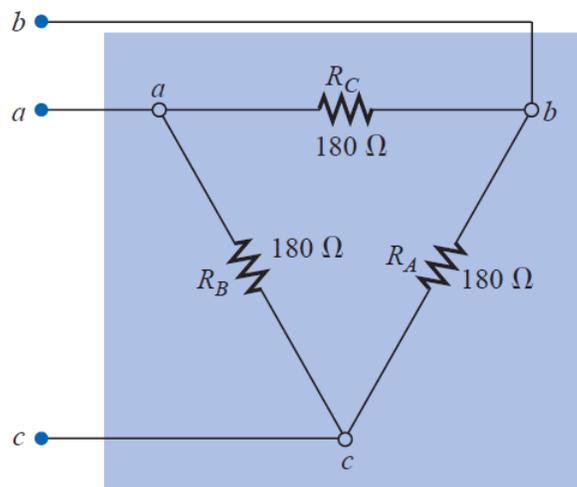

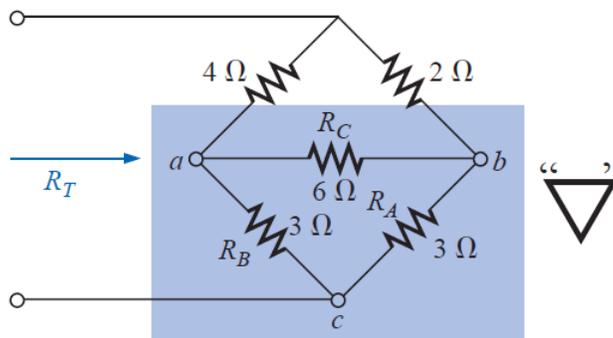EXAMPLE: Find the total resistance of the network




Solution:

Two resistors of the Δ were equal;
therefore, two resistors of the Y will
be equal.

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 3 \Omega + 6 \Omega} = \frac{18 \Omega}{12} = 1.5 \Omega \leftarrow$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3 \Omega)(6 \Omega)}{12 \Omega} = \frac{18 \Omega}{12} = 1.5 \Omega \leftarrow$$
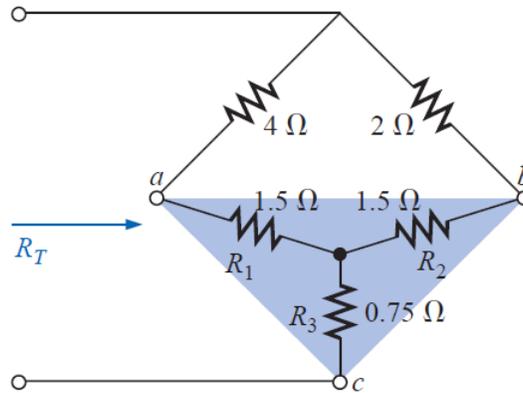
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3 \Omega)(3 \Omega)}{12 \Omega} = \frac{9 \Omega}{12} = 0.75 \Omega$$



$$\begin{aligned} R_T &= 0.75 \Omega + \frac{(4 \Omega + 1.5 \Omega)(2 \Omega + 1.5 \Omega)}{(4 \Omega + 1.5 \Omega) + (2 \Omega + 1.5 \Omega)} \\ &= 0.75 \Omega + \frac{(5.5 \Omega)(3.5 \Omega)}{5.5 \Omega + 3.5 \Omega} \\ &= 0.75 \Omega + 2.139 \Omega \\ R_T &= \mathbf{2.889 \Omega} \end{aligned}$$



الوحدة الحادية عشر الزمن: 90 دقيقة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Methods of Analysis

موضوعات المحاضرة



الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	11


Methods of Analysis

Source Conversions

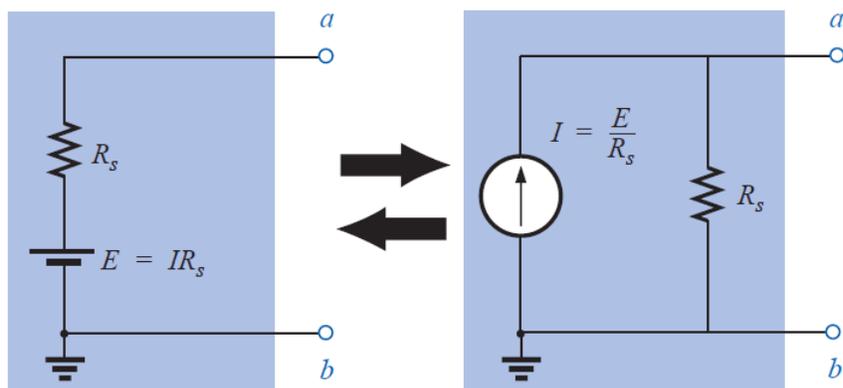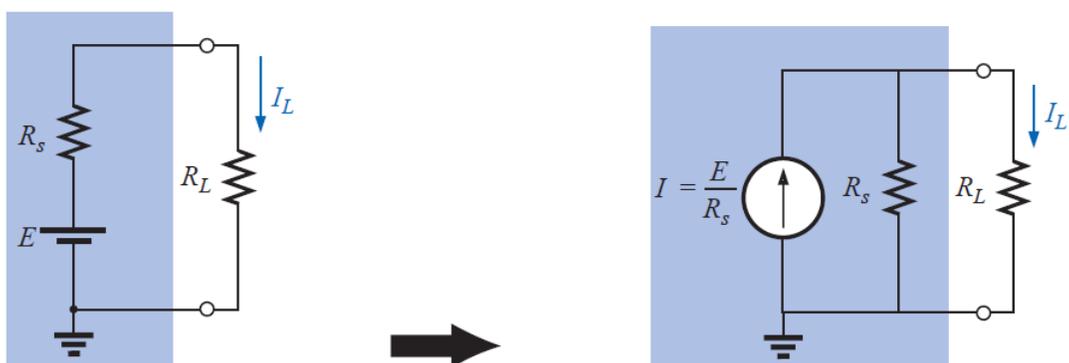To perform a conversion from one type of source to another, a voltage source must have a resistor in series with it, and a current source must have a resistor in parallel.



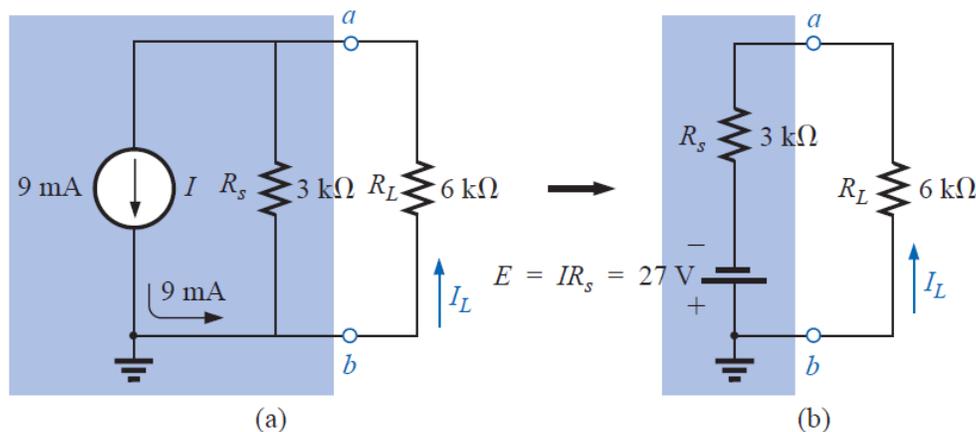EXAMPLE: Convert the current source of the circuit below to a voltage source, and find the load current for each source.



Solution:


$$(a): I_L = \frac{R_s I}{R_s + R_L} = \frac{(3 \text{ k}\Omega)(9 \text{ mA})}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = 3 \text{ mA}$$

$$(b): I_L = \frac{E}{R_s + R_L} = \frac{27 \text{ V}}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{27 \text{ V}}{9 \text{ k}\Omega} = 3 \text{ mA}$$

Mesh Analysis (Loop)

- Assign a distinct current in the clockwise direction to each independent, closed loop of the network.
- Indicate the polarities within each loop for each resistor as determined by the assumed direction of loop current for that loop.
- Write the linear equations for each loop.
- Solve the resulting linear equations for the assumed loop currents.

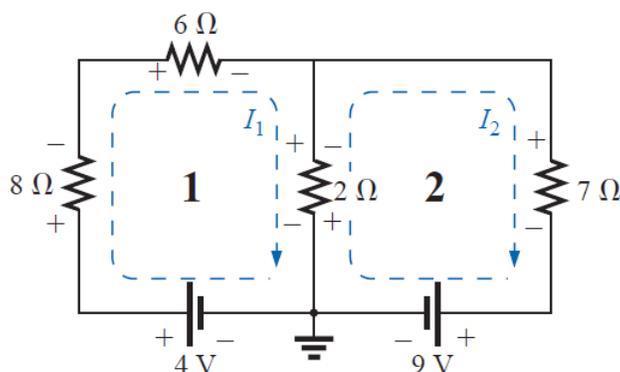EXAMPLE: Write the mesh equations for the network, and find the current through the 7-Ω resistor.



Solution:

$$I_1: (8 \Omega + 6 \Omega + 2 \Omega)I_1 - (2 \Omega)I_2 = 4 \text{ V}$$


$$I_2: (7 \Omega + 2 \Omega)I_2 - (2 \Omega)I_1 = -9 \text{ V}$$

$$\begin{aligned} 16I_1 - 2I_2 &= 4 \\ 9I_2 - 2I_1 &= -9 \end{aligned}$$

$$\begin{aligned} 16I_1 - 2I_2 &= 4 \\ -2I_1 + 9I_2 &= -9 \end{aligned}$$

$$I_2 = I_{7\Omega} = \frac{\begin{vmatrix} 16 & 4 \\ -2 & -9 \end{vmatrix}}{\begin{vmatrix} 16 & -2 \\ -2 & 9 \end{vmatrix}} = \frac{-144 + 8}{144 - 4} = \frac{-136}{140} = -0.971 \text{ A}$$

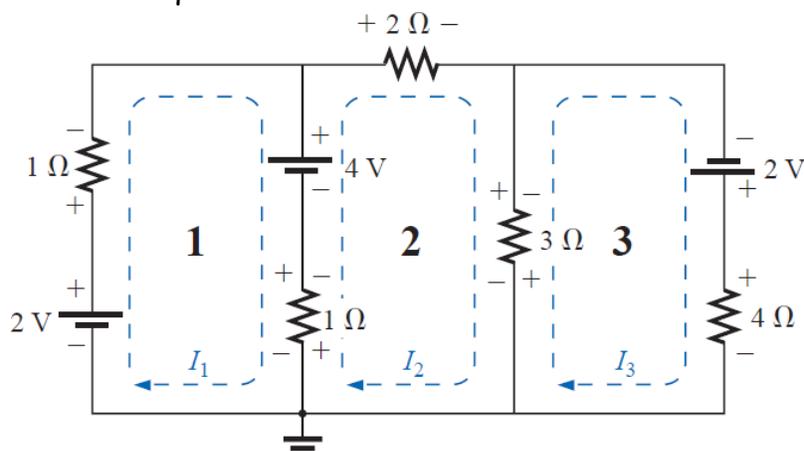
EXAMPLE: Write the mesh equations for the network



Solution:

$$\begin{aligned} 2I_1 - I_2 + 0 &= -2 \\ 6I_2 - I_1 - 3I_3 &= 4 \\ 7I_3 - 3I_2 + 0 &= 2 \end{aligned}$$

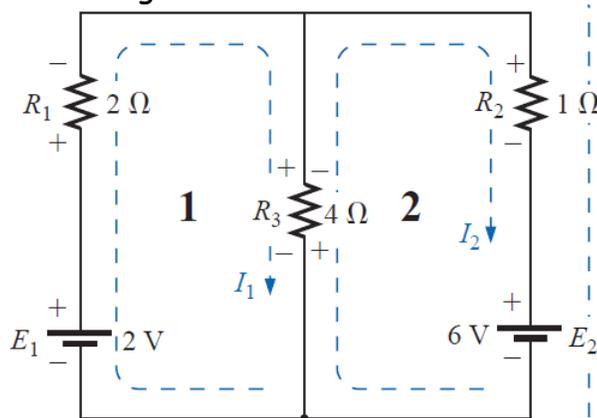EXAMPLE: Find the current through each branch of the network



Solution:

$$6I_1 - 4I_2 = 2 \quad \dots\dots\dots(1)$$

$$5I_2 - 4I_1 = -6 \quad \dots\dots\dots(2)$$

$$6I_1 - 4I_2 = 2$$


$$-4I_1 + 5I_2 = -6$$

$$I_1 = \frac{\begin{vmatrix} 2 & -4 \\ -6 & 5 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ -4 & 5 \end{vmatrix}} = \frac{(2 \times 5) - (-4 \times -6)}{(6 \times 5) - (-4 \times -4)} = \frac{10 - 24}{30 - 16} = \frac{-14}{14} = -1 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} 6 & 2 \\ -4 & 6 \end{vmatrix}}{\begin{vmatrix} 6 & -4 \\ -4 & 5 \end{vmatrix}} = -2 \text{ A}$$

$$\begin{aligned} I_{4\Omega} &= I_1 - I_2 = -1 \text{ A} - (-2 \text{ A}) = -1 \text{ A} + 2 \text{ A} \\ &= 1 \text{ A} \quad (\text{in the direction of } I_1) \end{aligned}$$

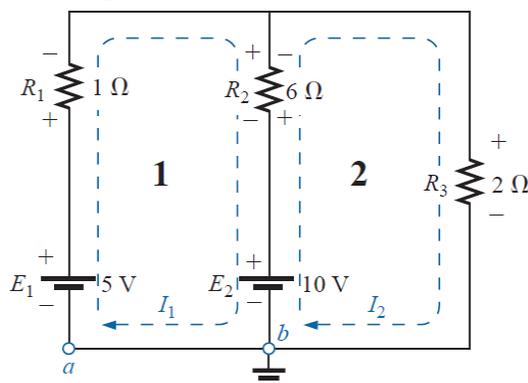EXAMPLE: Find the current through each branch of the network



Solution:

$$7I_1 - 6I_2 = 5 - 10 \dots\dots\dots(1)$$

$$8I_2 - 6I_1 = 10 \dots\dots\dots(2)$$

$$- 7I_1 + 6I_2 = 5$$


$$+ 6I_1 - 8I_2 = -10$$

$$I_1 = \frac{\begin{vmatrix} 5 & 6 \\ -10 & -8 \end{vmatrix}}{\begin{vmatrix} -7 & 6 \\ 6 & -8 \end{vmatrix}} = \frac{-40 + 60}{56 - 36} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} -7 & 5 \\ 6 & -10 \end{vmatrix}}{20} = \frac{70 - 30}{20} = \frac{40}{20} = 2 \text{ A}$$

$$I_{R_2} = I_2 - I_1 = 2 \text{ A} - 1 \text{ A} = 1 \text{ A} \text{ in the direction of } I_2$$

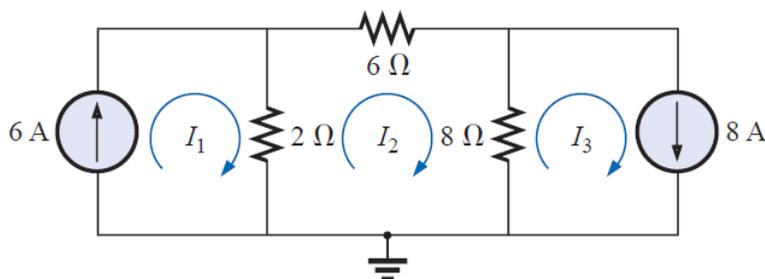EXAMPLE: Using mesh analysis, determine the currents of the network



Solution:

$$I_1 = 6 \text{ A}$$

$$I_3 = 8 \text{ A}$$

$$2I_1 - 16I_2 + 8I_3 = 0$$


$$2(6 \text{ A}) - 16I_2 + 8(8 \text{ A}) = 0$$

$$I_2 = \frac{76 \text{ A}}{16} = 4.75 \text{ A}$$

$$I_{2\Omega} \downarrow = I_1 - I_2 = 6 \text{ A} - 4.75 \text{ A} = 1.25 \text{ A}$$

$$I_{8\Omega} \uparrow = I_3 - I_2 = 8 \text{ A} - 4.75 \text{ A} = 3.25 \text{ A}$$

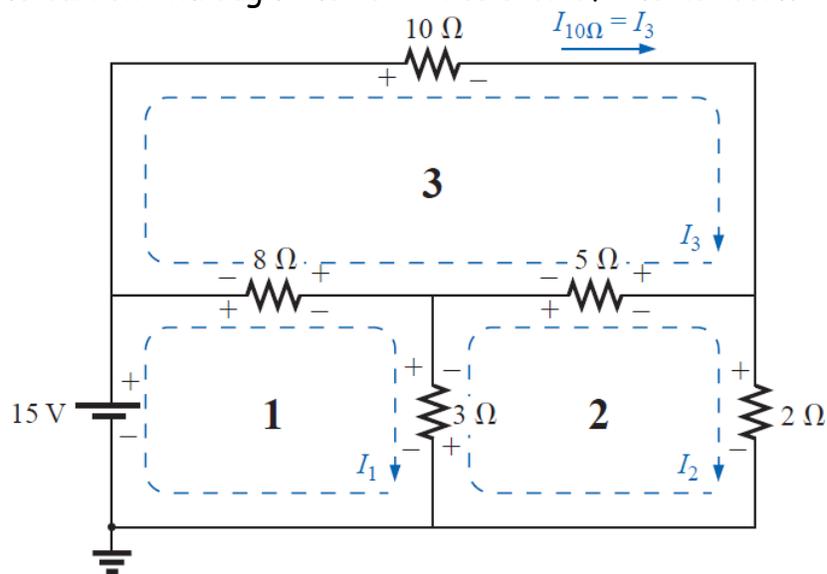EXAMPLE: Find the current through the 10- Ω resistor of the network



Solution:

$$I_1: \quad (8 \Omega + 3 \Omega)I_1 - (8 \Omega)I_3 - (3 \Omega)I_2 = 15 \text{ V}$$

$$I_2: \quad (3 \Omega + 5 \Omega + 2 \Omega)I_2 - (3 \Omega)I_1 - (5 \Omega)I_3 = 0$$

$$I_3: \quad (8 \Omega + 10 \Omega + 5 \Omega)I_3 - (8 \Omega)I_1 - (5 \Omega)I_2 = 0$$



$$11I_1 - 8I_3 - 3I_2 = 15$$

$$10I_2 - 3I_1 - 5I_3 = 0$$

$$23I_3 - 8I_1 - 5I_2 = 0$$

$$11I_1 - 3I_2 - 8I_3 = 15$$

$$-3I_1 + 10I_2 - 5I_3 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0$$

$$I_3 = I_{10\Omega} = \frac{\begin{vmatrix} 11 & -3 & 15 \\ -3 & 10 & 0 \\ -8 & -5 & 0 \end{vmatrix}}{\begin{vmatrix} 11 & -3 & -8 \\ -3 & 10 & -5 \\ -8 & -5 & 23 \end{vmatrix}} = 1.220 \text{ A}$$



الوحدة الثانية عشر الزمن: 90 دقيقة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Nodal Analysis


موضوعات المحاضرة
الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	12


Nodal Analysis

- Choose a reference node and assign a subscripted voltage label to the $(N - 1)$ remaining nodes of the network.
- Write the equations of node so that the column to the right of the equality sign is the algebraic sum of the current sources tied to the node of interest. A current source is assigned a positive sign if it supplies current to a node and a negative sign if it draws current from the node.
- Solve the resulting equations for the desired voltages.

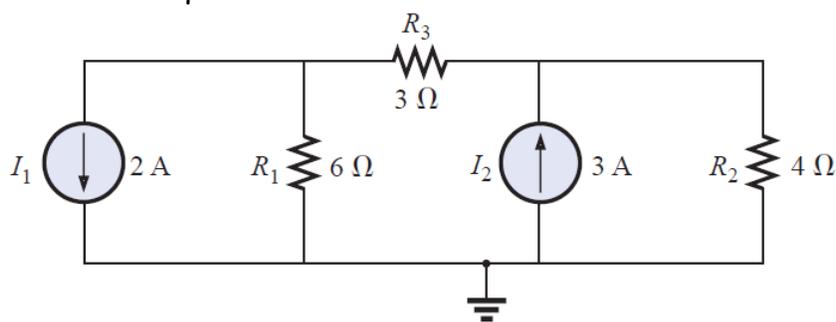EXAMPLE: Write the nodal equations for the network.



Solution:

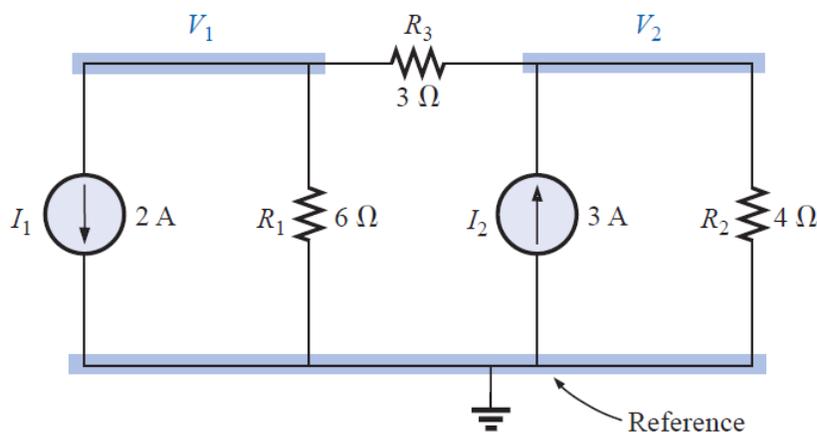

Drawing current
from node 1

$$V_1: \left(\frac{1}{6\Omega} + \frac{1}{3\Omega} \right) V_1 - \left(\frac{1}{3\Omega} \right) V_2 = -2 \text{ A}$$

Sum of conductances connected to node 1 Mutual conductance

Supplying current
to node 2


$$V_2: \left(\frac{1}{4\Omega} + \frac{1}{3\Omega} \right) V_2 - \left(\frac{1}{3\Omega} \right) V_1 = +3 \text{ A}$$

Sum of conductances connected to node 2 Mutual conductance


$$\frac{1}{2} V_1 - \frac{1}{3} V_2 = -2$$

$$-\frac{1}{3} V_1 + \frac{7}{12} V_2 = 3$$

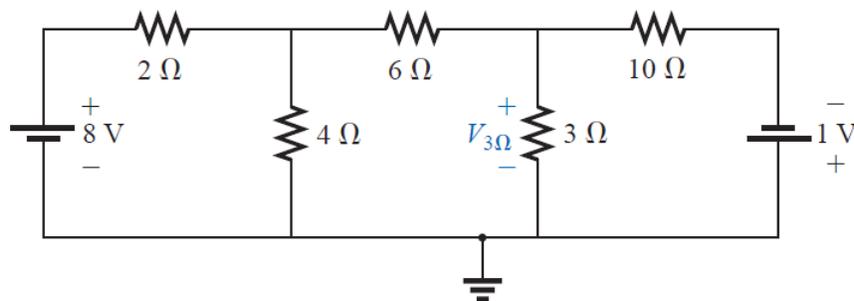EXAMPLE: Find the voltage across the 3-Ω resistor by nodal analysis.



Solution:

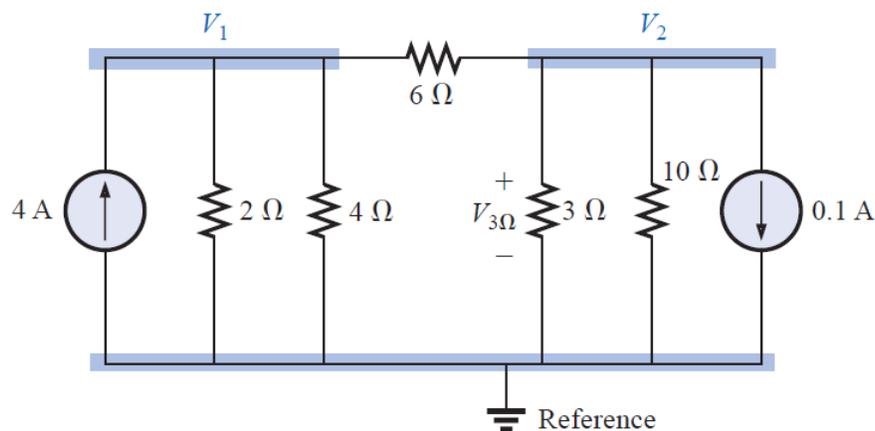

$$\left(\frac{1}{2\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{6\ \Omega}\right)V_1 - \left(\frac{1}{6\ \Omega}\right)V_2 = +4\ \text{A}$$

$$\left(\frac{1}{10\ \Omega} + \frac{1}{3\ \Omega} + \frac{1}{6\ \Omega}\right)V_2 - \left(\frac{1}{6\ \Omega}\right)V_1 = -0.1\ \text{A}$$

$$\frac{11}{12}V_1 - \frac{1}{6}V_2 = 4$$


$$-\frac{1}{6}V_1 + \frac{3}{5}V_2 = -0.1$$

$$11V_1 - 2V_2 = +48$$


$$-5V_1 + 18V_2 = -3$$

$$V_2 = V_{3\Omega} = \frac{\begin{vmatrix} 11 & 48 \\ -5 & -3 \end{vmatrix}}{\begin{vmatrix} 11 & -2 \\ -5 & 18 \end{vmatrix}} = \frac{-33 + 240}{198 - 10} = \frac{207}{188} = \mathbf{1.101\ \text{V}}$$

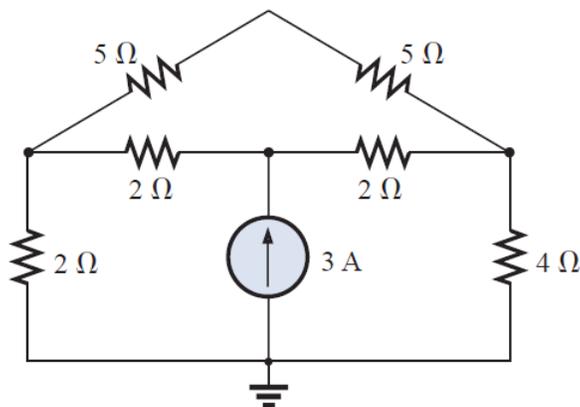EXAMPLE: Using nodal analysis, determine the potential across the 4- Ω resistor and it's current.



Solution:

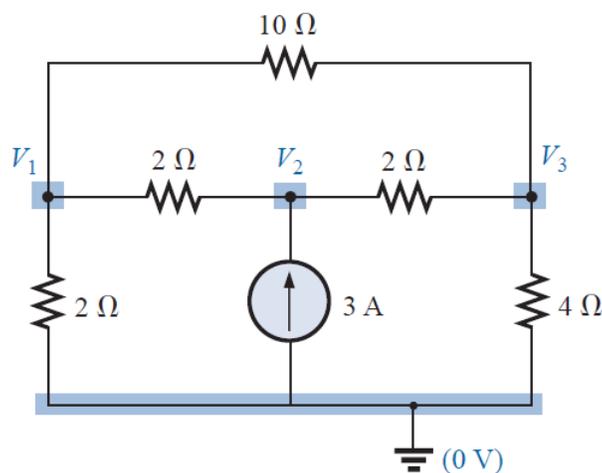

$$V_1: \left(\frac{1}{2\Omega} + \frac{1}{2\Omega} + \frac{1}{10\Omega} \right) V_1 - \left(\frac{1}{2\Omega} \right) V_2 - \left(\frac{1}{10\Omega} \right) V_3 = 0$$

$$V_2: \left(\frac{1}{2\Omega} + \frac{1}{2\Omega} \right) V_2 - \left(\frac{1}{2\Omega} \right) V_1 - \left(\frac{1}{2\Omega} \right) V_3 = 3\text{ A}$$

$$V_3: \left(\frac{1}{10\Omega} + \frac{1}{2\Omega} + \frac{1}{4\Omega} \right) V_3 - \left(\frac{1}{2\Omega} \right) V_2 - \left(\frac{1}{10\Omega} \right) V_1 = 0$$

$$1.1V_1 - 0.5V_2 - 0.1V_3 = 0$$

$$V_2 - 0.5V_1 - 0.5V_3 = 3$$

$$0.85V_3 - 0.5V_2 - 0.1V_1 = 0$$

$$V_3 = V_{4\Omega} = \frac{\begin{vmatrix} 1.1 & -0.5 & 0 \\ -0.5 & +1 & 3 \\ -0.1 & -0.5 & 0 \end{vmatrix}}{\begin{vmatrix} 1.1 & -0.5 & -0.1 \\ -0.5 & +1 & -0.5 \\ -0.1 & -0.5 & +0.85 \end{vmatrix}} = 4.645\text{ V}$$

$$I_{4\Omega} = \frac{V_3}{4} = \frac{4.645}{4} = 1.16\text{ A}$$

الوحدة الثالثة عشر - الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Superposition Theorem

The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
● جهاز حاسوب	● نشاط التعارف	13
● جهاز عرض	● محاضرة	
● سبورة	● مناقشة	
● اوراق واقلام	● سؤال وجواب	

Superposition Theorem


The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.

Number of networks to be analyzed	=	Number of independent sources
--------------------------------------	---	----------------------------------

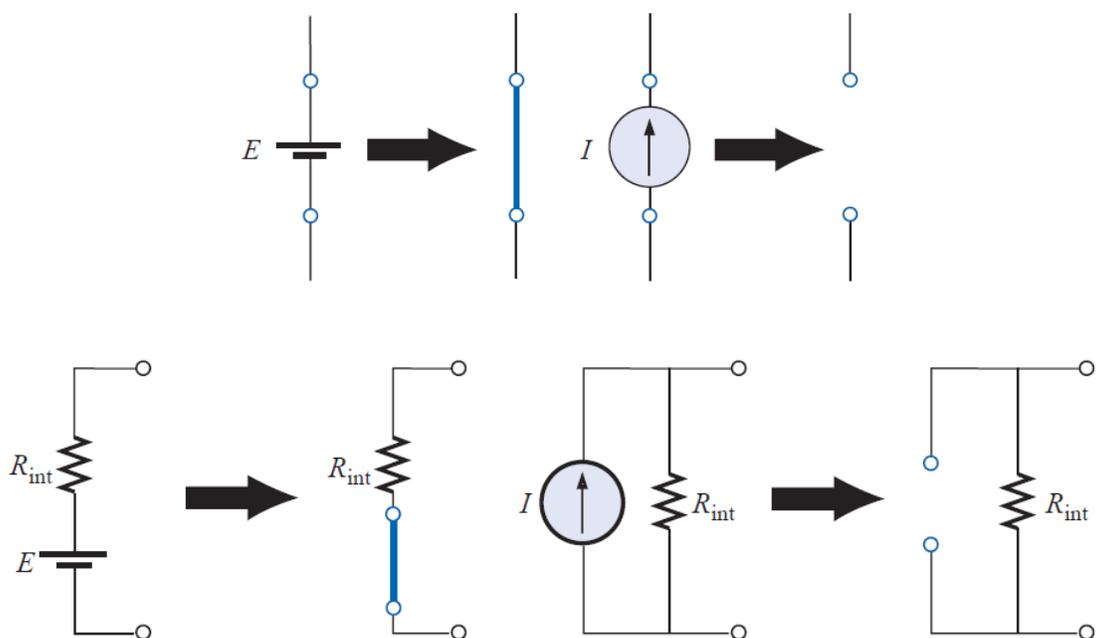


The total power delivered to a resistive element must be determined using the total current through or the total voltage across the element and cannot be determined by a simple sum of the power levels established by each source.

EXAMPLE: Determine I_1 for the network.

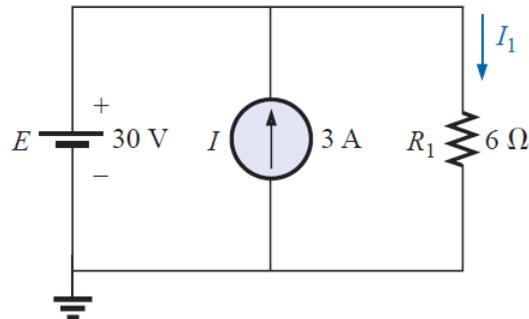


Solution:

1) Setting $E = 0 \text{ V}$

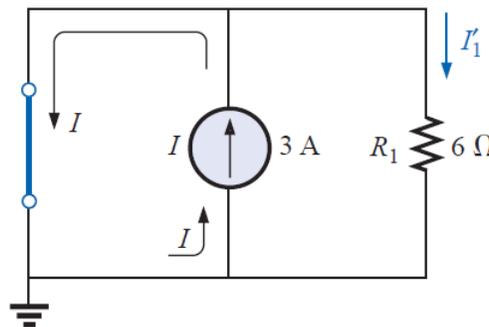

$$I'_1 = \frac{R_{sc} I}{R_{sc} + R_1} = \frac{(0 \Omega) I}{0 \Omega + 6 \Omega} = 0 \text{ A}$$


2) Setting $I = \text{zero}$

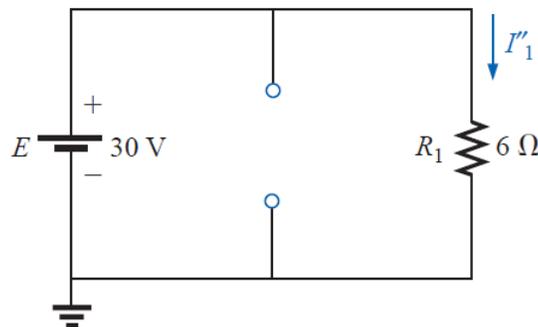

$$I''_1 = \frac{E}{R_1} = \frac{30 \text{ V}}{6 \Omega} = 5 \text{ A}$$


$$I_1 = I'_1 + I''_1 = 0 \text{ A} + 5 \text{ A} = 5 \text{ A}$$

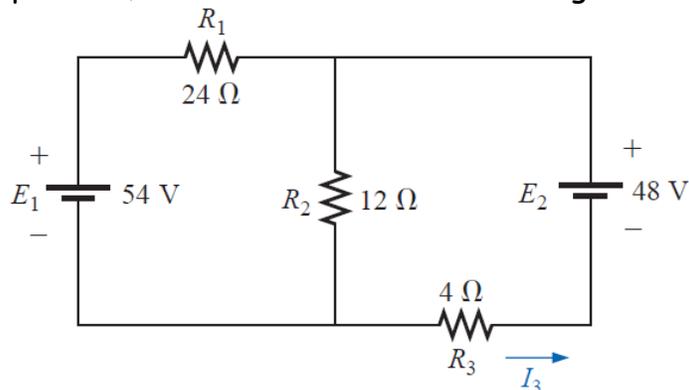EXAMPLE: Using superposition, determine the current through the 4- Ω resistor



Solution:

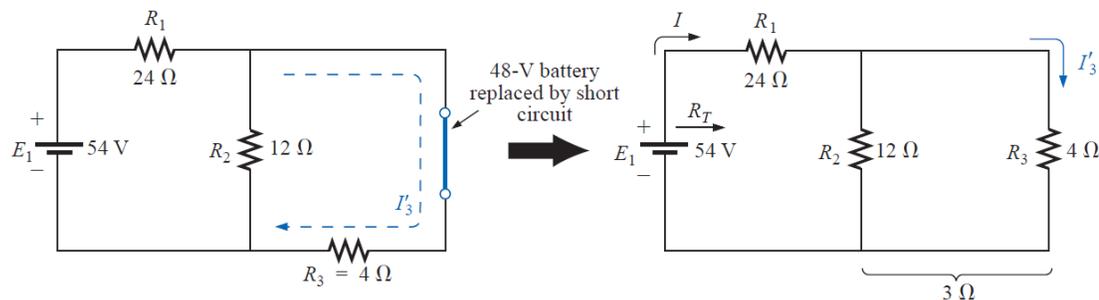1) Considering the effects of a 54-V source




$$R_T = R_1 + R_2 \parallel R_3 = 24 \Omega + 12 \Omega \parallel 4 \Omega = 24 \Omega + 3 \Omega = 27 \Omega$$

$$I = \frac{E_1}{R_T} = \frac{54 \text{ V}}{27 \Omega} = 2 \text{ A}$$

$$I'_3 = \frac{R_2 I}{R_2 + R_3} = \frac{(12 \Omega)(2 \text{ A})}{12 \Omega + 4 \Omega} = \frac{24 \text{ A}}{16} = 1.5 \text{ A}$$

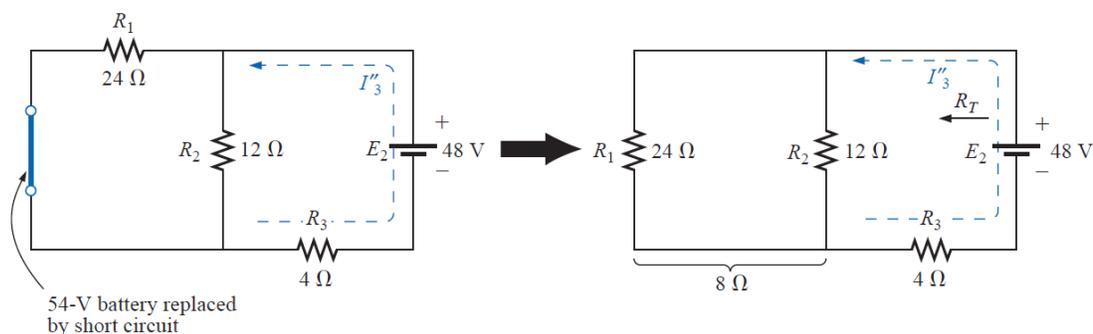
2) Considering the effects of the 48-V source




$$R_T = R_3 + R_1 \parallel R_2 = 4 \Omega + 24 \Omega \parallel 12 \Omega = 4 \Omega + 8 \Omega = 12 \Omega$$

$$I''_3 = \frac{E_2}{R_T} = \frac{48 \text{ V}}{12 \Omega} = 4 \text{ A}$$
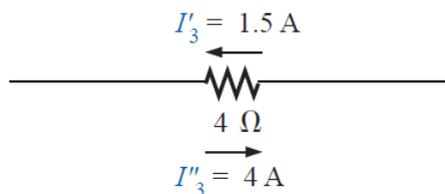
$$I_3 = I''_3 - I'_3 = 4 \text{ A} - 1.5 \text{ A} = 2.5 \text{ A}$$




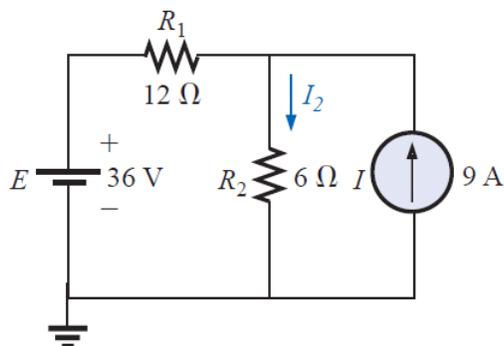EXAMPLE: Using superposition, find the current through the 6-Ω resistor of the network, and find its power.




Solution:

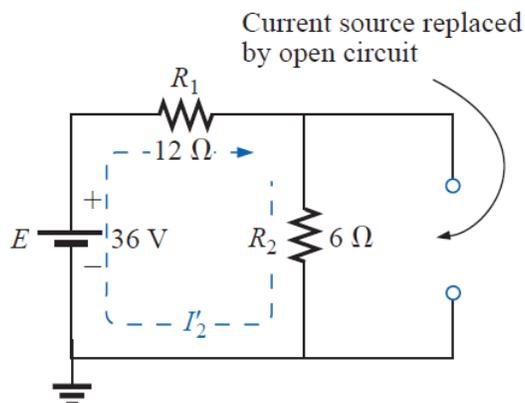1) Considering the effect of the 36-V source




$$I'_2 = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{36 \text{ V}}{12 \Omega + 6 \Omega} = 2 \text{ A}$$

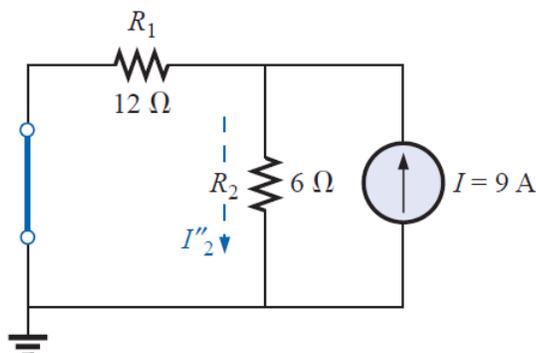2) Considering the effect of the 9-A source




$$I''_2 = \frac{R_1 I}{R_1 + R_2} = \frac{(12 \Omega)(9 \text{ A})}{12 \Omega + 6 \Omega} = \frac{108 \text{ A}}{18} = 6 \text{ A}$$
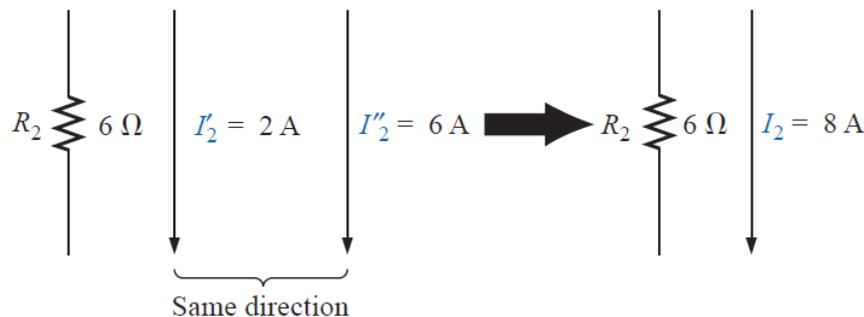
$$I_2 = I'_2 + I''_2 = 2 \text{ A} + 6 \text{ A} = 8 \text{ A}$$




$$\text{Power} = I^2 R = (8 \text{ A})^2 (6 \Omega) = 384 \text{ W}$$

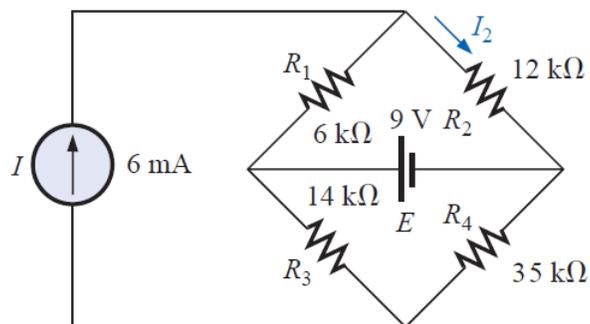EXAMPLE: Using the principle of superposition, find the current I_2 through the 12-k Ω resistor.




Solution:

1) Considering the effect of the 6-mA

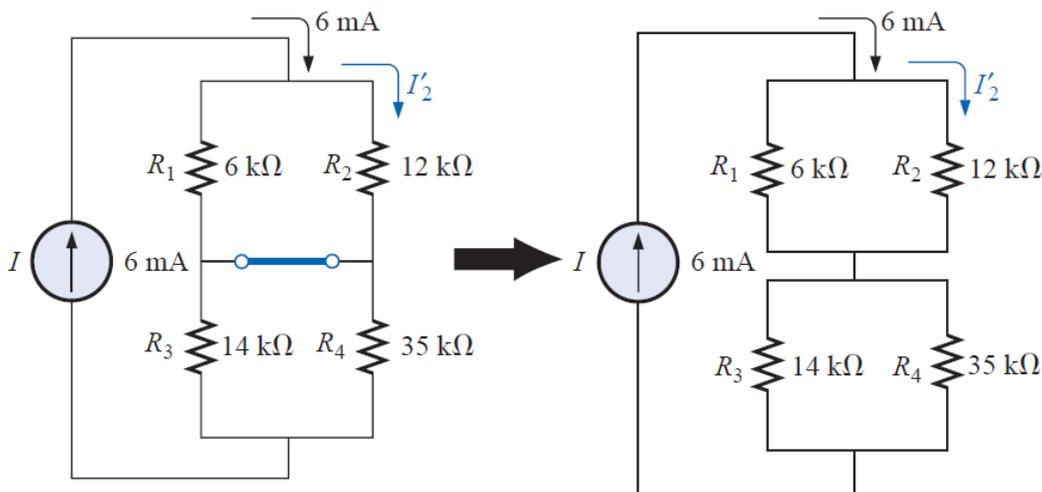

$$I_2' = \frac{R_1 I}{R_1 + R_2} = \frac{(6 \text{ k}\Omega)(6 \text{ mA})}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 2 \text{ mA}$$

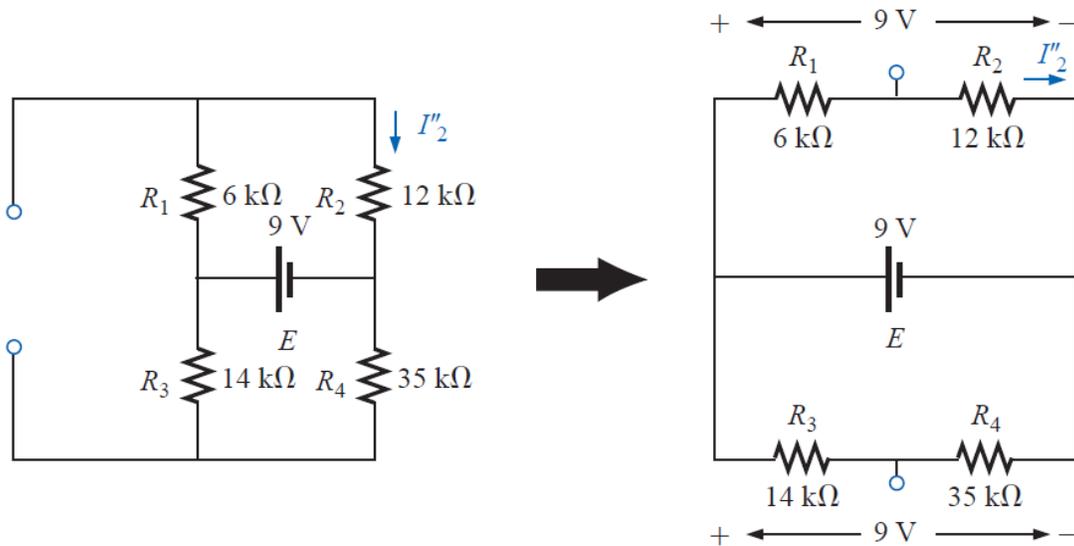2) Considering the effect of the 9-V voltage source



$$I''_2 = \frac{E}{R_1 + R_2} = \frac{9 \text{ V}}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$\begin{aligned} I_2 &= I'_2 + I''_2 \\ &= 2 \text{ mA} + 0.5 \text{ mA} \\ &= \mathbf{2.5 \text{ mA}} \end{aligned}$$



الوحدة الرابعة عشر- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Thevenin's Theorem

Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor,


موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	14

Thevenin's Theorem

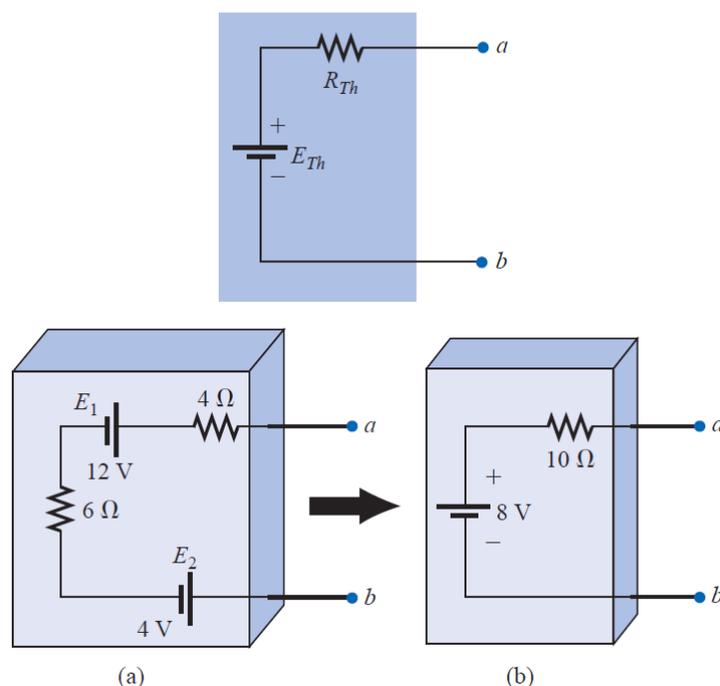Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor,




The following sequence of steps will lead to the proper value of R_{Th} and E_{Th} .

- 1) Remove that portion of the network across which the Thévenin equivalent circuit is to be found.
- 2) Mark the terminals of the remaining two-terminal network.
- 3) Calculate R_{Th} by first setting all sources to zero (voltage sources are replaced by short circuits and current sources by open circuits) and then finding the resultant resistance between the two marked terminals.
- 4) Calculate E_{Th} by first returning all sources to their original position and finding the open-circuit voltage between the marked terminals.
- 5) Draw the Thévenin equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.



So the load current will be equal to

$$I_L = \frac{E_{th}}{R_{th} + R_L}$$

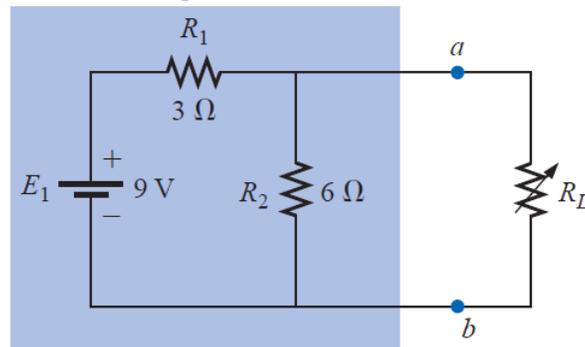
EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the network. Then find the current through R_L for values of $2\ \Omega$, $10\ \Omega$, and $100\ \Omega$.




Solution:

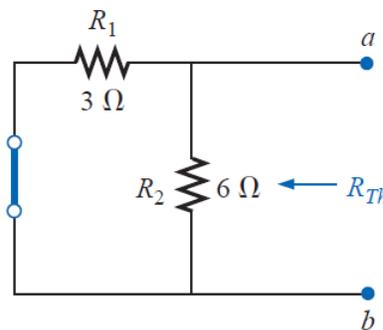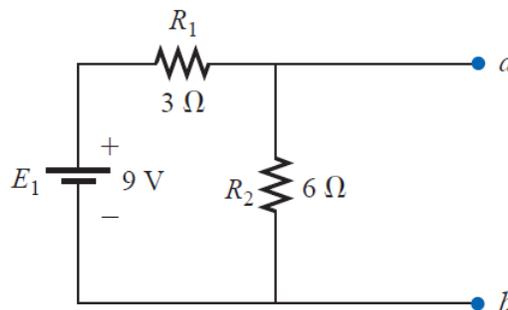
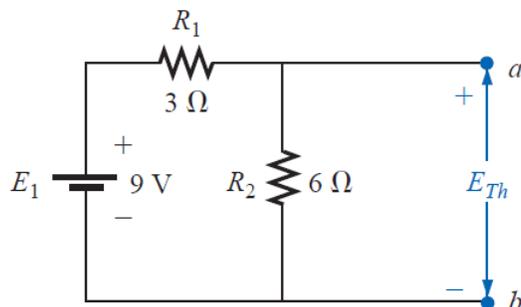
$$R_{Th} = R_1 \parallel R_2 = \frac{(3\ \Omega)(6\ \Omega)}{3\ \Omega + 6\ \Omega} = 2\ \Omega$$


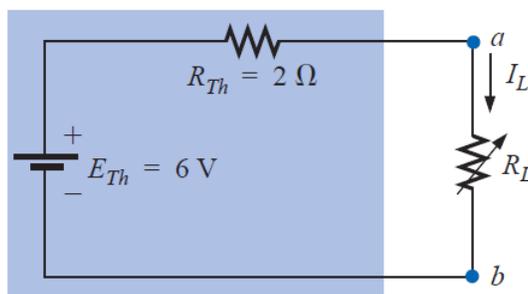
$$E_{Th} = \frac{R_2 E_1}{R_2 + R_1} = \frac{(6 \Omega)(9 \text{ V})}{6 \Omega + 3 \Omega} = \frac{54 \text{ V}}{9} = 6 \text{ V}$$




$$I_L = \frac{E_{Th}}{R_{Th} + R_L}$$

$$R_L = 2 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 2 \Omega} = 1.5 \text{ A}$$



$$R_L = 10 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 10 \Omega} = 0.5 \text{ A}$$

$$R_L = 100 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 100 \Omega} = 0.059 \text{ A}$$

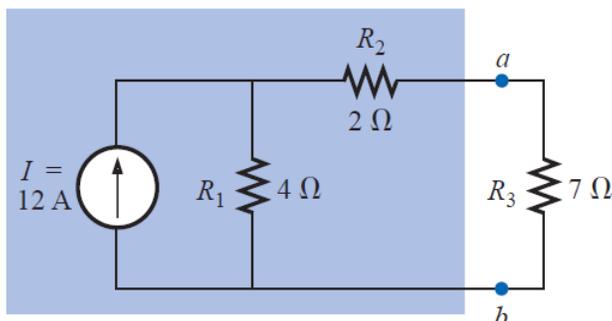
EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the network



Solution:

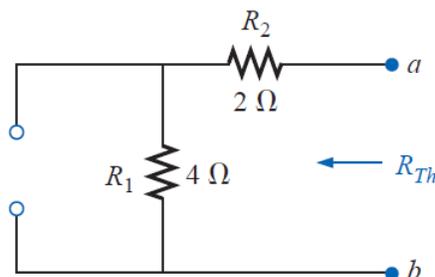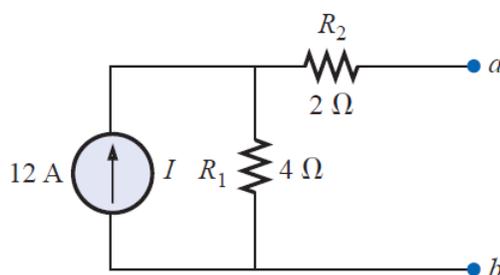

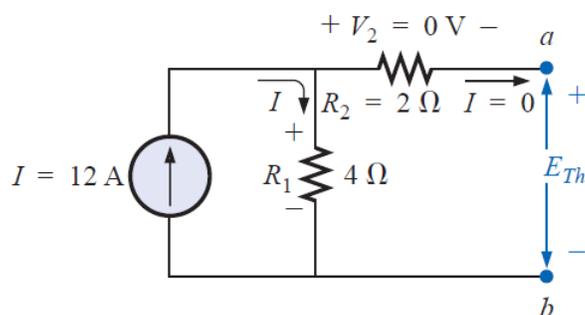
$$R_{Th} = R_1 + R_2 = 4 \Omega + 2 \Omega = 6 \Omega$$




$$V_2 = I_2 R_2 = (0) R_2 = 0 \text{ V}$$


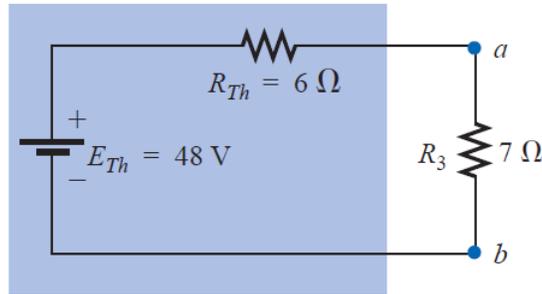
$$E_{Th} = V_1 = I_1 R_1 = I R_1 = (12 \text{ A})(4 \Omega) = 48 \text{ V}$$




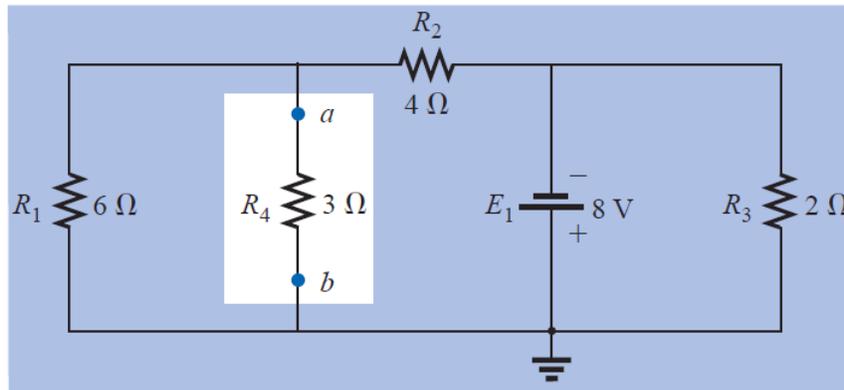
EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the network




Solution:

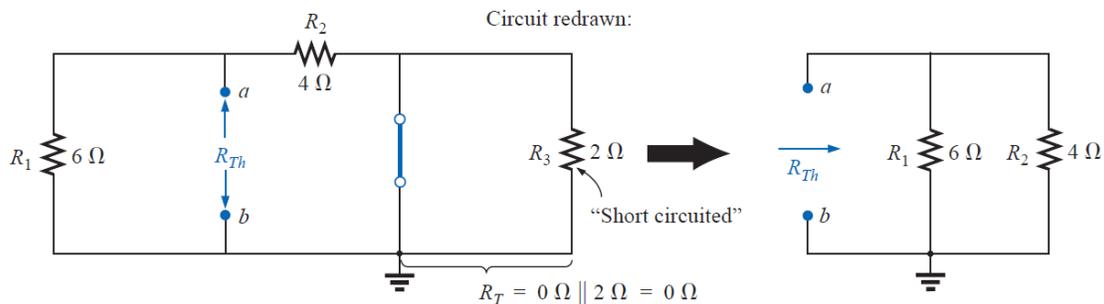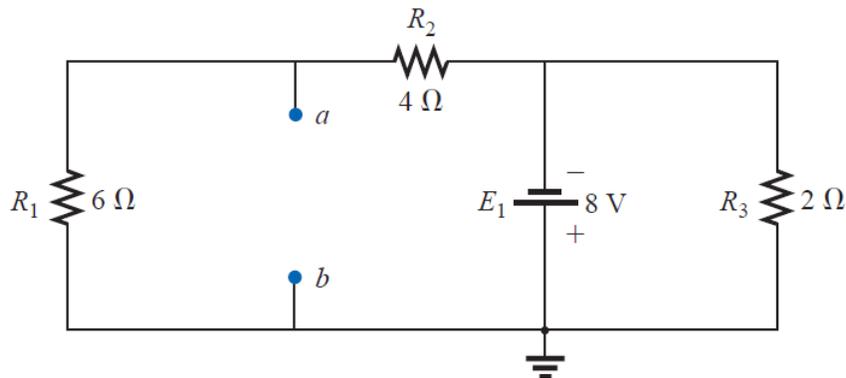

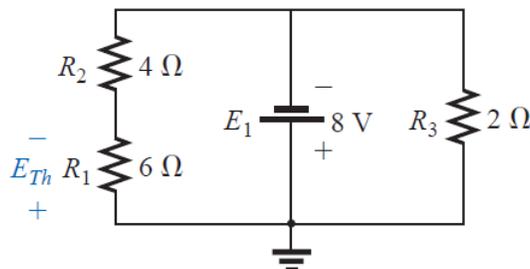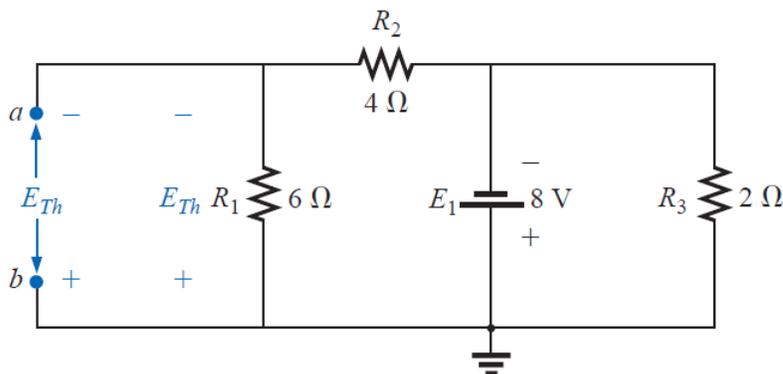
$$R_{Th} = R_1 \parallel R_2 = \frac{(6 \Omega)(4 \Omega)}{6 \Omega + 4 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$



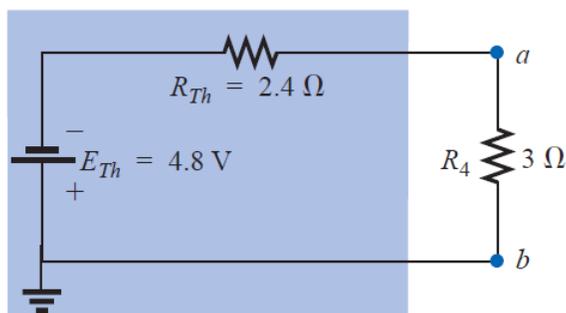
$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$



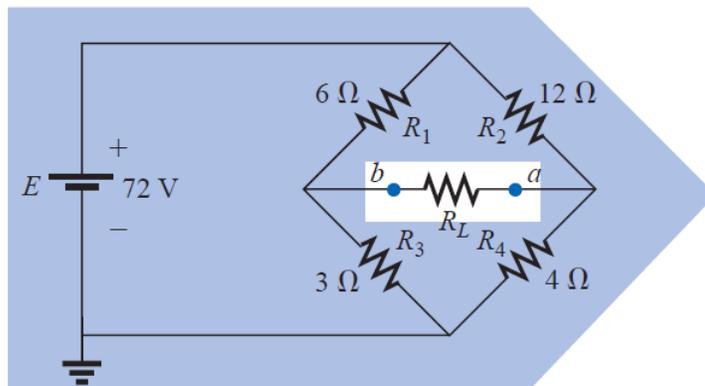
EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the bridge network



Solution:

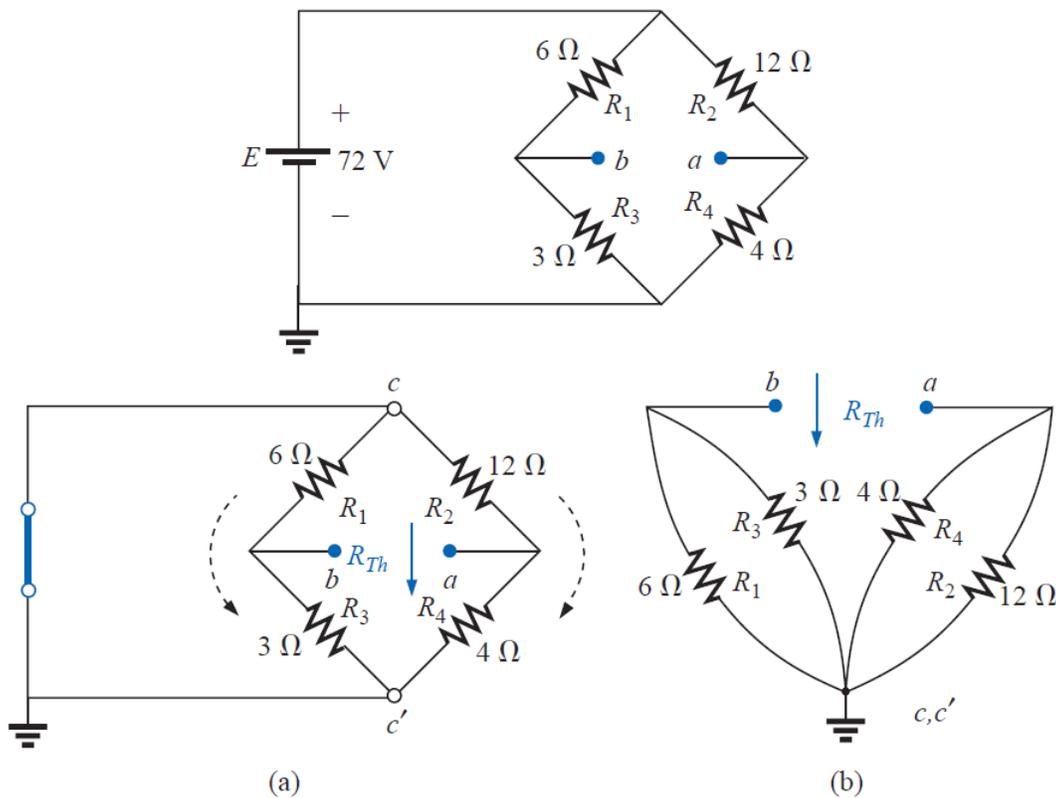
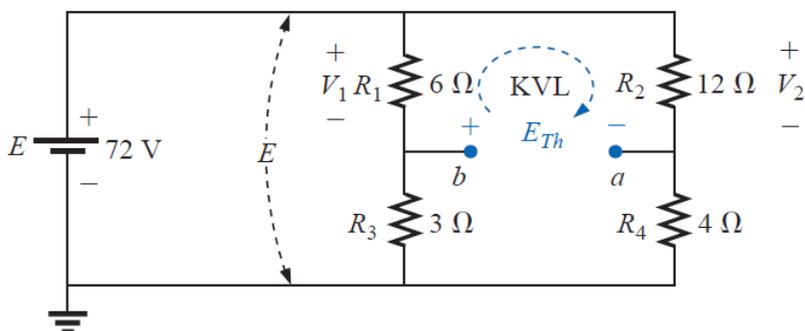
$$\begin{aligned} R_{Th} = R_{a-b} &= R_1 \parallel R_3 + R_2 \parallel R_4 \\ &= 6 \Omega \parallel 3 \Omega + 4 \Omega \parallel 12 \Omega \\ &= 2 \Omega + 3 \Omega = 5 \Omega \end{aligned}$$




$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{(6 \Omega)(72 \text{ V})}{6 \Omega + 3 \Omega} = \frac{432 \text{ V}}{9} = 48 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{(12 \Omega)(72 \text{ V})}{12 \Omega + 4 \Omega} = \frac{864 \text{ V}}{16} = 54 \text{ V}$$

$$\sum_{\odot} V = +E_{Th} + V_1 - V_2 = 0$$
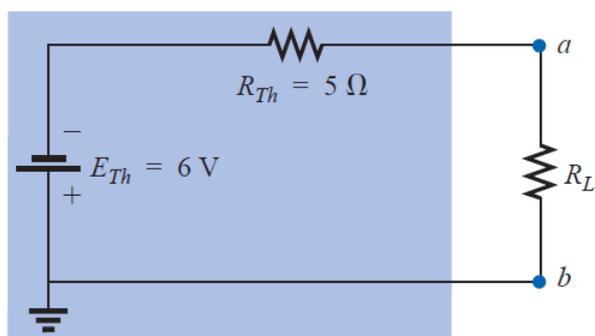
$$E_{Th} = V_2 - V_1 = 54 \text{ V} - 48 \text{ V} = 6 \text{ V}$$





الوحدة الخامسة عشر - الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Norton's Theorem

Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor


موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	15

Norton's Theorem

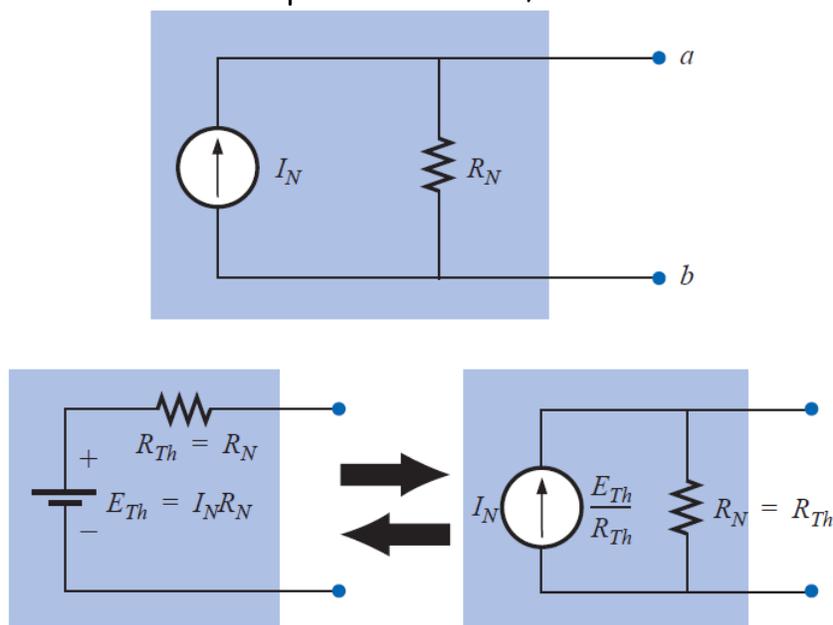Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor,




The steps leading to the proper values of I_N and R_N are now listed.

- 1) Remove that portion of the network across which the Norton equivalent circuit is found.
- 2) Mark the terminals of the remaining two-terminal network.
- 3) Calculate R_N by first setting all sources to zero (voltage sources are replaced with short circuits and current sources with open circuits) and then finding the resultant resistance between the two marked terminals.
- 4) Calculate I_N by first returning all sources to their original position and then finding the short-circuit current between the marked terminals.
- 5) Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.



Then

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

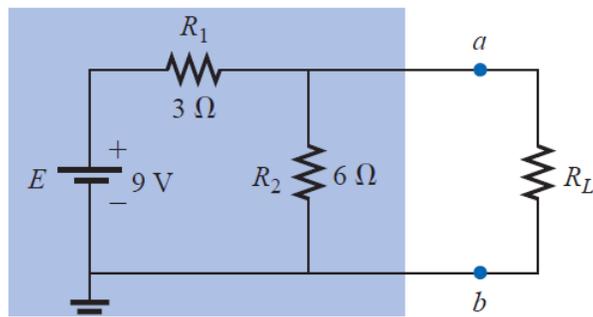
EXAMPLE: Find the Norton equivalent circuit for the network.



Solution:

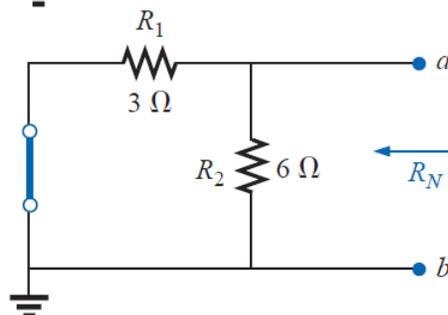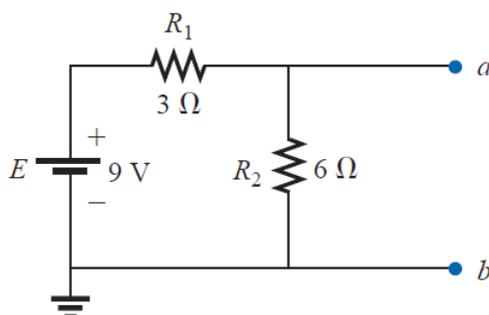

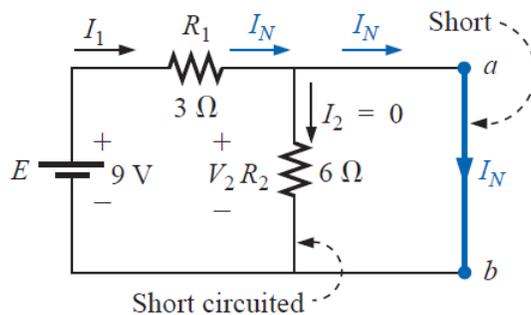
$$R_N = R_1 \parallel R_2 = 3 \Omega \parallel 6 \Omega = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 6 \Omega} = \frac{18 \Omega}{9} = 2 \Omega$$




$$V_2 = I_2 R_2 = (0)6 \Omega = 0 \text{ V}$$

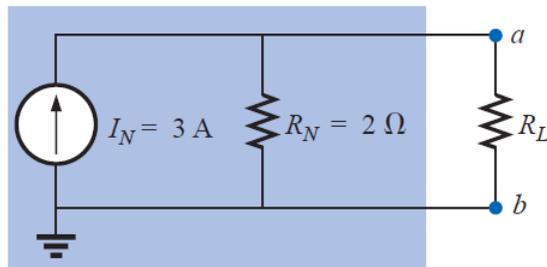
$$I_N = \frac{E}{R_1} = \frac{9 \text{ V}}{3 \Omega} = 3 \text{ A}$$




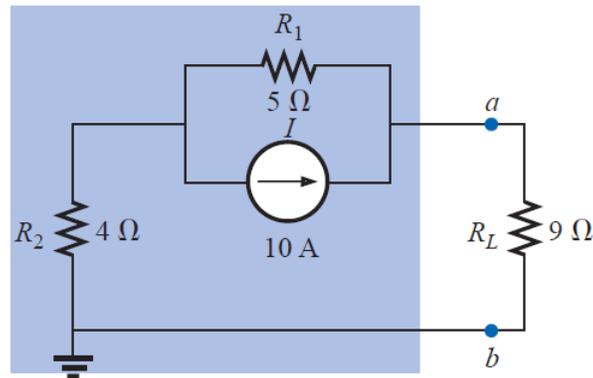EXAMPLE: Find the Norton equivalent circuit for the network external to the 9-Ω resistor.




Solution:

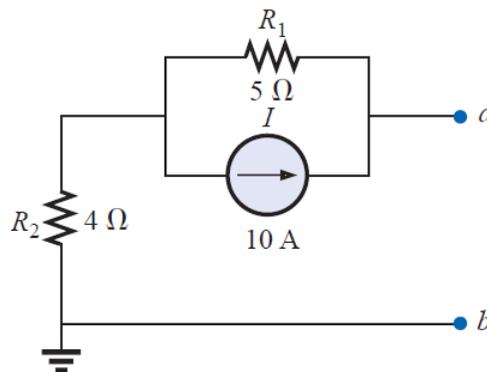


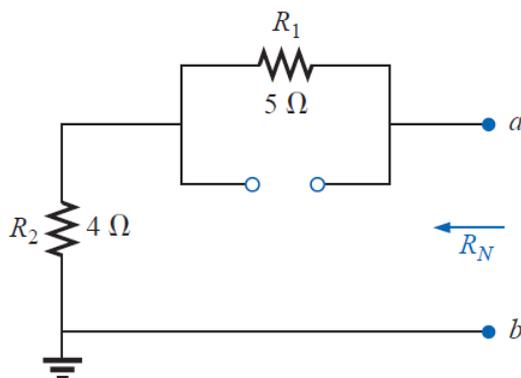

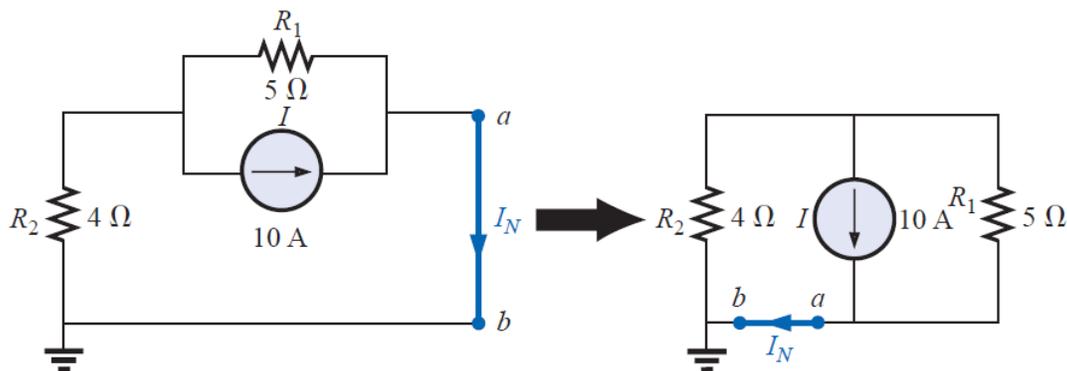
$$R_N = R_1 + R_2 = 5 \Omega + 4 \Omega = 9 \Omega$$



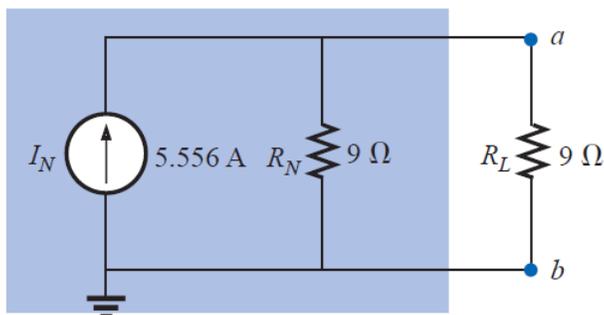
$$I_N = \frac{R_1 I}{R_1 + R_2} = \frac{(5 \Omega)(10 \text{ A})}{5 \Omega + 4 \Omega} = \frac{50 \text{ A}}{9} = 5.556 \text{ A}$$



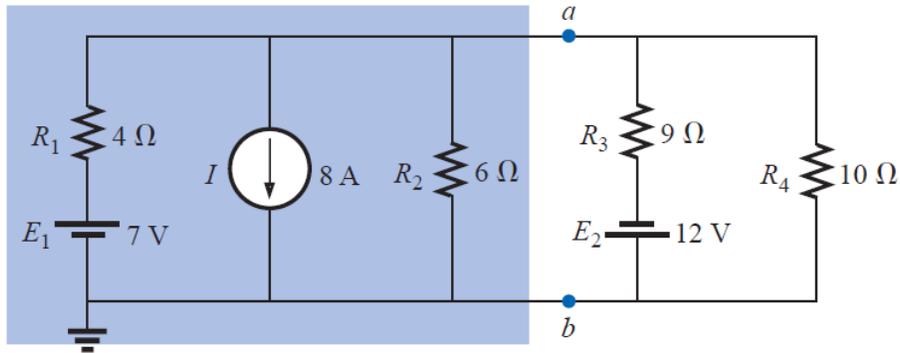EXAMPLE: Find the Norton equivalent circuit for the portion of the network to the left of $a-b$.




Solution:

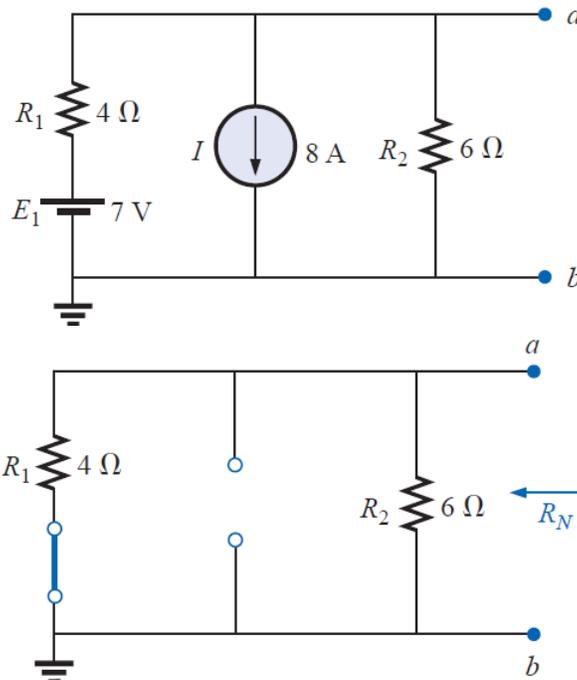


$$R_N = R_1 \parallel R_2 = 4 \Omega \parallel 6 \Omega = \frac{(4 \Omega)(6 \Omega)}{4 \Omega + 6 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$

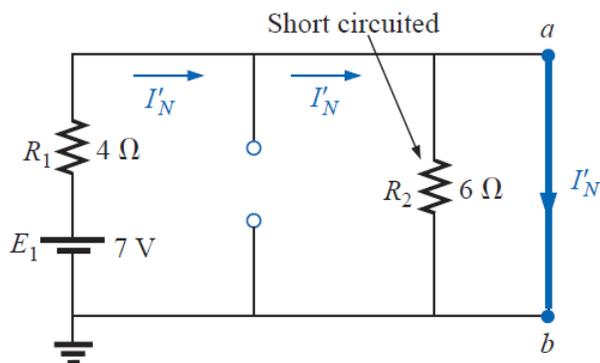1) (Using superposition) for the 7-V battery




$$I'_N = \frac{E_1}{R_1} = \frac{7\text{ V}}{4\ \Omega} = 1.75\text{ A}$$

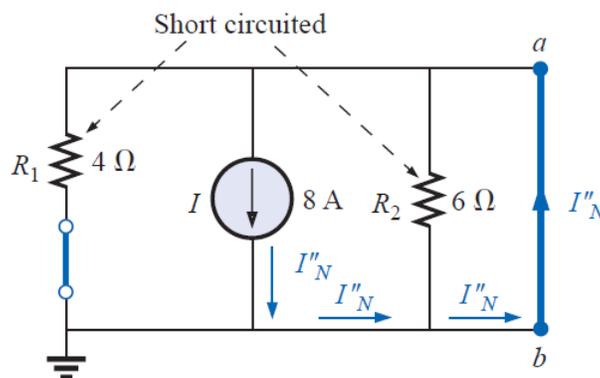2) (Using superposition) for the 8-A source



$$I''_N = I = 8\text{ A}$$
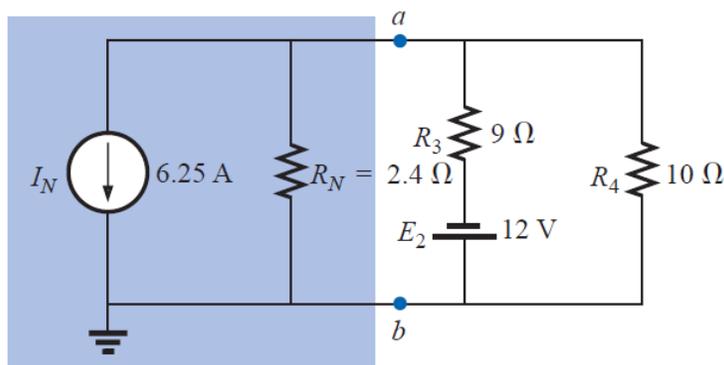
$$I_N = I''_N - I'_N = 8\text{ A} - 1.75\text{ A} = 6.25\text{ A}$$



الوحدة السادسة عشر- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Maximum Power Transfer Theorem

A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thévenin resistance of the network as "seen" by the load

موضوعات المحاضرة


Examples

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	16

Maximum Power Transfer Theorem

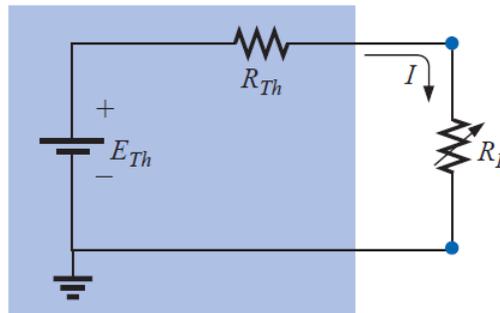A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thévenin resistance of the network as "seen" by the load.



$$R_L = R_{Th}$$

$$I = \frac{E_{Th}}{R_{Th} + R_L} = \frac{E_{Th}}{2R_{Th}}$$


$$P_L = I^2 R_L = \left(\frac{E_{Th}}{2R_{Th}} \right)^2 R_{Th} = \frac{E_{Th}^2 R_{Th}}{4R_{Th}^2}$$

$$P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}}$$

Or

$$P_{L_{max}} = \frac{I_N^2 R_N}{4}$$

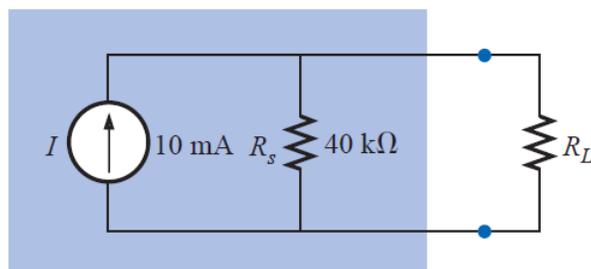EXAMPLE: Determine the R_L necessary to transfer maximum power to R_L , and calculate the power of R_L under these conditions.




Solution:


$$R_L = R_s = 40 \text{ k}\Omega$$

$$P_{L_{\max}} = \frac{I_N^2 R_N}{4} = \frac{(10 \text{ mA})^2 (40 \text{ k}\Omega)}{4} = 1 \text{ W}$$

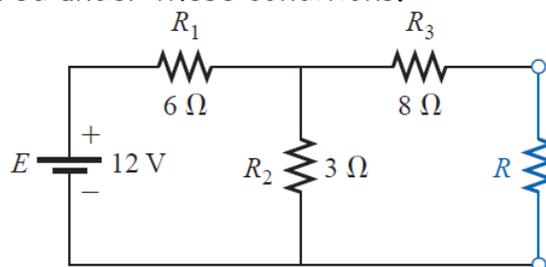EXAMPLE: For the network. Determine the value of R for maximum power to R , and calculate the power delivered under these conditions.




Solution:

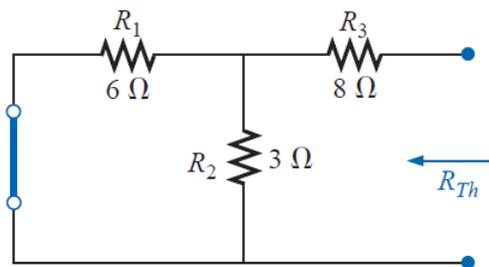

$$R_{Th} = R_3 + R_1 \parallel R_2 = 8 \Omega + \frac{(6 \Omega)(3 \Omega)}{6 \Omega + 3 \Omega} = 8 \Omega + 2 \Omega$$


$$R = R_{Th} = 10 \Omega$$

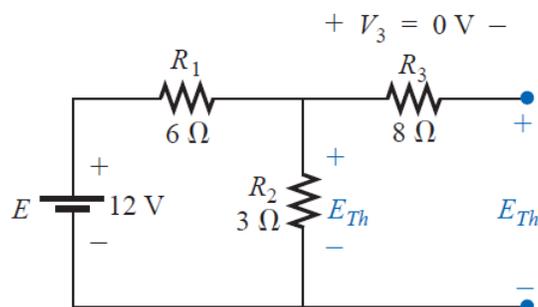


$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{(3 \Omega)(12 \text{ V})}{3 \Omega + 6 \Omega} = \frac{36 \text{ V}}{9} = 4 \text{ V}$$

$$P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(4 \text{ V})^2}{4(10 \Omega)} = 0.4 \text{ W}$$

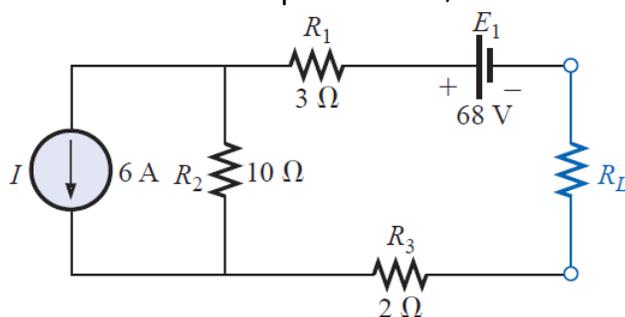EXAMPLE: Find the value of R_L for maximum power to R_L , and determine the maximum power.




Solution:

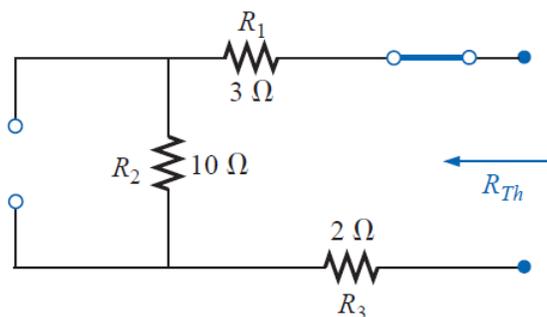

$$R_{Th} = R_1 + R_2 + R_3 = 3 \Omega + 10 \Omega + 2 \Omega = 15 \Omega$$

$$R_L = R_{Th} = 15 \Omega$$

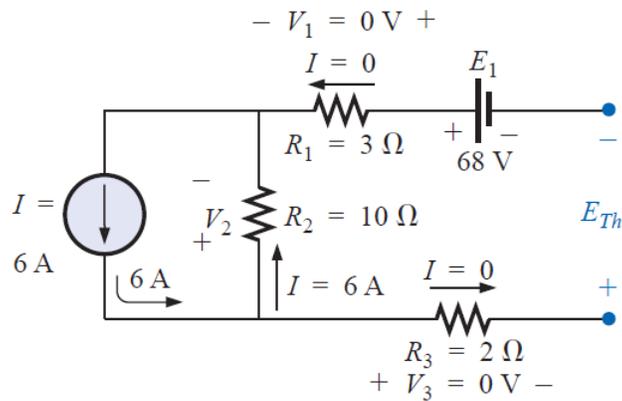

$$V_1 = V_3 = 0 \text{ V}$$

$$V_2 = I_2 R_2 = IR_2 = (6 \text{ A})(10 \Omega) = 60 \text{ V}$$

$$\sum_{\mathcal{C}} V = -V_2 - E_1 + E_{Th} = 0$$

$$E_{Th} = V_2 + E_1 = 60 \text{ V} + 68 \text{ V} = 128 \text{ V}$$

$$P_{L_{\max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{(128 \text{ V})^2}{4(15 \Omega)} = \mathbf{273.07 \text{ W}}$$



الوحدة السابعة عشر - الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Magnetic Circuits

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	17


Magnetic Circuits

Magnetic Fields: is a field of force produced by a magnetic object or particle, or by a changing electric field.

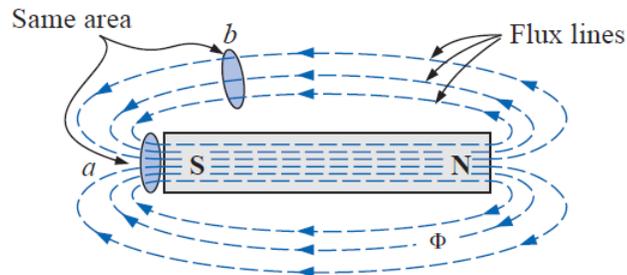
Magnetic Flux Lines: is a measure of the [magnetic field strength](#) existing on a two dimensional surface, the [unit](#) of magnetic flux is the ([weber](#)). The symbol for magnetic flux is (Φ).



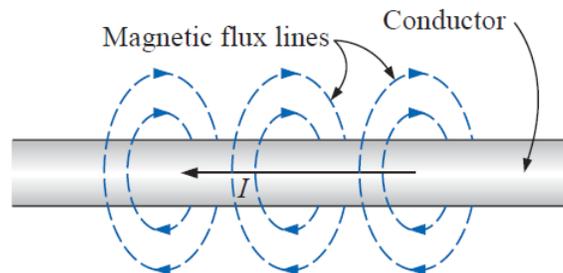
* The magnetic flux lines around a current-carrying conductor (*right-hand rule*).



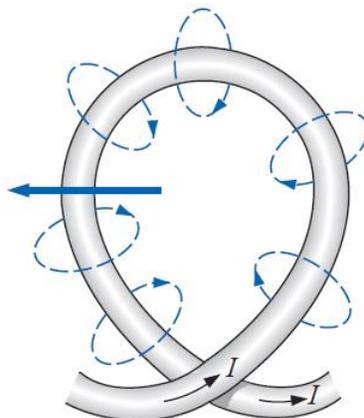
* The Flux distribution of a single-turn coil.



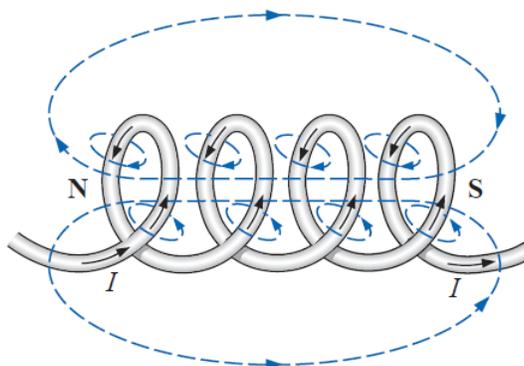* The Flux distribution of a current-carrying coil.



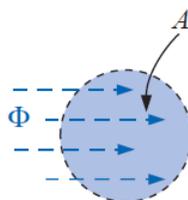Flux Density: The number of flux lines per unit area, is denoted by the capital letter **B**, and is measured in *teslas (T)*.



$$B = \frac{\Phi}{A}$$

Where

B : is flux density in teslas (T)

Φ : is magnetic flux in webers (Wb)

A : is cross-sectional area in square meters (m^2)

EXAMPLE: determine the flux density B in teslas for the figure below.



$$\begin{aligned}\Phi &= 6 \times 10^{-5} \text{ Wb} \\ A &= 1.2 \times 10^{-3} \text{ m}^2\end{aligned}$$

Solution:

$$B = \frac{\Phi}{A} = \frac{6 \times 10^{-5} \text{ Wb}}{1.2 \times 10^{-3} \text{ m}^2} = 5 \times 10^{-2} \text{ T}$$

Permeability: is a measure of the ease with which magnetic flux lines can be established in the material, the symbol for Permeability is (μ), the units of Permeability is Wb/A·m.

* The permeability of free space μ_0 (vacuum) is

$$\mu_0 = 4\pi \times 10^{-7} \frac{\text{Wb}}{\text{A} \cdot \text{m}}$$

* The permeability of material μ is

$$\mu = \mu_0 \mu_r$$

Where μ_r is the relative permeability of material.

Reluctance: It is analogous to [resistance](#) in an [electrical circuit](#), but rather than dissipating magnetic energy it stores magnetic energy. the symbol for Reluctance is (\mathcal{R}), the units of Reluctance is (At/Wb).

$$\mathcal{R} = \frac{l}{\mu A}$$

Where

l : is the length in meters (m).

μ : is Permeability

A : is cross-sectional area in square meters (m^2)


Ohm's Law for Magnetic Circuits: the magnetomotive force (mmf) \mathcal{F} , which is the external force (or "pressure") required to set up the magnetic flux lines within the magnetic material. The opposition to the setting up of the flux Φ is the reluctance \mathcal{R} .

$$\Phi = \frac{\mathcal{F}}{\mathcal{R}}$$

* The magnetomotive force \mathcal{F} is proportional to the product of the number of turns around the core is

$$\mathcal{F} = NI$$

(ampere-turns, At)

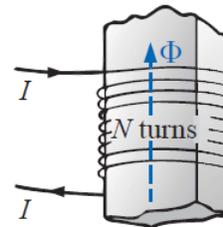


Magnetizing Force: The magnetomotive force per unit length.

$$H = \frac{\mathcal{F}}{l} \quad (\text{At/m})$$

The magnetic force H of the number of turns around the core is

$$H = \frac{NI}{l} \quad (\text{At/m})$$

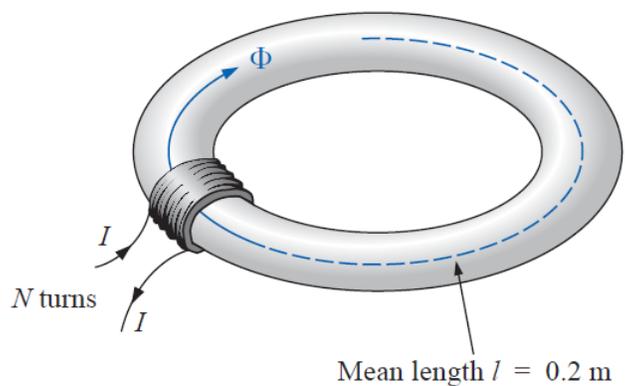EXAMPLE: determine the magnetic force if $NI = 40 \text{ At}$ and $l = 0.2 \text{ m}$.



Solution:



الوحدة الثامنة عشر - الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

موضوعات المحاضرة


Sinusoidal Alternating Waveforms

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	18

Sinusoidal Alternating Waveforms

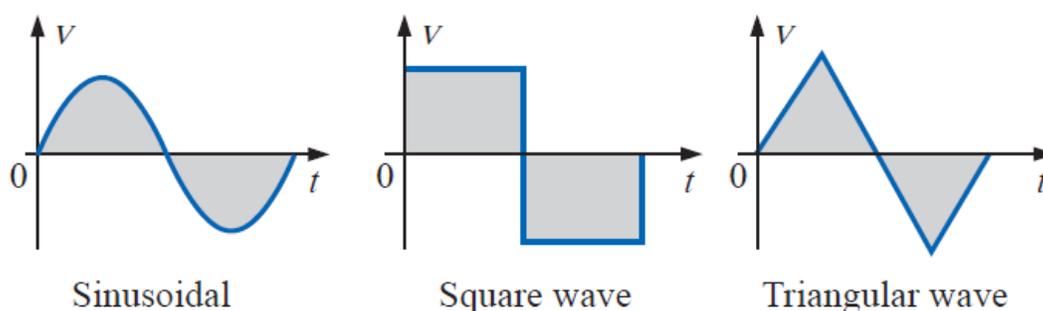
The terminology **(ac)** voltage or **(ac)** current refers to alternating voltage or current. The term alternating indicates only that waveforms alternate between two prescribed levels in a set time sequence. To be absolutely correct the term sinusoidal, square, triangular must be also applied.



The pattern of particular interest is the **sinusoidal ac** waveform voltage.

SINUSOIDAL ac VOLTAGE DEFINITIONS

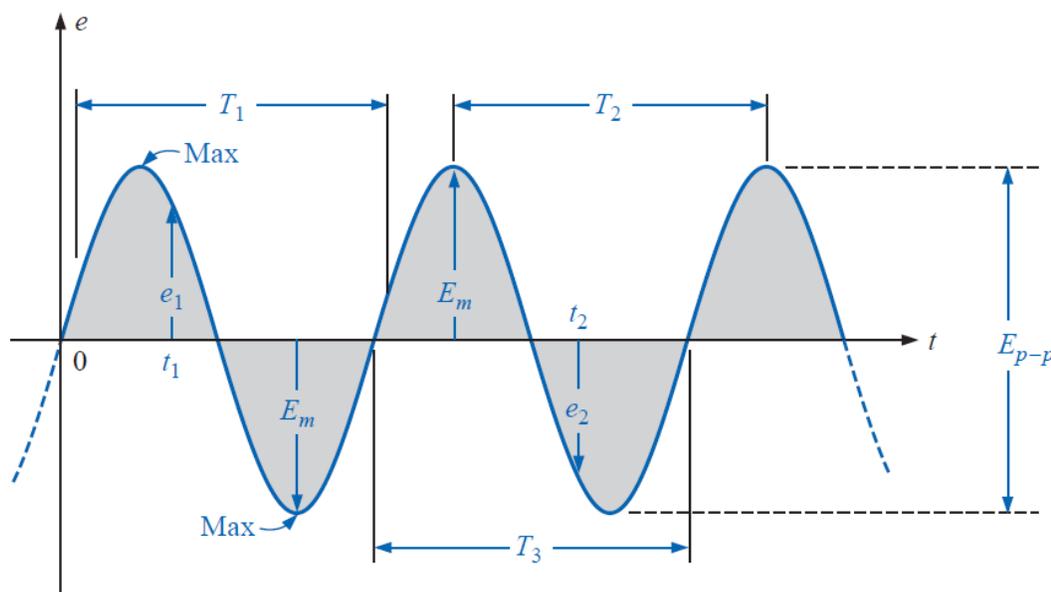The vertical scaling is in volts or amperes and the horizontal scaling is always in units of time.



Waveform: The path traced by a quantity, such as the voltage plotted as a function of some variable such as time (as above), position, degrees, radians, temperature, and so on.

Instantaneous value: The magnitude of a waveform at any instant of time; denoted by lowercase letters (e_1 , e_2).

Peak amplitude: The maximum value of a waveform as measured from its *average*, or *mean*, value, denoted by uppercase letters (such as E_m for sources of voltage and V_m for the voltage drop across a load).


Peak value: The maximum instantaneous value of a function as measured from the zero-volt level.

Peak-to-peak value: Denoted by E_{p-p} or V_{p-p} , the full voltage between positive and negative peaks of the waveform, that is, the sum of the magnitude of the positive and negative peaks.


Periodic waveform: A waveform that continually repeats itself after the same time interval.

Period (T): The time interval between successive repetitions of a periodic waveform (the period $T_1 = T_2 = T_3$),

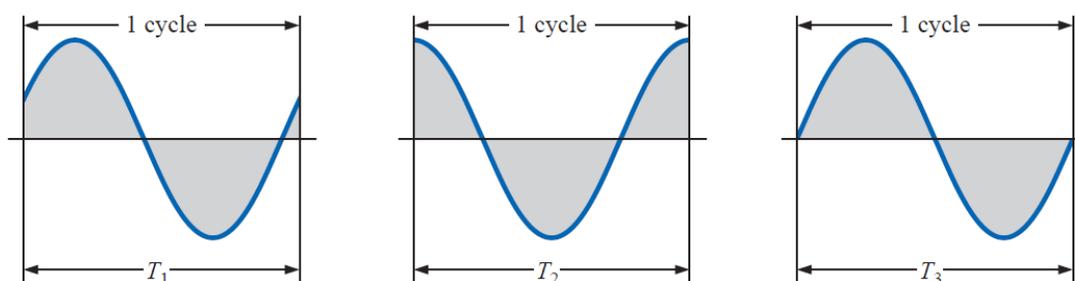Cycle: The portion of a waveform contained in *one period* of time.



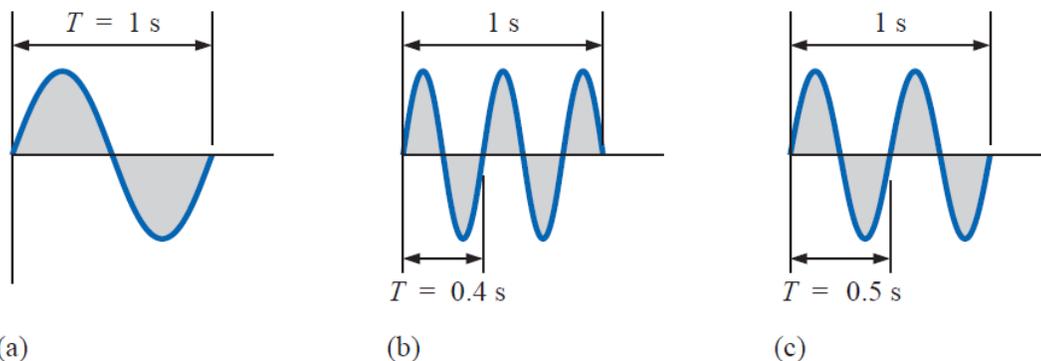Frequency (f): The number of cycles that occur in 1 s.



(a) is 1 cycle per second, and for (b), 2 1/2 cycles per second. If a waveform of similar shape had a period of 0.5 s (c), the frequency would be 2 cycles per second.

$$1 \text{ hertz (Hz)} = 1 \text{ cycle per second (c/s)}$$

$$f = \frac{1}{T}$$

$$f = \text{Hz}$$

$$T = \text{seconds (s)}$$

$$T = \frac{1}{f}$$

EXAMPLE: Find the period of a periodic waveform with a frequency of

- 60 Hz.
- 1000 Hz.


Solutions:

$$\text{a. } T = \frac{1}{f} = \frac{1}{60 \text{ Hz}} \cong 0.01667 \text{ s or } \mathbf{16.67 \text{ ms}}$$

(a recurring value since 60 Hz is so prevalent)

$$\text{b. } T = \frac{1}{f} = \frac{1}{1000 \text{ Hz}} = 10^{-3} \text{ s} = \mathbf{1 \text{ ms}}$$

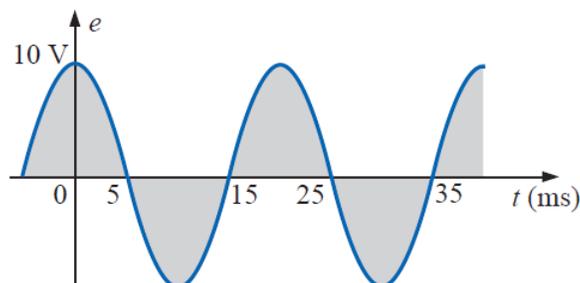EXAMPLE: Determine the frequency of the waveform



Solutions:


From the figure, $T = (25 \text{ ms} - 5 \text{ ms}) = 20 \text{ ms}$, and

$$f = \frac{1}{T} = \frac{1}{20 \times 10^{-3} \text{ s}} = 50 \text{ Hz}$$


THE SINE WAVE

The sinusoidal waveform is the only alternating waveform whose shape is unaffected by the response characteristics of R, L, and C elements.

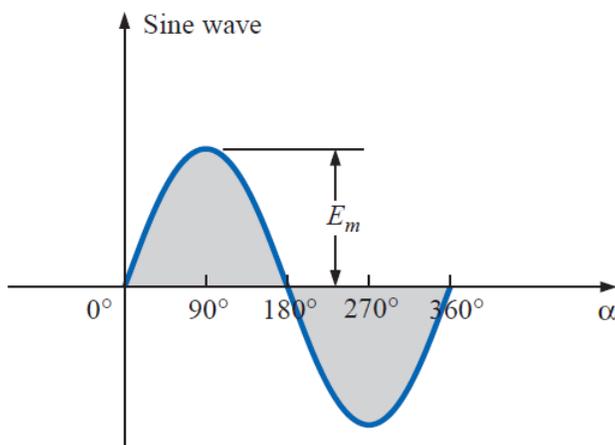In other words, if the voltage across (or current through) a resistor, coil, or capacitor is sinusoidal in nature, the resulting current (or voltage, respectively) for each will also have sinusoidal characteristics.



$2\pi \text{ rad} = 360^\circ$

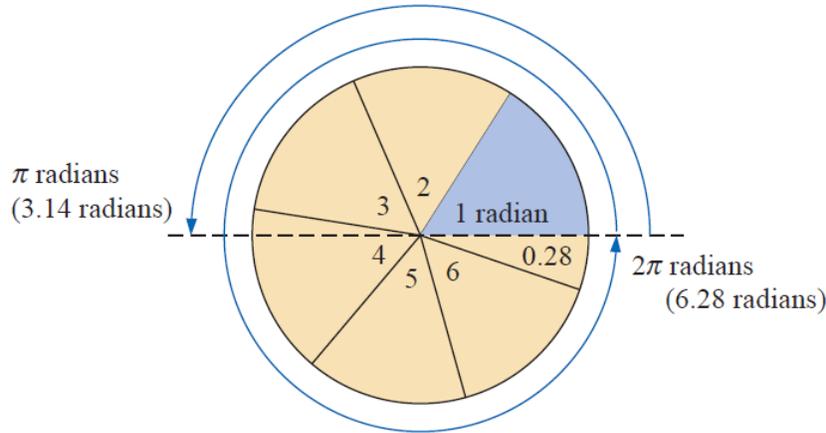

$$\text{Radians} = \left(\frac{\pi}{180^\circ} \right) \times (\text{degrees})$$


$$\text{Degrees} = \left(\frac{180^\circ}{\pi} \right) \times (\text{radians})$$

$$90^\circ: \text{ Radians} = \frac{\pi}{180^\circ}(90^\circ) = \frac{\pi}{2} \text{ rad}$$

$$30^\circ: \text{ Radians} = \frac{\pi}{180^\circ}(30^\circ) = \frac{\pi}{6} \text{ rad}$$

$$\frac{\pi}{3} \text{ rad: Degrees} = \frac{180^\circ}{\pi} \left(\frac{\pi}{3} \right) = 60^\circ$$
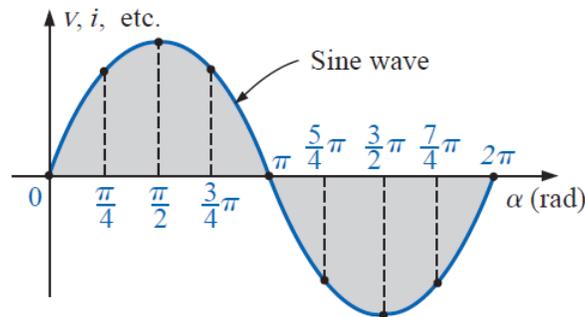
$$\frac{3\pi}{2} \text{ rad: Degrees} = \frac{180^\circ}{\pi} \left(\frac{3\pi}{2} \right) = 270^\circ$$





Angular velocity: The velocity, with which the radius vector rotates about the center, can be determined from the following equation:

$$\text{Angular velocity} = \frac{\text{distance (degrees or radians)}}{\text{time (seconds)}}$$

$$\omega = \frac{2\pi}{T} \quad (\text{rad/s})$$

$$\omega = 2\pi f \quad (\text{rad/s})$$



الوحدة التاسعة عشر - الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

GENERAL FORMAT FOR THE SINUSOIDAL VOLTAGE OR CURRENT

موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	19


GENERAL FORMAT FOR THE SINUSOIDAL VOLTAGE OR CURRENT

The basic mathematical format for the sinusoidal waveform is:

$$A_m \sin \alpha$$

where A_m is the peak value of the waveform and α is the unit of measure for the horizontal axis.

$$\alpha = \omega t$$

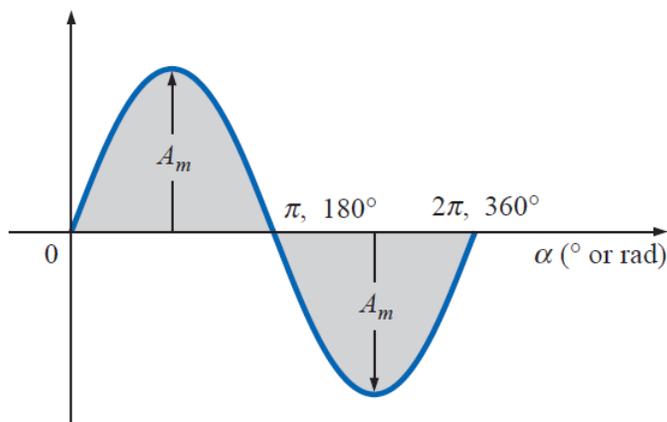

$$A_m \sin \omega t$$

For electrical quantities such as current and voltage, the general format is:

$$i = I_m \sin \omega t = I_m \sin \alpha$$

$$e = E_m \sin \omega t = E_m \sin \alpha$$

EXAMPLE: Given $e = 5 \sin \alpha$, determine e at $\alpha = 40^\circ$ and $\alpha = 0.8 \pi$.

Solution:

For $\alpha = 40^\circ$,

$$e = 5 \sin 40^\circ = 5(0.6428) = 3.214 \text{ V}$$

For $\alpha = 0.8\pi$,


$$\alpha (^{\circ}) = \frac{180^{\circ}}{\pi} (0.8\pi) = 144^{\circ}$$

and $e = 5 \sin 144^{\circ} = 5(0.5878) = 2.939 \text{ V}$


EXAMPLE: Sketch $e = 10 \sin 314 t$ with the abscissa

- angle (α) in degrees.
- angle (α) in radians.
- time (t) in seconds.

Solution:

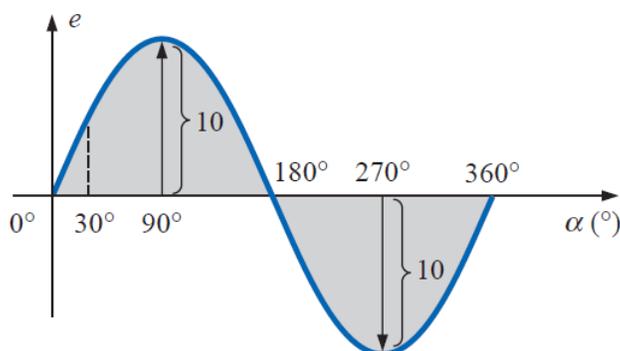

(a)

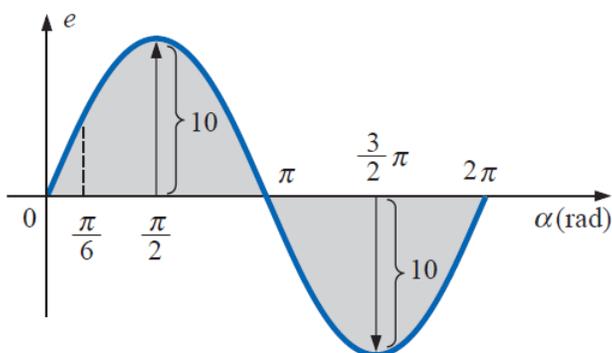


(b)

$$c. 360^\circ: T = \frac{2\pi}{\omega} = \frac{2\pi}{314} = 20 \text{ ms}$$

$$180^\circ: \frac{T}{2} = \frac{20 \text{ ms}}{2} = 10 \text{ ms}$$

$$90^\circ: \frac{T}{4} = \frac{20 \text{ ms}}{4} = 5 \text{ ms}$$
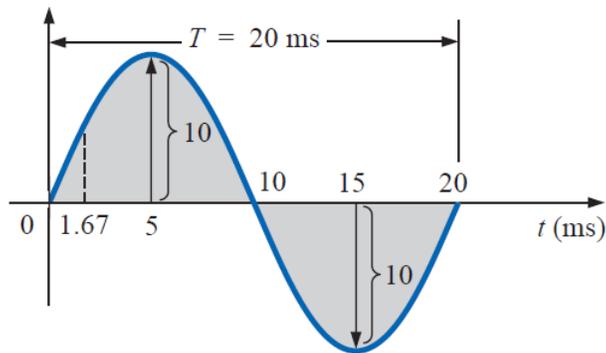
$$30^\circ: \frac{T}{12} = \frac{20 \text{ ms}}{12} = 1.67 \text{ ms}$$



EXAMPLE: Given $i = 6 \times 10^{-3} \sin 1000 t$, determine i at $t = 2 \text{ ms}$.

Solution:

$$\alpha = \omega t = 1000t = (1000 \text{ rad/s})(2 \times 10^{-3} \text{ s}) = 2 \text{ rad}$$

$$\alpha (^\circ) = \frac{180^\circ}{\pi \text{ rad}} (2 \text{ rad}) = 114.59^\circ$$

$$\begin{aligned} i &= (6 \times 10^{-3})(\sin 114.59^\circ) \\ &= (6 \text{ mA})(0.9093) = \mathbf{5.46 \text{ mA}} \end{aligned}$$



الوحدة العشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

PHASE RELATIONS

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	20

PHASE RELATIONS


* If the waveform passes through the horizontal axis with a *positive going* (increasing with time) slope *before* 0° .

$$A_m \sin(\omega t + \theta)$$

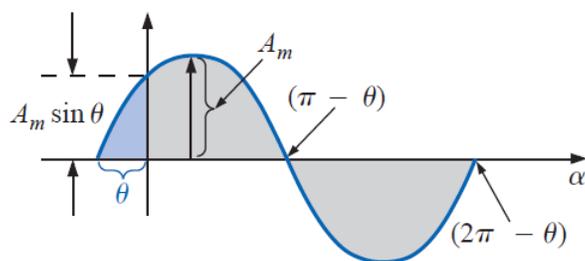


* If the waveform passes through the horizontal axis with a positive-going slope *after* 0° ,

$$A_m \sin(\omega t - \theta)$$

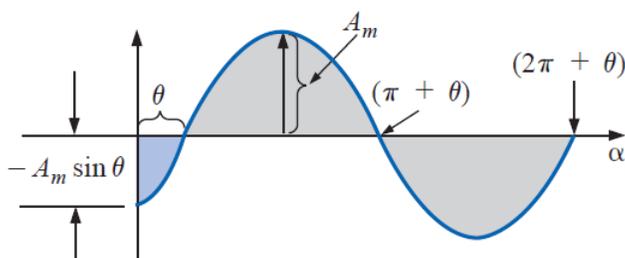

* If the waveform crosses the horizontal axis with a positive-going slope 90° ($\pi/2$) sooner, it is called a *cosine wave*.

$$\sin(\omega t + 90^\circ) = \sin\left(\omega t + \frac{\pi}{2}\right) = \cos \omega t$$

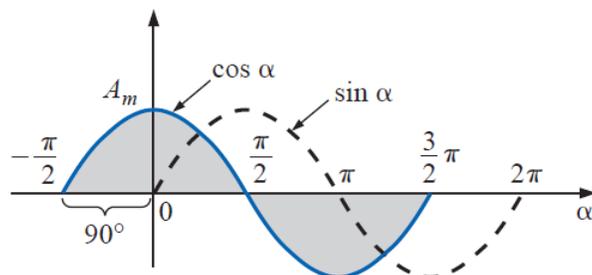


EXAMPLE 13.12 What is the phase relationship between the sinusoidal waveforms of each of the following sets?


- $v = 10 \sin(\omega t + 30^\circ)$
 $i = 5 \sin(\omega t + 70^\circ)$
- $i = 15 \sin(\omega t + 60^\circ)$
 $v = 10 \sin(\omega t - 20^\circ)$
- $i = 2 \cos(\omega t + 10^\circ)$
 $v = 3 \sin(\omega t - 10^\circ)$
- $i = -\sin(\omega t + 30^\circ)$
 $v = 2 \sin(\omega t + 10^\circ)$
- $i = -2 \cos(\omega t - 60^\circ)$
 $v = 3 \sin(\omega t - 150^\circ)$

Solutions:

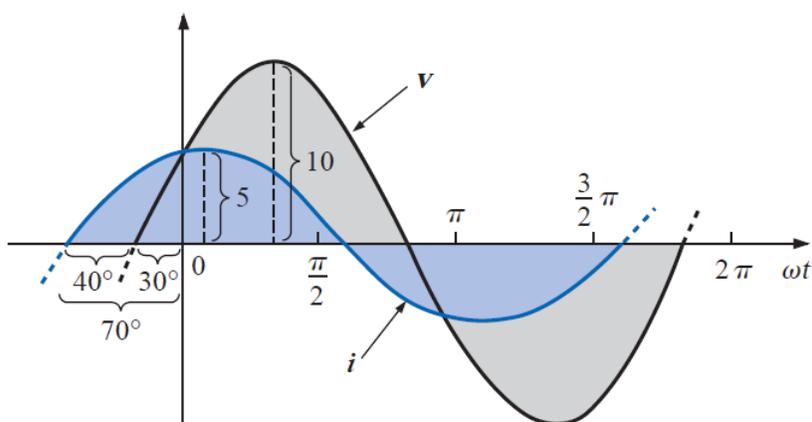a) i leads v by 40° , or v lags i by 40° .



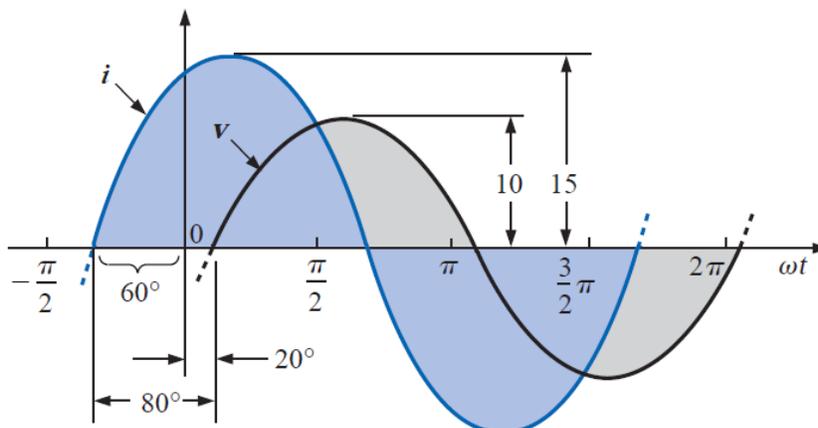
b) i leads v by 80° , or v lags i by 80° .



c)

$$i = 2 \cos(\omega t + 10^\circ) = 2 \sin(\omega t + 10^\circ + 90^\circ) \\ = 2 \sin(\omega t + 100^\circ)$$

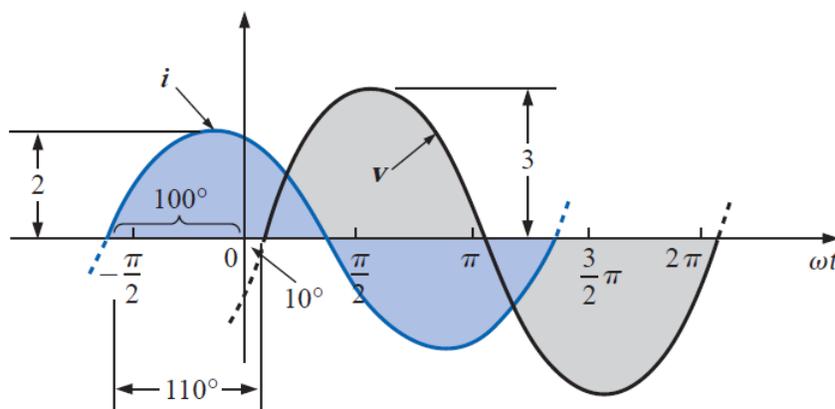
i leads *v* by 110° , or *v* lags *i* by 110° .



d)

$$-\sin(\omega t + 30^\circ) = \sin(\omega t + 30^\circ - 180^\circ) \\ = \sin(\omega t - 150^\circ)$$

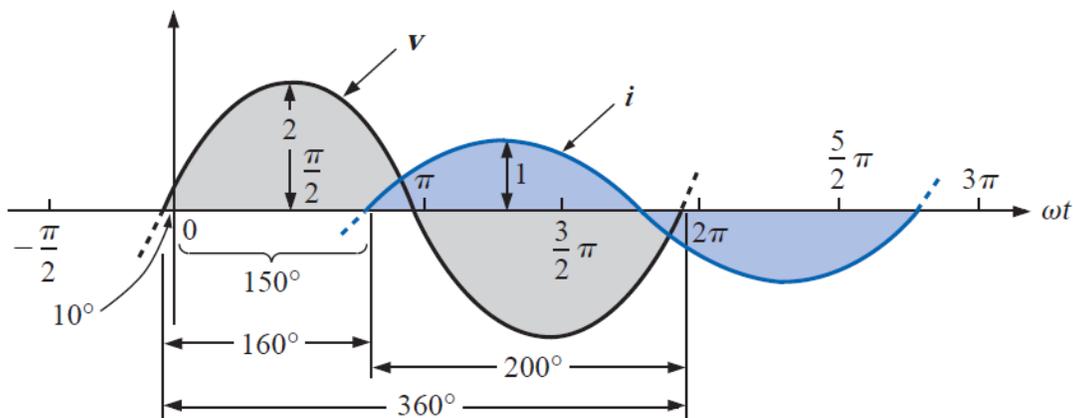
v leads *i* by 160° , or *i* lags *v* by 160° .



e)

$$i = -2 \cos(\omega t - 60^\circ) = 2 \cos(\omega t - 60^\circ - 180^\circ) \quad \text{By choice}$$

$$= 2 \cos(\omega t - 240^\circ)$$

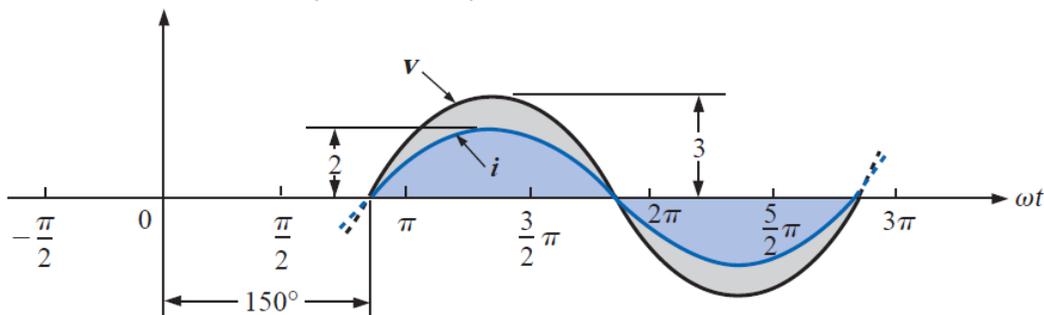

However, $\cos \alpha = \sin(\alpha + 90^\circ)$

$$\text{so that } 2 \cos(\omega t - 240^\circ) = 2 \sin(\omega t - 240^\circ + 90^\circ)$$

$$= 2 \sin(\omega t - 150^\circ)$$

v and i are in phase.



الوحدة الواحد والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

AVERAGE VALUE (mean)

موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية


الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب	• نشاط التعارف	21
• جهاز عرض	• محاضرة	
• سبورة	• مناقشة	
• اوراق واقلام	• سؤال وجواب	

AVERAGE VALUE (mean)


The average value of alternating waveform is the equivalent (DC) value over a complete cycle. In general the average value of a waveform is given as:

$$G \text{ (average value)} = \frac{\text{algebraic sum of areas}}{\text{length of curve}}$$

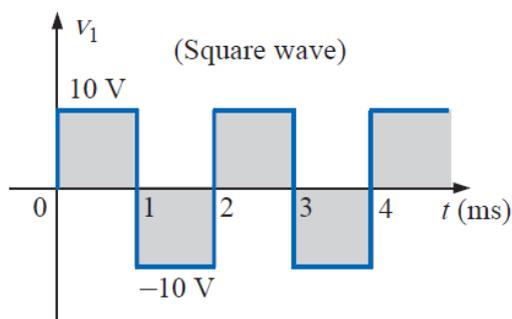EXAMPLE: Determine the average value of the waveforms



(a)

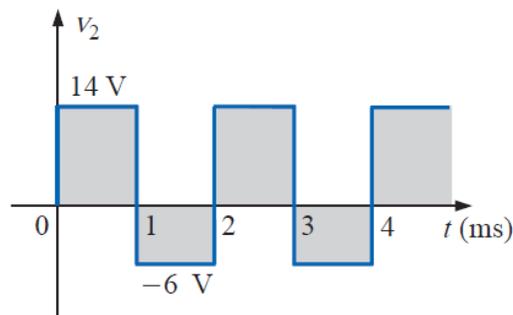

(b)

Solutions:

a) By inspection, the area above the axis equals the area below over one cycle, resulting in an average value of zero volts.


$$\begin{aligned} G &= \frac{(10 \text{ V})(1 \text{ ms}) - (10 \text{ V})(1 \text{ ms})}{2 \text{ ms}} \\ &= \frac{0}{2 \text{ ms}} = \mathbf{0 \text{ V}} \end{aligned}$$

b)


$$\begin{aligned} G &= \frac{(14 \text{ V})(1 \text{ ms}) - (6 \text{ V})(1 \text{ ms})}{2 \text{ ms}} \\ &= \frac{14 \text{ V} - 6 \text{ V}}{2} = \frac{8 \text{ V}}{2} = \mathbf{4 \text{ V}} \end{aligned}$$

EXAMPLE: Find the average values of the following waveforms over one full cycle:

a)

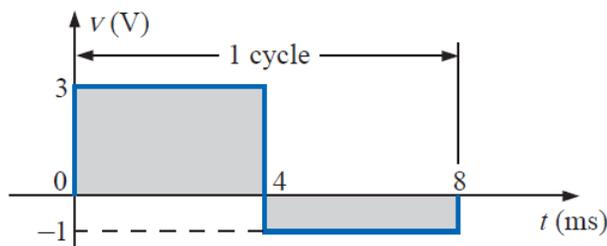

b)

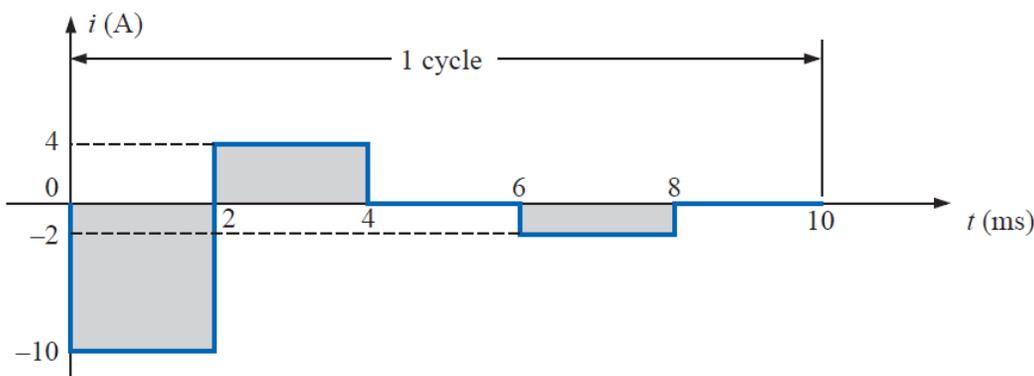

Solutions:

$$a. G = \frac{+(3 \text{ V})(4 \text{ ms}) - (1 \text{ V})(4 \text{ ms})}{8 \text{ ms}} = \frac{12 \text{ V} - 4 \text{ V}}{8} = 1 \text{ V}$$


$$b. G = \frac{-(10 \text{ V})(2 \text{ ms}) + (4 \text{ V})(2 \text{ ms}) - (2 \text{ V})(2 \text{ ms})}{10 \text{ ms}}$$

$$= \frac{-20 \text{ V} + 8 \text{ V} - 4 \text{ V}}{10} = -\frac{16 \text{ V}}{10} = -1.6 \text{ V}$$


The area of **sine wave** (for one half) can be calculated by the following:

$$\text{Area} = \int_0^{\pi} A_m \sin \alpha \, d\alpha$$
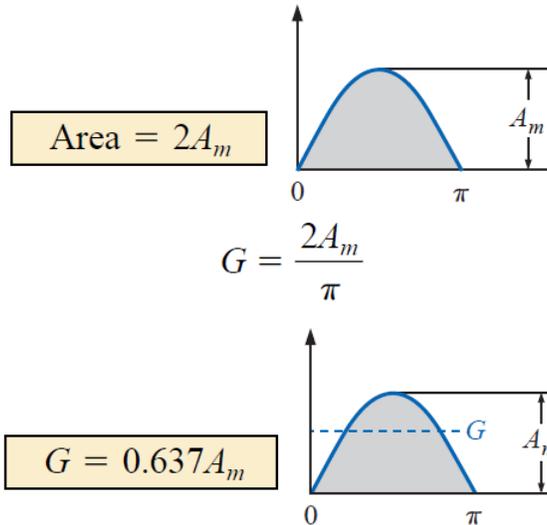
$$\begin{aligned} \text{Area} &= A_m [-\cos \alpha]_0^{\pi} \\ &= -A_m (\cos \pi - \cos 0^\circ) \\ &= -A_m [-1 - (+1)] = -A_m (-2) \end{aligned}$$



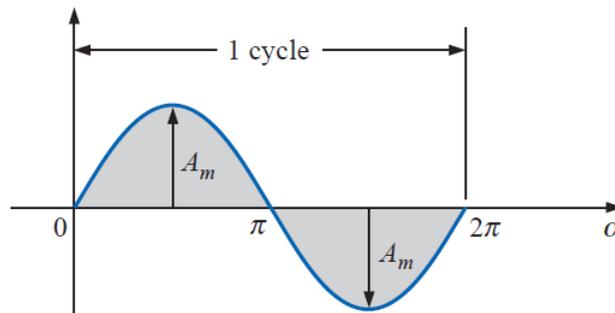EXAMPLE: Determine the average value of the sinusoidal waveform




Solutions:

The average value of a pure sinusoidal waveform over one full cycle is zero.

$$G = \frac{+2A_m - 2A_m}{2\pi} = 0 \text{ V}$$

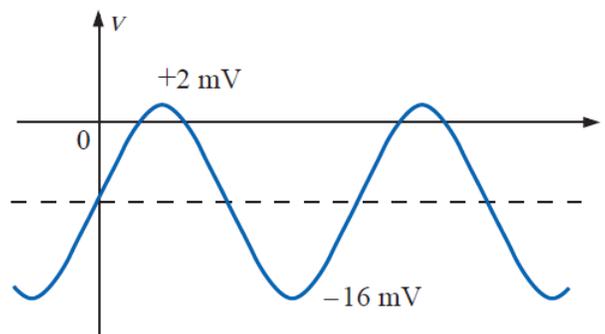
EXAMPLE: Determine the average value of the waveform



Solutions:

The peak-to-peak value of the sinusoidal function is $16 \text{ mV} + 2 \text{ mV} = 18 \text{ mV}$. The peak amplitude of the sinusoidal waveform is, therefore, $18 \text{ mV}/2 = 9 \text{ mV}$. Counting down 9 mV from 2 mV (or 9 mV up from -16 mV) results in an average or dc level of -7 mV .

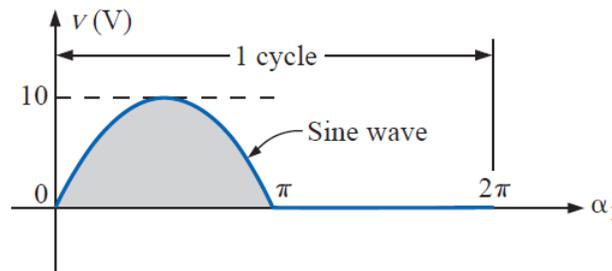EXAMPLE: Determine the average value of the waveform



Solutions:

$$G = \frac{2A_m + 0}{2\pi} = \frac{2(10 \text{ V})}{2\pi} \cong 3.18 \text{ V}$$



الوحدة الثانية والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

The effective value (or the rms value) of an alternating waveform is given by the steady (dc) current which when flowing through a given circuit, for a given time produces the same heat produced by the alternating current when flowing the same circuit for the same time.

موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب	• نشاط التعارف	22
• جهاز عرض	• محاضرة	
• سبورة	• مناقشة	
• اوراق واقلام	• سؤال وجواب	



EFFECTIVE (rms) VALUES

The effective value (or the rms value) of an alternating waveform is given by the steady (dc) current which when flowing through a given circuit, for a given time produces the same heat produced by the alternating current when flowing the same circuit for the same time.

Effective value of the sinusoidal is:

$$I_{\text{eff}} = 0.707I_m$$


$$E_{\text{eff}} = 0.707E_m$$

The effective value of any quantity plotted as a function of time can be found by using the following equation:

$$I_{\text{eff}} = \sqrt{\frac{\int_0^T i^2(t) dt}{T}}$$

$$I_{\text{eff}} = \sqrt{\frac{\text{area}(i^2(t))}{T}}$$

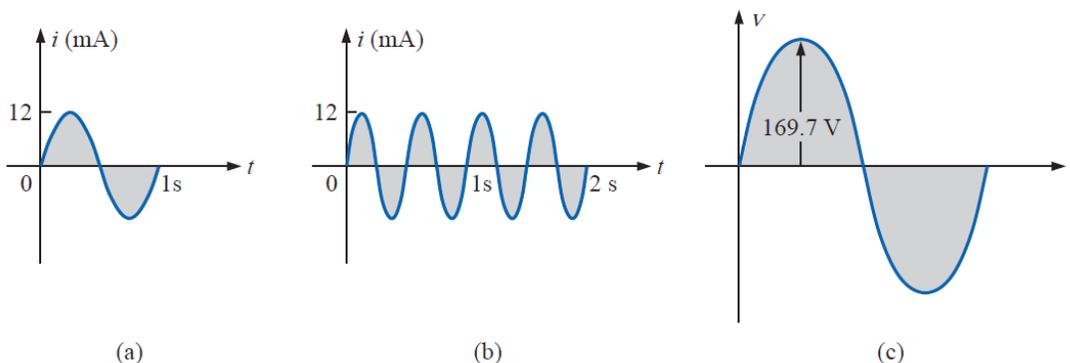
EXAMPLE: Find the rms values of the sinusoidal waveform



Solution:

For part (a), $I_{rms} = 0.707(12 * 10^{-3} \text{ A}) = 8.484 \text{ mA}$. For part (b), again $I_{rms} = 8.484 \text{ mA}$. Note that frequency did not change the effective value in (b) above compared to (a). For part (c), $V_{rms} = 0.707(169.73 \text{ V}) \cong 120 \text{ V}$.

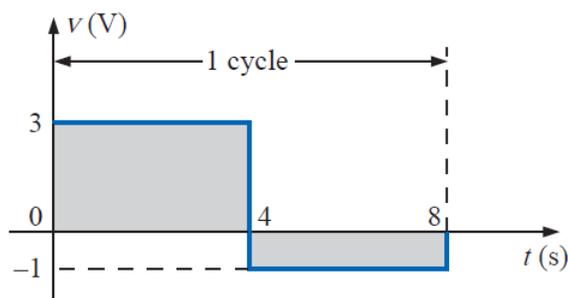
EXAMPLE: Find the effective or rms value of the waveform



Solution:

$$V_{rms} = \sqrt{\frac{(9)(4) + (1)(4)}{8}} = \sqrt{\frac{40}{8}} = 2.236 \text{ V}$$

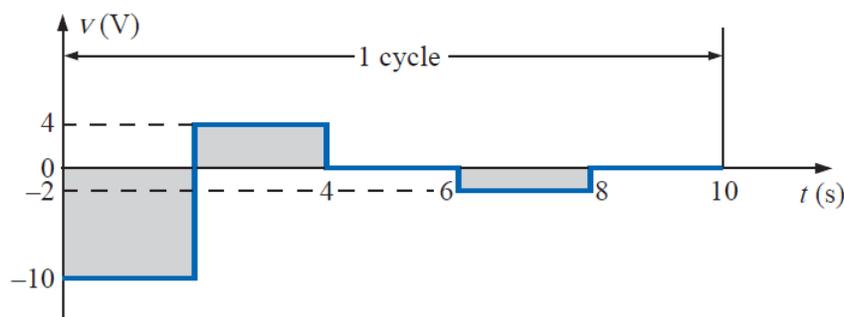
EXAMPLE: Calculate the rms value of the voltage



Solution:

$$V_{\text{rms}} = \sqrt{\frac{(100)(2) + (16)(2) + (4)(2)}{10}} = \sqrt{\frac{240}{10}}$$
$$= 4.899 \text{ V}$$

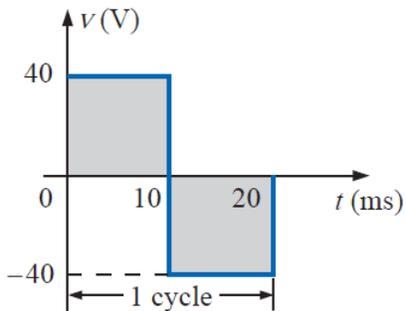EXAMPLE: Determine the average and rms values of the square wave.



Solution:

$$V_{\text{rms}} = \sqrt{\frac{(1600)(10 \times 10^{-3}) + (1600)(10 \times 10^{-3})}{20 \times 10^{-3}}}$$
$$= \sqrt{\frac{32,000 \times 10^{-3}}{20 \times 10^{-3}}} = \sqrt{1600}$$
$$V_{\text{rms}} = 40 \text{ V}$$



الوحدة الثالثة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

موضوعات المحاضرة


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	22

RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

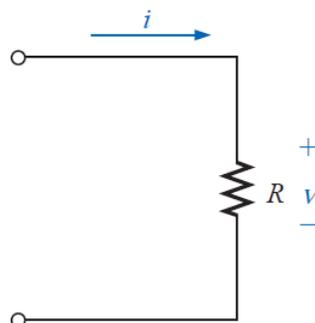1) Resistor

For a purely resistive element, the voltage across and the current through the element are in phase, with their peak values related by Ohm's law.



For $v = V_m \sin \omega t$,


$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R}$$

Or

$$v = iR = (I_m \sin \omega t)R = I_m R \sin \omega t = V_m \sin \omega t$$


$$V_m = I_m R$$

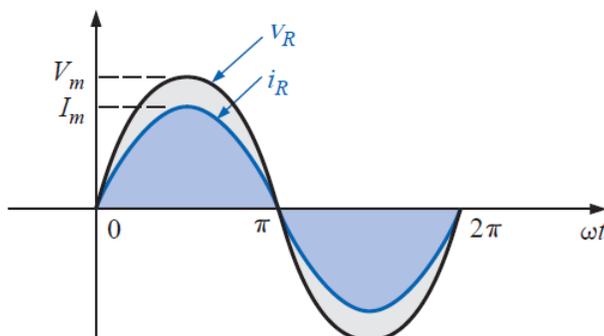

2) Inductor

For an inductor, v_L leads i_L by 90° , or i_L lags v_L by 90° .

$$v_L = L \frac{di_L}{dt}$$

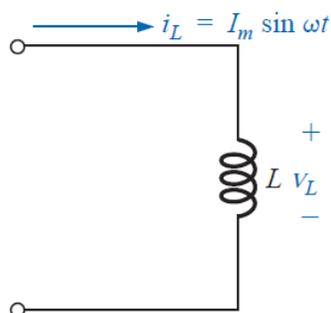

$$\frac{di_L}{dt} = \frac{d}{dt}(I_m \sin \omega t) = \omega I_m \cos \omega t$$


$$v_L = L \frac{di_L}{dt} = L(\omega I_m \cos \omega t) = \omega L I_m \cos \omega t$$

$$v_L = V_m \sin(\omega t + 90^\circ)$$

$$V_m = \omega L I_m$$

$$i_L = I_m \sin(\omega t \pm \theta)$$
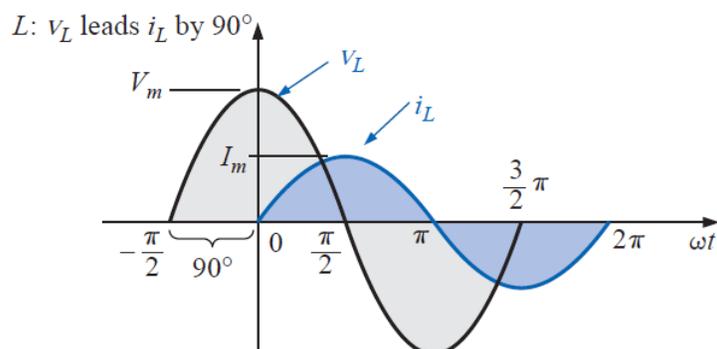
$$v_L = \omega L I_m \sin(\omega t \pm \theta + 90^\circ)$$



The quantity ωL , called the **reactance** (from the word *reaction*) of an inductor, is symbolically represented by X_L and is measured in ohms; that is,

$$X_L = \omega L \quad (\text{ohms, } \Omega)$$


$$X_L = \frac{V_m}{I_m} \quad (\text{ohms, } \Omega)$$

$$X_L = \omega L = 2\pi fL = 2\pi Lf$$

3) Capacitor

For a particular capacitance, the greater the rate of change of voltage across the capacitor, the greater the capacitive current.

$$i_C = C \frac{dv_C}{dt}$$

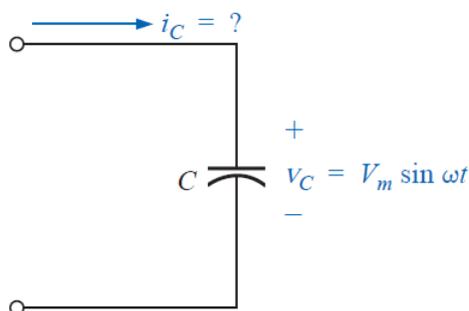

$$\frac{dv_C}{dt} = \frac{d}{dt}(V_m \sin \omega t) = \omega V_m \cos \omega t$$

$$i_C = C \frac{dv_C}{dt} = C(\omega V_m \cos \omega t) = \omega C V_m \cos \omega t$$

$$i_C = I_m \sin(\omega t + 90^\circ)$$

$$I_m = \omega C V_m$$

For a capacitor, i_C leads v_C by 90° , or v_C lags i_C by 90° .

$$v_C = V_m \sin(\omega t \pm \theta)$$

$$i_C = \omega C V_m \sin(\omega t \pm \theta + 90^\circ)$$


The quantity $1/\omega C$, called the **reactance** of a capacitor, is symbolically represented by X_C and is measured in ohms; that is,

$$X_C = \frac{1}{\omega C} \quad (\text{ohms}, \Omega)$$

$$X_C = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega)$$

$$X_C = \frac{1}{2\pi f C}$$

C: i_C leads v_C by 90° .

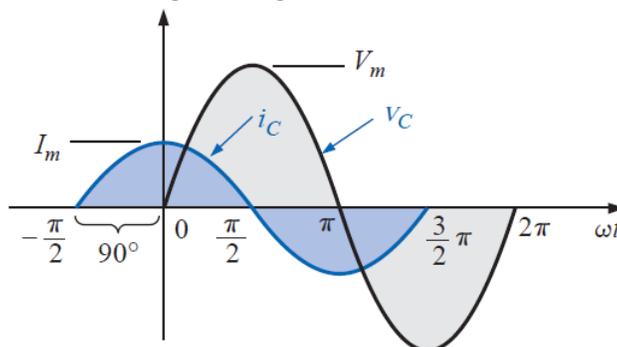

EXAMPLE: The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is 10Ω . Sketch the curves for v and i .

a) $v = 100 \sin 377t$

b) $v = 25 \sin(377t + 60^\circ)$


Solutions:

a)

$$I_m = \frac{V_m}{R} = \frac{100 \text{ V}}{10 \Omega} = 10 \text{ A}$$

(v and i are in phase)

$$i = 10 \sin 377t$$

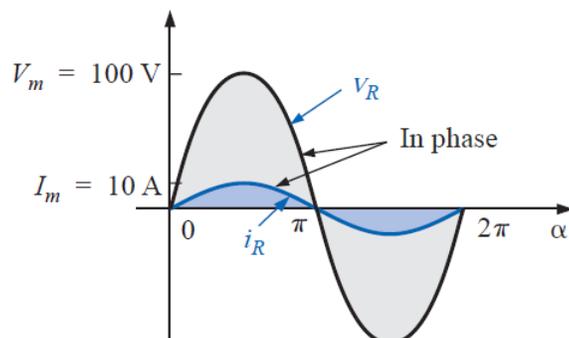


b)

$$I_m = \frac{V_m}{R} = \frac{25 \text{ V}}{10 \Omega} = 2.5 \text{ A}$$

(v and i are in phase)

$$i = 2.5 \sin(377t + 60^\circ)$$

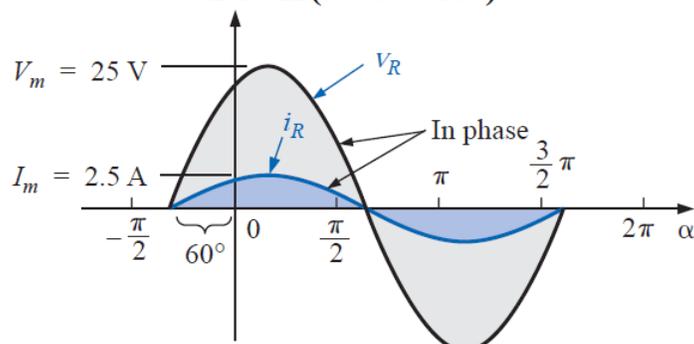

EXAMPLE: The current through a 0.1-H coil is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the v and i curves.

a) $i = 10 \sin 377t$

b) $i = 7 \sin(377t - 70^\circ)$

Solutions:


a)

$$X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.7 \Omega$$

$$V_m = I_m X_L = (10 \text{ A})(37.7 \Omega) = 377 \text{ V}$$

v leads i by 90°

$$v = 377 \sin(377t + 90^\circ)$$

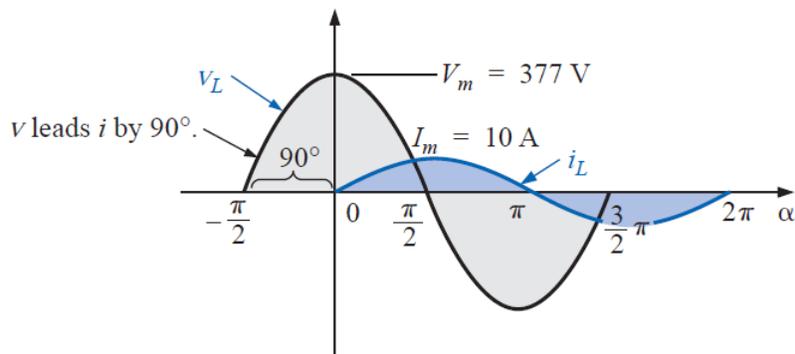


b)

$$V_m = I_m X_L = (7 \text{ A})(37.7 \Omega) = 263.9 \text{ V}$$

v leads i by 90°

$$v = 263.9 \sin(377t - 70^\circ + 90^\circ)$$

$$v = 263.9 \sin(377t + 20^\circ)$$

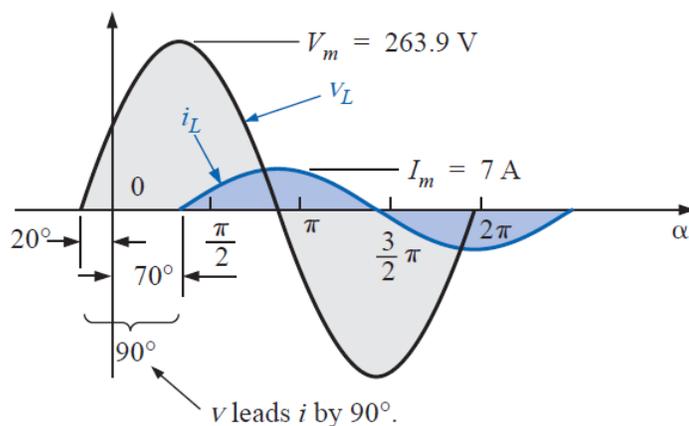

EXAMPLE: The voltage across a $1\text{-}\mu\text{F}$ capacitor is provided below. What is the sinusoidal expression for the current? Sketch the v and i curves.


$$v = 30 \sin 400t$$

Solutions:

$$X_C = \frac{1}{\omega C} = \frac{1}{(400 \text{ rad/s})(1 \times 10^{-6} \text{ F})} = \frac{10^6 \Omega}{400} = 2500 \Omega$$

$$I_m = \frac{V_m}{X_C} = \frac{30 \text{ V}}{2500 \Omega} = 0.0120 \text{ A} = 12 \text{ mA}$$

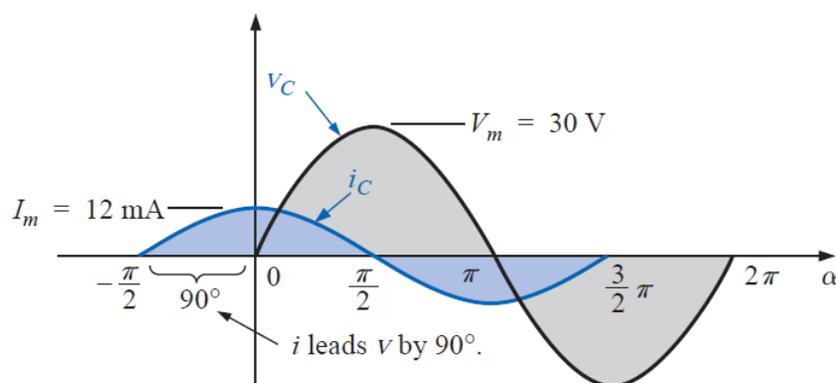i leads v by 90° $i = 12 \times 10^{-3} \sin(400t + 90^\circ)$



EXAMPLE: At what frequency will the reactance of a 200-mH inductor match the resistance level of a 5-k Ω resistor?

Solutions:

$$5000 \Omega = X_L = 2\pi fL = 2\pi Lf$$

$$= 2\pi(200 \times 10^{-3} \text{ H})f = 1.257f$$

$$f = \frac{5000 \text{ Hz}}{1.257} \cong 3.98 \text{ kHz}$$



الوحدة الرابعة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

A **complex number** represents a point in a two-dimensional plane located with reference to two distinct axes. This point can also determine a radius vector drawn from the origin to the point.

موضوعات المحاضرة

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	24

COMPLEX NUMBERS


A **complex number** represents a point in a two-dimensional plane located with reference to two distinct axes. This point can also determine a radius vector drawn from the origin to the point. The horizontal axis is called the *real axis*, while the vertical axis is called the *imaginary axis*.

Two forms are used to represent a complex number: **rectangular** and **polar**.

1) RECTANGULAR FORM

The format for the **rectangular form** is

$$C = X + jY$$

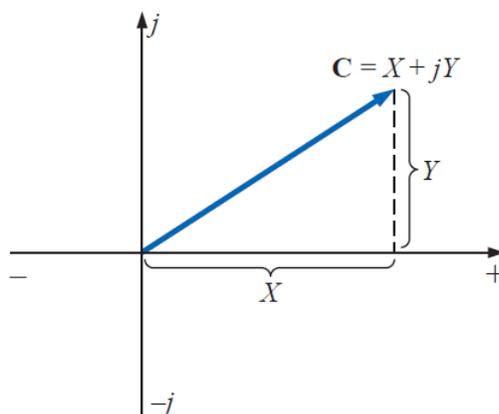


EXAMPLE: Sketch the following complex numbers in the complex plane:


- a) $C = 3 + j 4$
- b) $C = 0 - j 6$
- c) $C = -10 - j20$

Solutions:


- a)

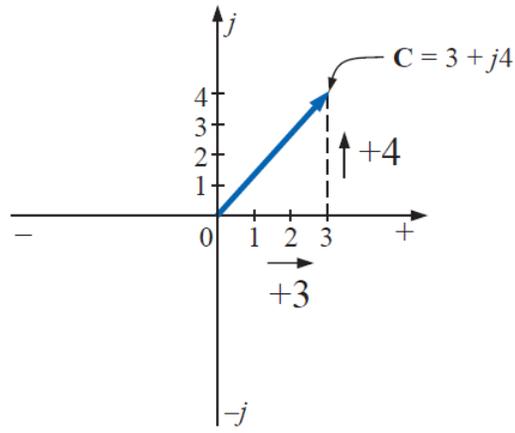

b)

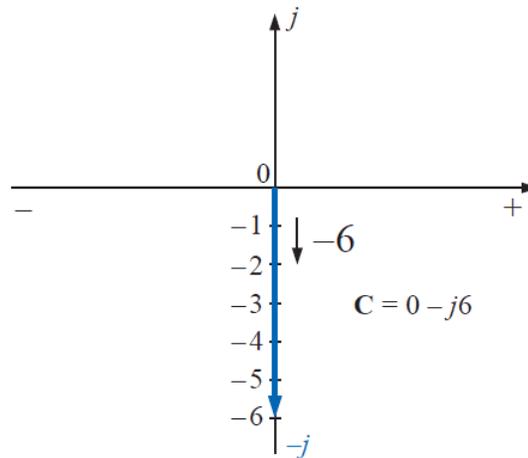


c)

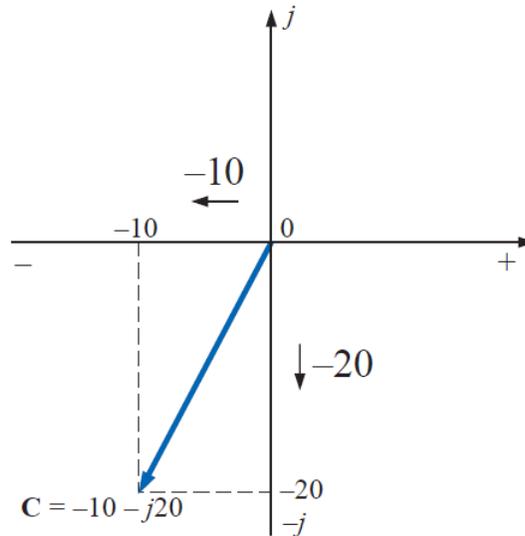

2) POLAR FORM

The format for the **polar form** is

$$C = Z \angle \theta$$

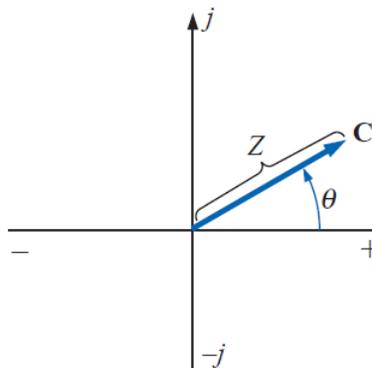


$$-C = -Z \angle \theta = Z \angle \theta \pm 180^\circ$$

EXAMPLE: Sketch the following complex numbers in the complex plane:


- a) $C = 5 \angle 30^\circ$
- b) $C = 7 \angle -120^\circ$
- c) $C = -4.2 \angle 60^\circ$

Solutions:

a)

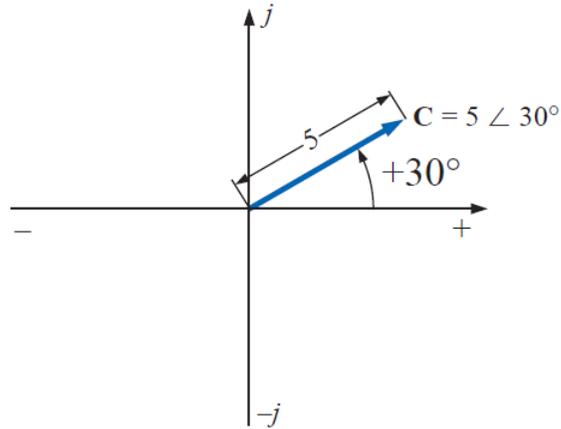


b)

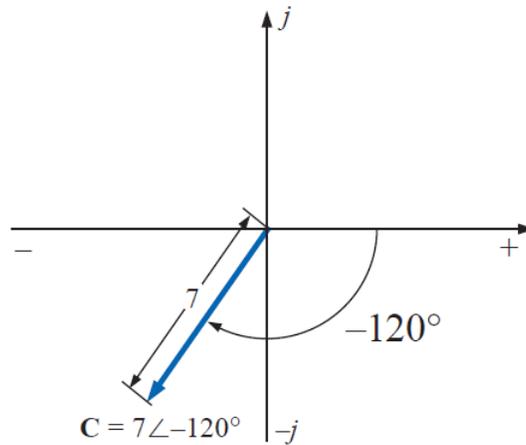


c)
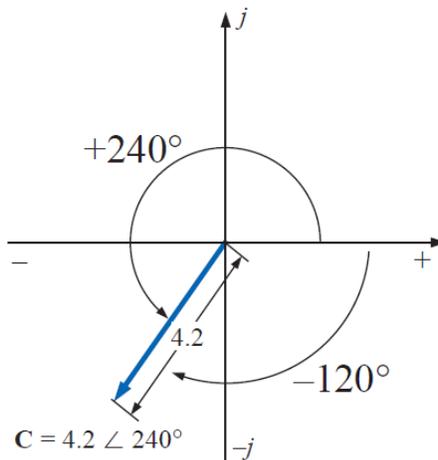
$$C = -4.2 \angle 60^\circ = 4.2 \angle 60^\circ + 180^\circ \\ = 4.2 \angle +240^\circ$$



CONVERSION BETWEEN FORMS

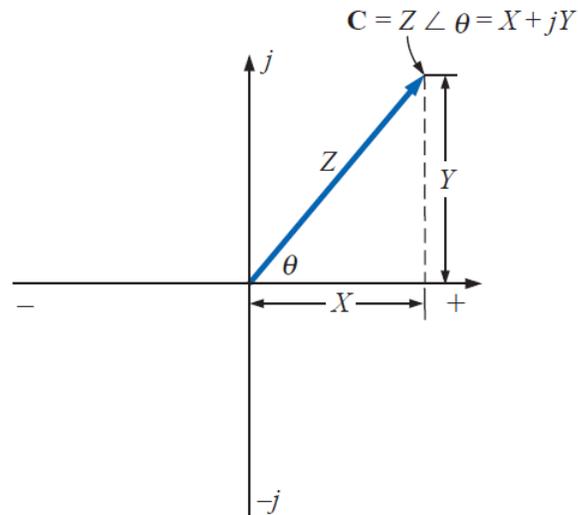

1) Rectangular to Polar

$$Z = \sqrt{X^2 + Y^2}$$

$$\theta = \tan^{-1} \frac{Y}{X}$$

2) Polar to Rectangular

$$X = Z \cos \theta$$

$$Y = Z \sin \theta$$

EXAMPLE: Convert the following from rectangular to polar form:


$$C = 3 + j4$$

Solutions:

$$Z = \sqrt{(3)^2 + (4)^2} = \sqrt{25} = 5$$


$$\theta = \tan^{-1}\left(\frac{4}{3}\right) = 53.13^\circ$$

$$C = 5 \angle 53.13^\circ$$

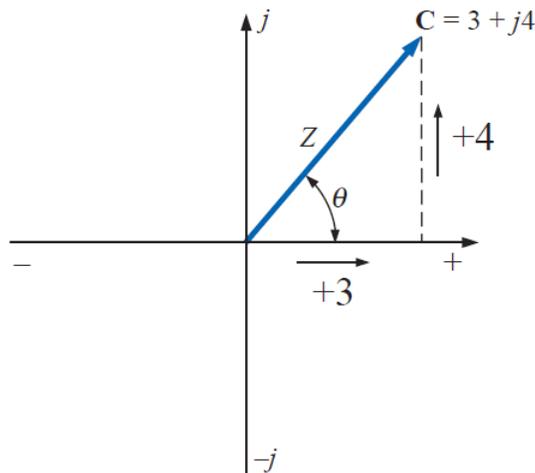

EXAMPLE: Convert the following from polar to rectangular form:

$$C = 10 \angle 45^\circ$$

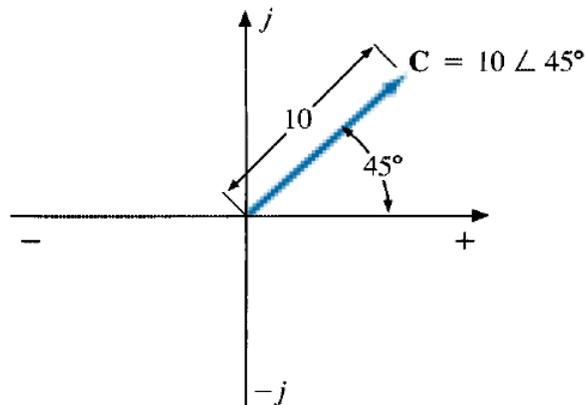

Solutions:

$$X = 10 \cos 45^\circ = (10)(0.707) = 7.07$$

$$Y = 10 \sin 45^\circ = (10)(0.707) = 7.07$$

$$C = 7.07 + j7.07$$



الوحدة الخامسة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Complex numbers lend themselves readily to the basic mathematical operations of addition, subtraction, multiplication, and division.

موضوعات المحاضرة الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	25

MATHEMATICAL OPERATIONS WITH COMPLEX NUMBERS

Complex numbers lend themselves readily to the basic mathematical operations of addition, subtraction, multiplication, and division. A few basic rules and definitions must be understood before considering these operations.

$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$\frac{1}{j} = -j$$

1) Addition

$$C_1 = \pm X_1 \pm j Y_1 \quad \text{and} \quad C_2 = \pm X_2 \pm j Y_2$$

$$C_1 + C_2 = (\pm X_1 \pm X_2) + j (\pm Y_1 \pm Y_2)$$

EXAMPLE:

- Add $C_1 = 2 + j4$ and $C_2 = 3 + j1$.
- Add $C_1 = 3 + j6$ and $C_2 = -6 + j3$.

Solutions:

a)

$$C_1 + C_2 = (2 + 3) + j(4 + 1) = 5 + j5$$

b)

$$C_1 + C_2 = (3 - 6) + j(6 + 3) = -3 + j9$$

2) Subtraction

$$C_1 = \pm X_1 \pm j Y_1 \quad \text{and} \quad C_2 = \pm X_2 \pm j Y_2$$

$$C_1 - C_2 = [\pm X_1 - (\pm X_2)] + j[\pm Y_1 - (\pm Y_2)]$$

EXAMPLE:



- a. Subtract $C_2 = 1 + j4$ from $C_1 = 4 + j6$.
b. Subtract $C_2 = -2 + j5$ from $C_1 = +3 + j3$.

Solutions:

a)

$$C_1 - C_2 = (4 - 1) + j(6 - 4) = 3 + j2$$

b)

$$C_1 - C_2 = [3 - (-2)] + j(3 - 5) = 5 - j2$$

3) Multiplication

$$C_1 = X_1 + jY_1 \quad \text{and} \quad C_2 = X_2 + jY_2$$

$$C_1 \cdot C_2 = (X_1X_2 - Y_1Y_2) + j(Y_1X_2 + X_1Y_2)$$

$$C_1 = Z_1 \angle \theta_1 \quad \text{and} \quad C_2 = Z_2 \angle \theta_2$$

$$C_1 \cdot C_2 = Z_1Z_2 \angle \theta_1 + \theta_2$$

EXAMPLE:

- a. Find $C_1 \cdot C_2$ if

$$C_1 = 5 \angle 20^\circ \quad \text{and} \quad C_2 = 10 \angle 30^\circ$$

- b. Find $C_1 \cdot C_2$ if

$$C_1 = 2 \angle -40^\circ \quad \text{and} \quad C_2 = 7 \angle +120^\circ$$

Solutions:

a. $C_1 \cdot C_2 = (5 \angle 20^\circ)(10 \angle 30^\circ) = (5)(10) \angle 20^\circ + 30^\circ = 50 \angle 50^\circ$

b. $C_1 \cdot C_2 = (2 \angle -40^\circ)(7 \angle +120^\circ) = (2)(7) \angle -40^\circ + 120^\circ$
 $= 14 \angle +80^\circ$

4) Division

$$C_1 = Z_1 \angle \theta_1 \quad \text{and} \quad C_2 = Z_2 \angle \theta_2$$

$$\frac{C_1}{C_2} = \frac{Z_1}{Z_2} \angle \theta_1 - \theta_2$$



EXAMPLE:

- a. Find C_1/C_2 if $C_1 = 15 \angle 10^\circ$ and $C_2 = 2 \angle 7^\circ$.
b. Find C_1/C_2 if $C_1 = 8 \angle 120^\circ$ and $C_2 = 16 \angle -50^\circ$.

Solutions:


a.
$$\frac{C_1}{C_2} = \frac{15 \angle 10^\circ}{2 \angle 7^\circ} = \frac{15}{2} \angle 10^\circ - 7^\circ = 7.5 \angle 3^\circ$$

b.
$$\frac{C_1}{C_2} = \frac{8 \angle 120^\circ}{16 \angle -50^\circ} = \frac{8}{16} \angle 120^\circ - (-50^\circ) = 0.5 \angle 170^\circ$$

$$\frac{1}{Z \angle \theta} = \frac{1}{Z} \angle -\theta$$

PHASORS

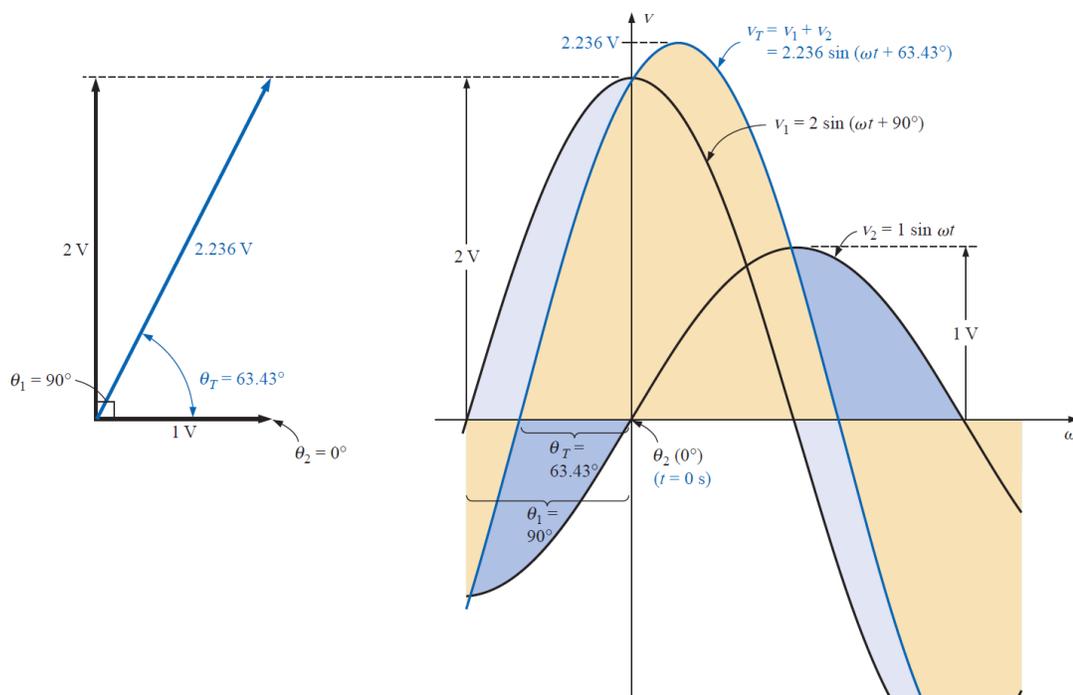The *radius vector*, having a constant magnitude (length) with one end fixed at the origin, is called a **phasor** when applied to electric circuits.



$$e = V_m \sin(\omega t + \theta) \Rightarrow e = \frac{V_m}{\sqrt{2}} \angle \theta = 0.707 V_m \angle \theta$$

EXAMPLE: Convert the following from the time to the phasor domain:


Time Domain	Phasor Domain
a. $\sqrt{2}(50) \sin \omega t$	$50 \angle 0^\circ$
b. $69.6 \sin(\omega t + 72^\circ)$	$(0.707)(69.6) \angle 72^\circ = 49.21 \angle 72^\circ$
c. $45 \cos \omega t$	$(0.707)(45) \angle 90^\circ = 31.82 \angle 90^\circ$

EXAMPLE: Write the sinusoidal expression for the following phasors if the frequency is 60 Hz:

Phasor Domain	Time Domain
a. $\mathbf{I} = 10 \angle 30^\circ$	$i = \sqrt{2}(10) \sin(2\pi 60t + 30^\circ)$ and $i = 14.14 \sin(377t + 30^\circ)$
b. $\mathbf{V} = 115 \angle -70^\circ$	$v = \sqrt{2}(115) \sin(377t - 70^\circ)$ and $v = 162.6 \sin(377t - 70^\circ)$

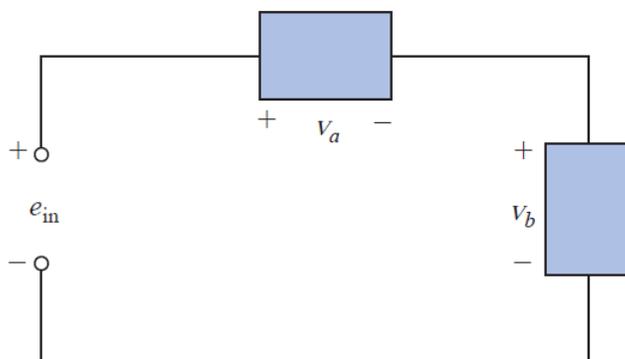EXAMPLE: Find the input voltage of the circuit

$$\left. \begin{aligned} v_a &= 50 \sin(377t + 30^\circ) \\ v_b &= 30 \sin(377t + 60^\circ) \end{aligned} \right\} f = 60 \text{ Hz}$$



Solutions:

$$e_{\text{in}} = v_a + v_b$$

Converting from the time to the phasor domain yields

$$v_a = 50 \sin(377t + 30^\circ) \Rightarrow \mathbf{V}_a = 35.35 \text{ V} \angle 30^\circ$$

$$v_b = 30 \sin(377t + 60^\circ) \Rightarrow \mathbf{V}_b = 21.21 \text{ V} \angle 60^\circ$$

Converting from polar to rectangular form for addition yields

$$\mathbf{V}_a = 35.35 \text{ V} \angle 30^\circ = 30.61 \text{ V} + j17.68 \text{ V}$$

$$\mathbf{V}_b = 21.21 \text{ V} \angle 60^\circ = 10.61 \text{ V} + j18.37 \text{ V}$$

$$\begin{aligned} \mathbf{E}_{\text{in}} &= \mathbf{V}_a + \mathbf{V}_b = (30.61 \text{ V} + j17.68 \text{ V}) + (10.61 \text{ V} + j18.37 \text{ V}) \\ &= 41.22 \text{ V} + j36.05 \text{ V} \end{aligned}$$

$$\mathbf{E}_{\text{in}} = 41.22 \text{ V} + j36.05 \text{ V} = 54.76 \text{ V} \angle 41.17^\circ$$



$$E_{in} = 54.76 \text{ V} \angle 41.17^\circ \Rightarrow e_{in} = \sqrt{2}(54.76) \sin(377t + 41.17^\circ)$$

$$e_{in} = 77.43 \sin(377t + 41.17^\circ)$$

الوحدة السادس والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

IMPEDANCE AND THE PHASOR DIAGRAM

موضوعات المحاضرة


Examples

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">• جهاز حاسوب• جهاز عرض• سبورة• اوراق واقلام	<ul style="list-style-type: none">• نشاط التعارف• محاضرة• مناقشة• سؤال وجواب	26


IMPEDANCE AND THE PHASOR DIAGRAM

1) Resistive Elements

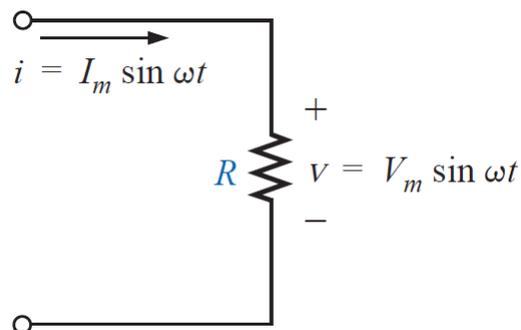

$$\mathbf{Z}_R = R \angle 0^\circ$$

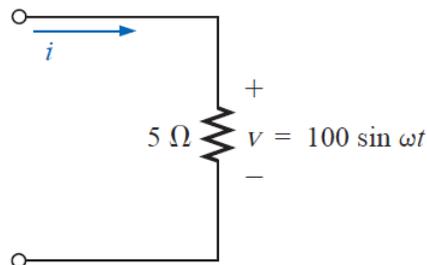EXAMPLE: find the current i for the circuit. Sketch the waveforms of v and i .




Solutions:

$$v = 100 \sin \omega t \Rightarrow \text{phasor form } \mathbf{V} = 70.71 \text{ V } \angle 0^\circ$$


$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_R} = \frac{V \angle \theta}{R \angle 0^\circ} = \frac{70.71 \text{ V } \angle 0^\circ}{5 \Omega \angle 0^\circ} = 14.14 \text{ A } \angle 0^\circ$$
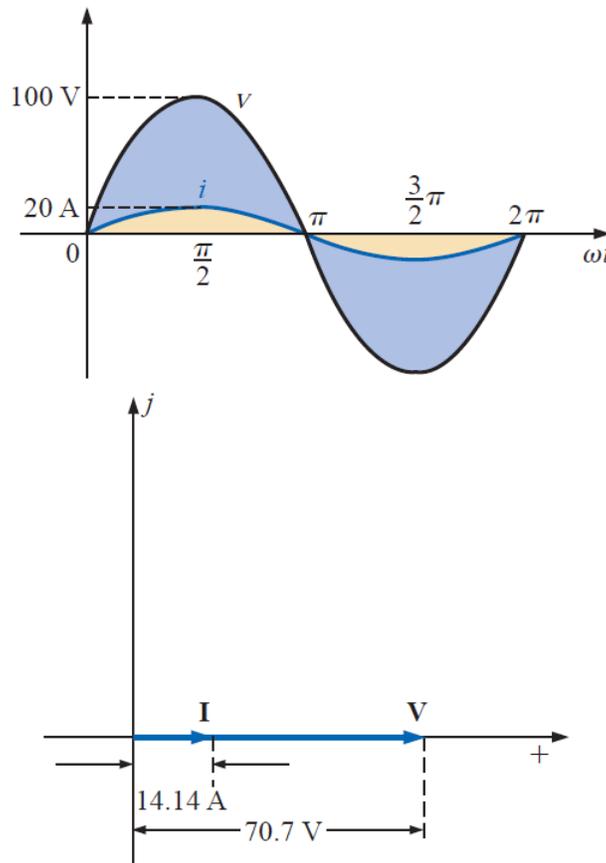
$$i = \sqrt{2}(14.14) \sin \omega t = \mathbf{20 \sin \omega t}$$



EXAMPLE: find the voltage v for the circuit. Sketch the waveforms of v and i .

$$i = 4 \sin(\omega t + 30^\circ)$$


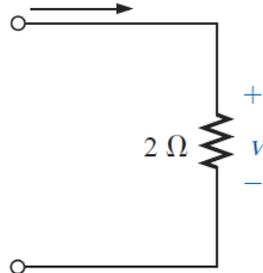


Solutions:


$$i = 4 \sin(\omega t + 30^\circ) \Rightarrow \text{phasor form } \mathbf{I} = 2.828 \text{ A } \angle 30^\circ$$

$$\mathbf{V} = \mathbf{I}Z_R = (I \angle \theta)(R \angle 0^\circ) = (2.828 \text{ A } \angle 30^\circ)(2 \Omega \angle 0^\circ) \\ = 5.656 \text{ V } \angle 30^\circ$$
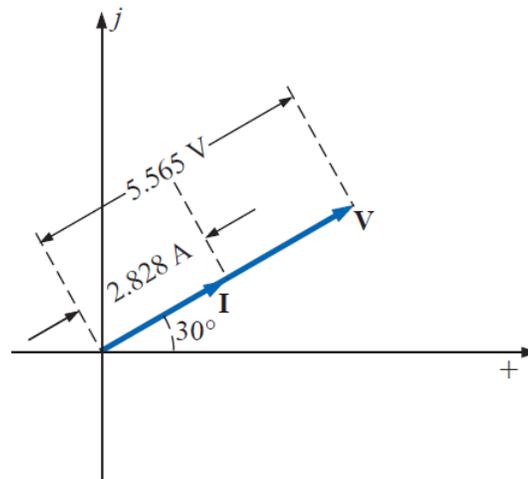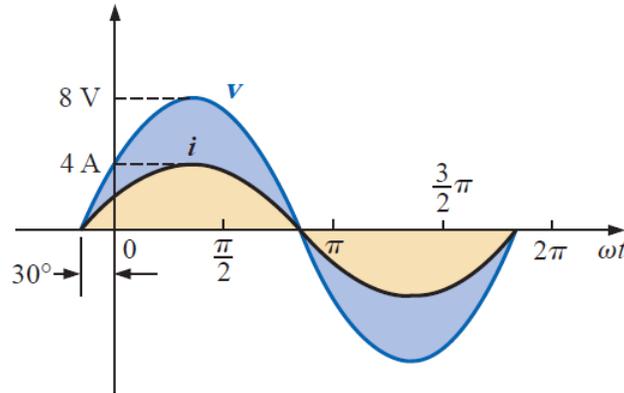
$$v = \sqrt{2}(5.656) \sin(\omega t + 30^\circ) = \mathbf{8.0 \sin(\omega t + 30^\circ)}$$




2) Inductive Reactance

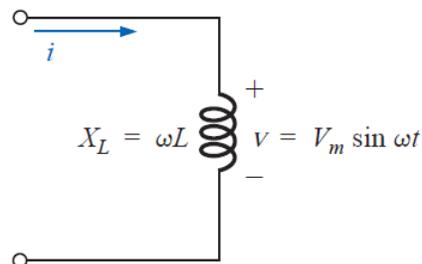

$$Z_L = X_L \angle 90^\circ$$

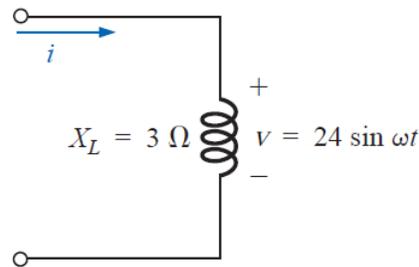EXAMPLE: find the current i for the circuit. Sketch the v and i curves.





Solutions:


$$v = 24 \sin \omega t \Rightarrow \text{phasor form } \mathbf{V} = 16.968 \text{ V } \angle 0^\circ$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_L} = \frac{V \angle \theta}{X_L \angle 90^\circ} = \frac{16.968 \text{ V } \angle 0^\circ}{3 \Omega \angle 90^\circ} = 5.656 \text{ A } \angle -90^\circ$$
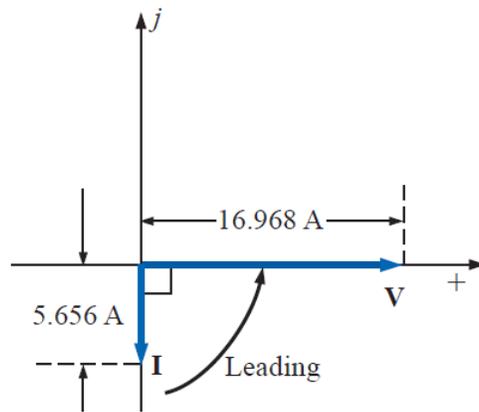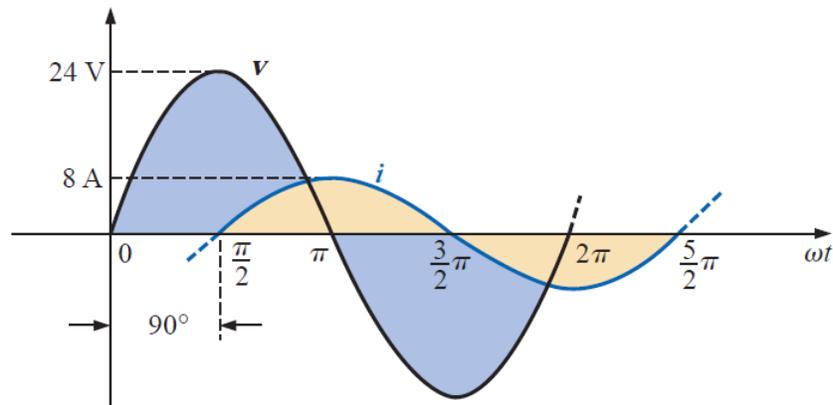
$$i = \sqrt{2}(5.656) \sin(\omega t - 90^\circ) = \mathbf{8.0 \sin(\omega t - 90^\circ)}$$




3) Capacitive Reactance

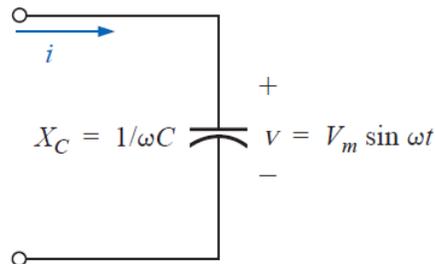

$$\mathbf{Z}_C = X_C \angle -90^\circ$$

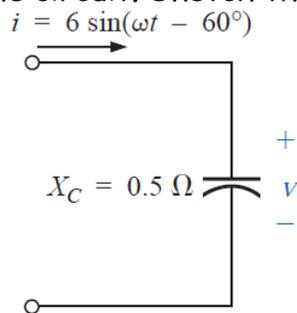EXAMPLE: find the voltage v for the circuit. Sketch the v and i curves.





Solutions:

$$i = 6 \sin(\omega t - 60^\circ) \Rightarrow \text{phasor notation } \mathbf{I} = 4.242 \text{ A } \angle -60^\circ$$

$$\mathbf{V} = \mathbf{I} \mathbf{Z}_C = (I \angle \theta)(X_C \angle -90^\circ) = (4.242 \text{ A } \angle -60^\circ)(0.5 \Omega \angle -90^\circ) \\ = 2.121 \text{ V } \angle -150^\circ$$
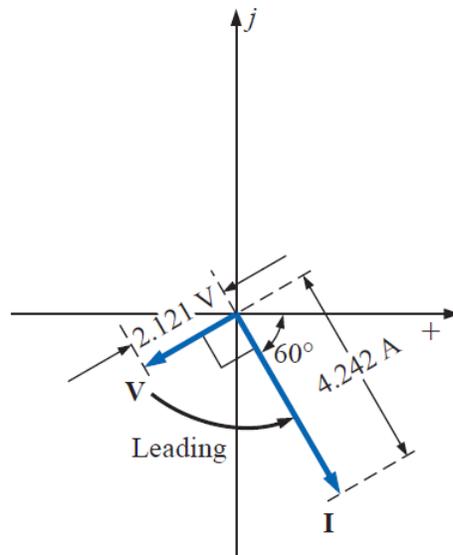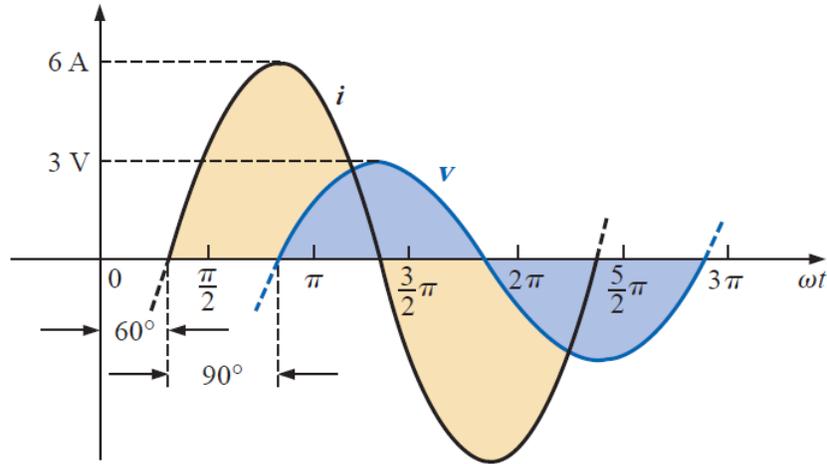
$$\text{and } v = \sqrt{2}(2.121) \sin(\omega t - 150^\circ) = 3.0 \sin(\omega t - 150^\circ)$$





الوحدة السابعة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة


يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

SERIES CONFIGURATION

موضوعات المحاضرة
الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
● جهاز حاسوب ● جهاز عرض ● سبورة ● اوراق واقلام	● نشاط التعارف ● محاضرة ● مناقشة ● سؤال وجواب	27


SERIES CONFIGURATION

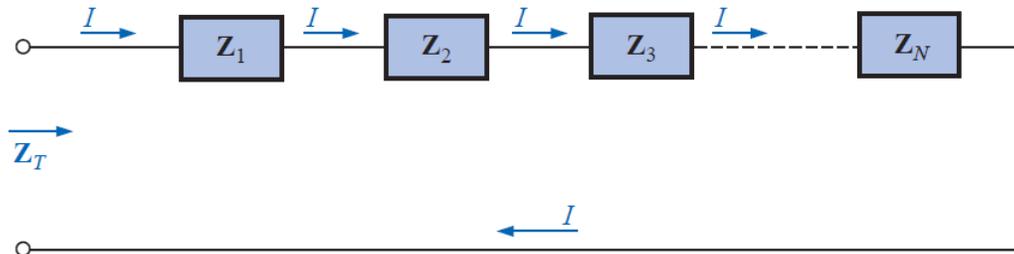

$$Z_T = Z_1 + Z_2 + Z_3 + \dots + Z_N$$


1) R-L

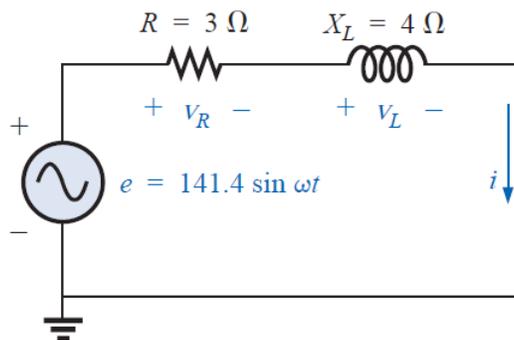EXAMPLE: Determine the input impedance to the series network and find i , V_R, V_L . Draw the impedance diagram.



Solutions:
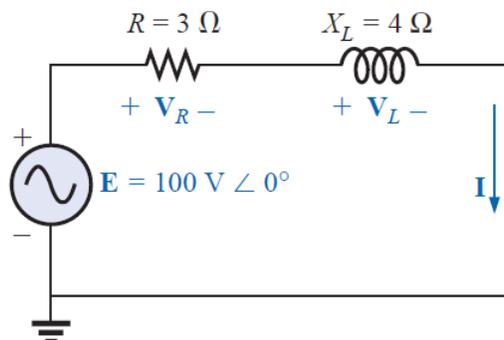
$$e = 141.4 \sin \omega t \Rightarrow \mathbf{E} = 100 \text{ V } \angle 0^\circ$$




$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 3 \Omega \angle 0^\circ + 4 \Omega \angle 90^\circ = 3 \Omega + j4 \Omega$$

$$\mathbf{Z}_T = 5 \Omega \angle 53.13^\circ$$

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 20 \text{ A} \angle -53.13^\circ$$


$$\begin{aligned} \mathbf{V}_R &= \mathbf{I}\mathbf{Z}_R = (20 \text{ A} \angle -53.13^\circ)(3 \Omega \angle 0^\circ) \\ &= 60 \text{ V} \angle -53.13^\circ \end{aligned}$$
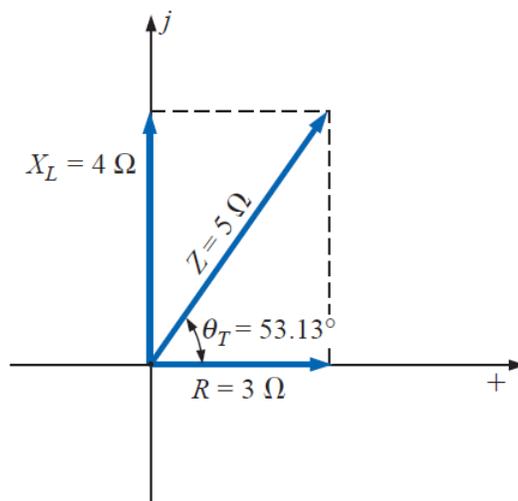
$$\begin{aligned} \mathbf{V}_L &= \mathbf{I}\mathbf{Z}_L = (20 \text{ A} \angle -53.13^\circ)(4 \Omega \angle 90^\circ) \\ &= 80 \text{ V} \angle 36.87^\circ \end{aligned}$$




2) R-C

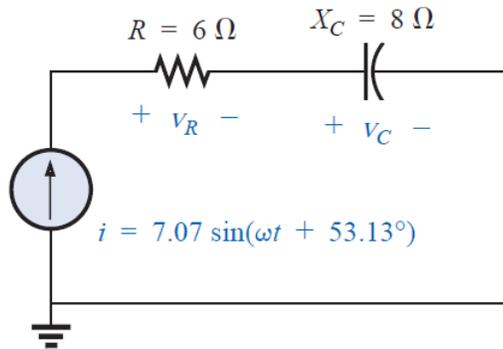EXAMPLE: Determine the input impedance to the series network and find E , V_R , V_C . Draw the impedance diagram.



Solutions:
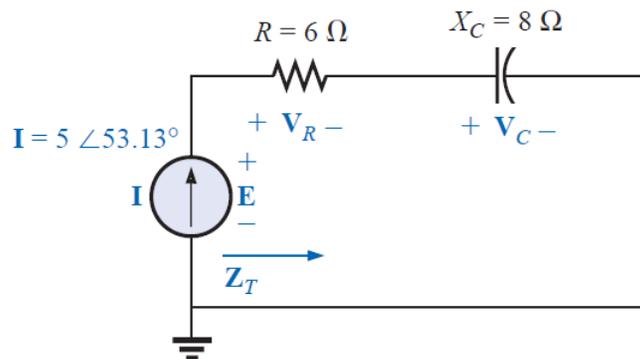
$$i = 7.07 \sin(\omega t + 53.13^\circ) \Rightarrow \mathbf{I} = 5 \text{ A } \angle 53.13^\circ$$




$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 6 \Omega \angle 0^\circ + 8 \Omega \angle -90^\circ = 6 \Omega - j8 \Omega$$

$$\mathbf{Z}_T = 10 \Omega \angle -53.13^\circ$$

$$\mathbf{E} = \mathbf{I}\mathbf{Z}_T = (5 \text{ A } \angle 53.13^\circ)(10 \Omega \angle -53.13^\circ) = 50 \text{ V } \angle 0^\circ$$


$$\begin{aligned} \mathbf{V}_R &= \mathbf{I}\mathbf{Z}_R = (I \angle \theta)(R \angle 0^\circ) = (5 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) \\ &= 30 \text{ V } \angle 53.13^\circ \end{aligned}$$
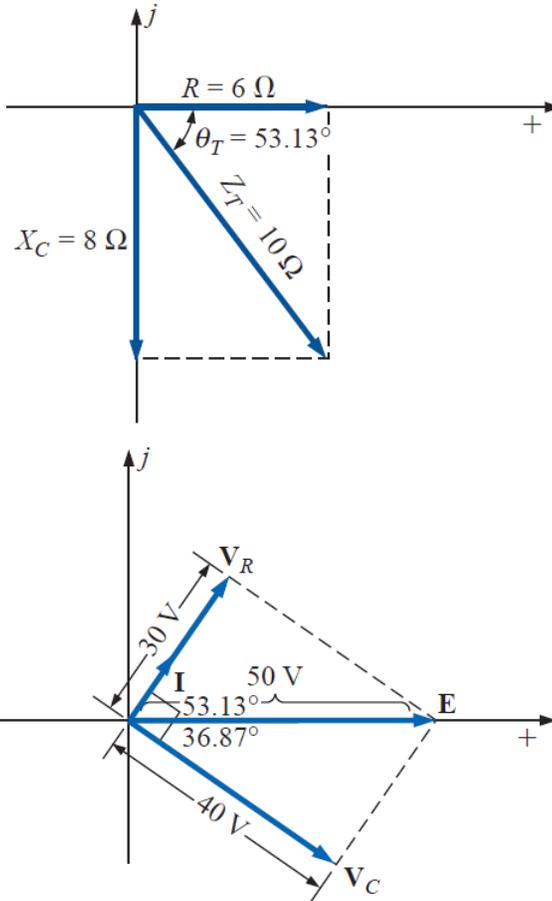
$$\begin{aligned} \mathbf{V}_C &= \mathbf{I}\mathbf{Z}_C = (I \angle \theta)(X_C \angle -90^\circ) = (5 \text{ A } \angle 53.13^\circ)(8 \Omega \angle -90^\circ) \\ &= 40 \text{ V } \angle -36.87^\circ \end{aligned}$$



3) R-L-C

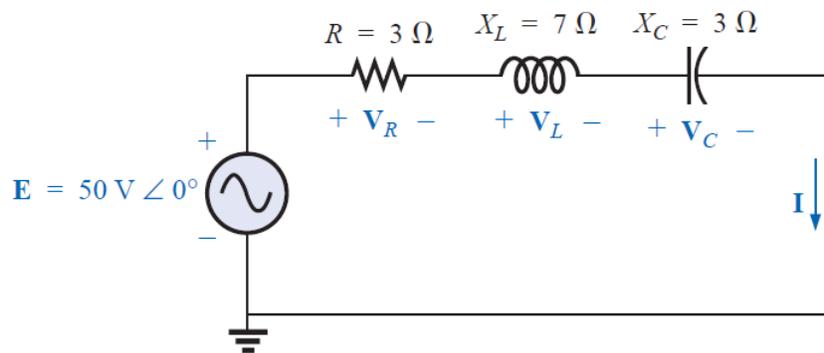EXAMPLE: Determine the input impedance to the series network and find i , V_r , V_c , V_L . Draw the impedance diagram.



Solutions:

$$\begin{aligned} Z_T &= Z_1 + Z_2 + Z_3 = R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 3 \Omega + j 7 \Omega - j 3 \Omega = 3 \Omega + j 4 \Omega \end{aligned}$$



$$Z_T = 5 \Omega \angle 53.13^\circ$$

$$I = \frac{E}{Z_T} = \frac{50 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 10 \text{ A} \angle -53.13^\circ$$


$$\begin{aligned} V_R &= \mathbf{I}Z_R = (I \angle \theta)(R \angle 0^\circ) = (10 \text{ A} \angle -53.13^\circ)(3 \Omega \angle 0^\circ) \\ &= 30 \text{ V} \angle -53.13^\circ \end{aligned}$$

$$\begin{aligned} V_L &= \mathbf{I}Z_L = (I \angle \theta)(X_L \angle 90^\circ) = (10 \text{ A} \angle -53.13^\circ)(7 \Omega \angle 90^\circ) \\ &= 70 \text{ V} \angle 36.87^\circ \end{aligned}$$
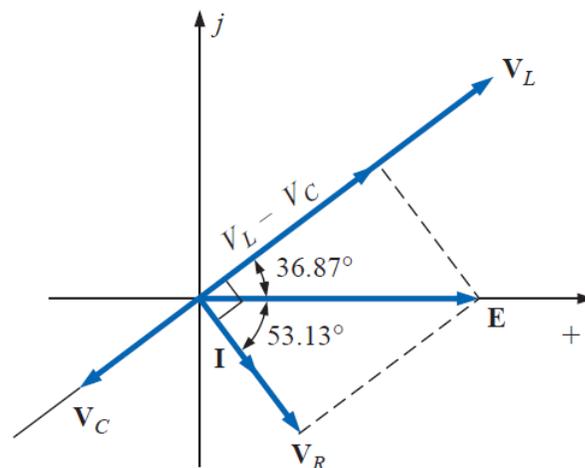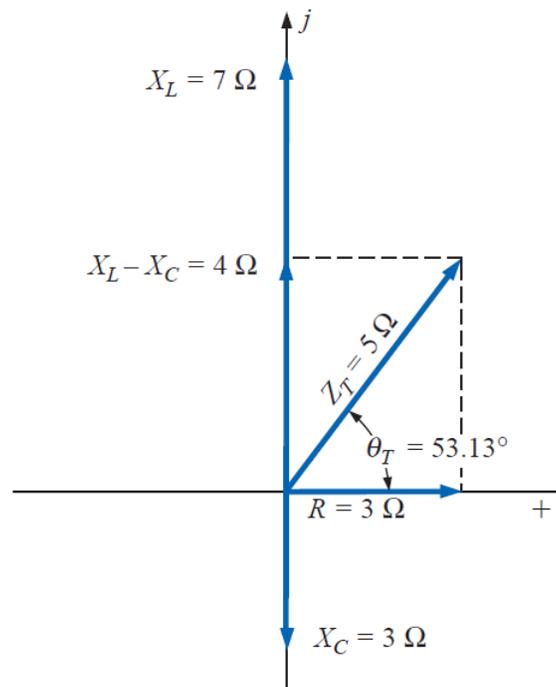
$$\begin{aligned} V_C &= \mathbf{I}Z_C = (I \angle \theta)(X_C \angle -90^\circ) = (10 \text{ A} \angle -53.13^\circ)(3 \Omega \angle -90^\circ) \\ &= 30 \text{ V} \angle -143.13^\circ \end{aligned}$$



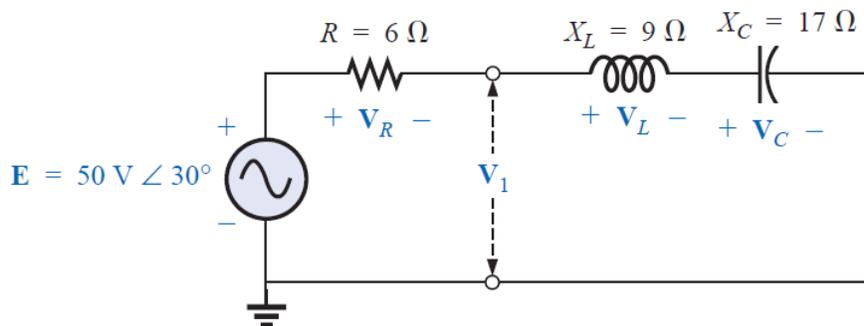EXAMPLE: Using the voltage divider rule, find the unknown voltages V_R , V_L , V_C , and V_1 for the circuit.



Solutions:

$$V_R = \frac{Z_R E}{Z_R + Z_L + Z_C} = \frac{(6 \Omega \angle 0^\circ)(50 \text{ V} \angle 30^\circ)}{6 \Omega \angle 0^\circ + 9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ}$$

$$= \frac{300 \angle 30^\circ}{6 + j9 - j17} = \frac{300 \angle 30^\circ}{6 - j8}$$

$$= \frac{300 \angle 30^\circ}{10 \angle -53.13^\circ} = 30 \text{ V} \angle 83.13^\circ$$

$$V_L = \frac{Z_L E}{Z_T} = \frac{(9 \Omega \angle 90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{450 \text{ V} \angle 120^\circ}{10 \angle -53.13^\circ}$$

$$= 45 \text{ V} \angle 173.13^\circ$$

$$V_C = \frac{Z_C E}{Z_T} = \frac{(17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{850 \text{ V} \angle -60^\circ}{10 \angle -53^\circ}$$


$$= 85 \text{ V} \angle -6.87^\circ$$

$$V_1 = \frac{(Z_L + Z_C)E}{Z_T} = \frac{(9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ}$$

$$= \frac{(8 \angle -90^\circ)(50 \angle 30^\circ)}{10 \angle -53.13^\circ}$$

$$= \frac{400 \angle -60^\circ}{10 \angle -53.13^\circ} = 40 \text{ V} \angle -6.87^\circ$$

PARALLEL ac CIRCUITS

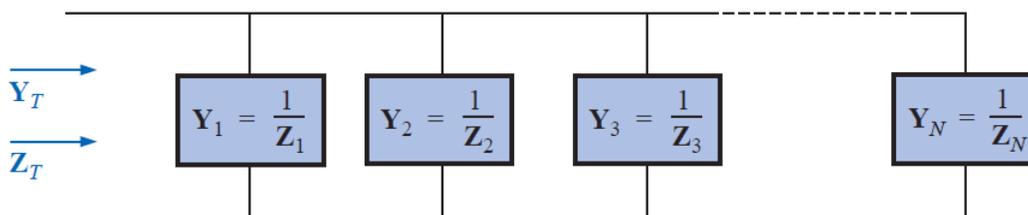

$$\mathbf{Y}_T = \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3 + \cdots + \mathbf{Y}_N$$


$$\frac{1}{\mathbf{Z}_T} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \cdots + \frac{1}{\mathbf{Z}_N}$$

For two impedances in parallel

$$\mathbf{Z}_T = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

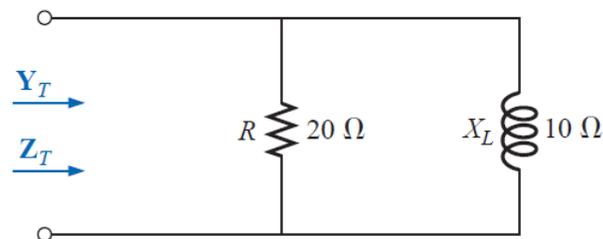EXAMPLE: For the network

- Find the admittance of each parallel branch.
- Determine the input admittance.
- Calculate the input impedance.
- Draw the admittance diagram.



Solutions:

$$\begin{aligned} \text{a. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{20 \Omega} \angle 0^\circ \\ &= 0.05 \text{ S} \angle 0^\circ = 0.05 \text{ S} + j 0 \end{aligned}$$

$$\begin{aligned} \mathbf{Y}_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10 \Omega} \angle -90^\circ \\ &= 0.1 \text{ S} \angle -90^\circ = 0 - j 0.1 \text{ S} \end{aligned}$$


$$\begin{aligned} \text{b. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L = (0.05 \text{ S} + j 0) + (0 - j 0.1 \text{ S}) \\ &= 0.05 \text{ S} - j 0.1 \text{ S} = G - j B_L \end{aligned}$$

$$\begin{aligned} \text{c. } \mathbf{Z}_T &= \frac{1}{\mathbf{Y}_T} = \frac{1}{0.05 \text{ S} - j 0.1 \text{ S}} = \frac{1}{0.112 \text{ S} \angle -63.43^\circ} \\ &= 8.93 \Omega \angle 63.43^\circ \end{aligned}$$


Or

$$\begin{aligned} \mathbf{Z}_T &= \frac{\mathbf{Z}_R \mathbf{Z}_L}{\mathbf{Z}_R + \mathbf{Z}_L} = \frac{(20 \Omega \angle 0^\circ)(10 \Omega \angle 90^\circ)}{20 \Omega + j 10 \Omega} \\ &= \frac{200 \Omega \angle 90^\circ}{22.36 \angle 26.57^\circ} = 8.93 \Omega \angle 63.43^\circ \end{aligned}$$

d.

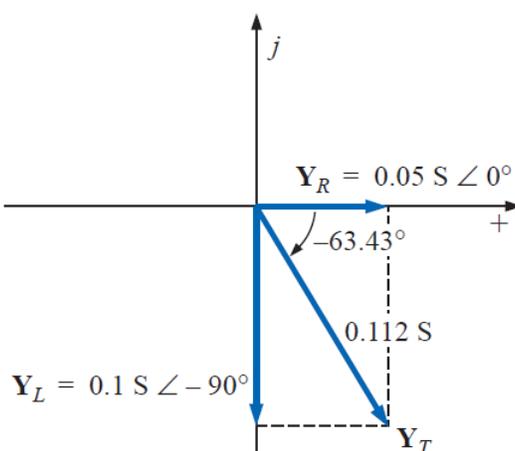

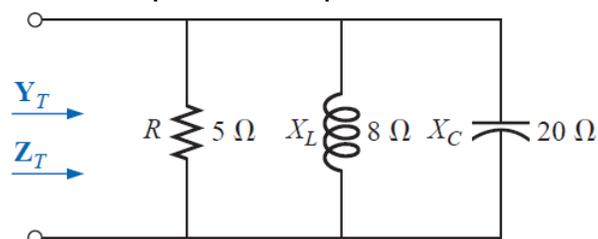EXAMPLE: Repeat the above Example for the parallel network.



Solutions:

$$\begin{aligned} \text{a. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{5 \Omega} \angle 0^\circ \\ &= 0.2 \text{ S} \angle 0^\circ = 0.2 \text{ S} + j 0 \end{aligned}$$

$$Y_L = B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{8 \Omega} \angle -90^\circ$$

$$= 0.125 \text{ S} \angle -90^\circ = 0 - j 0.125 \text{ S}$$

$$Y_C = B_C \angle 90^\circ = \frac{1}{X_C} \angle 90^\circ = \frac{1}{20 \Omega} \angle 90^\circ$$

$$= 0.050 \text{ S} \angle +90^\circ = 0 + j 0.050 \text{ S}$$


b. $Y_T = Y_R + Y_L + Y_C$

$$= (0.2 \text{ S} + j 0) + (0 - j 0.125 \text{ S}) + (0 + j 0.050 \text{ S})$$

$$= 0.2 \text{ S} - j 0.075 \text{ S} = 0.2136 \text{ S} \angle -20.56^\circ$$

c. $Z_T = \frac{1}{0.2136 \text{ S} \angle -20.56^\circ} = 4.68 \Omega \angle 20.56^\circ$

d.

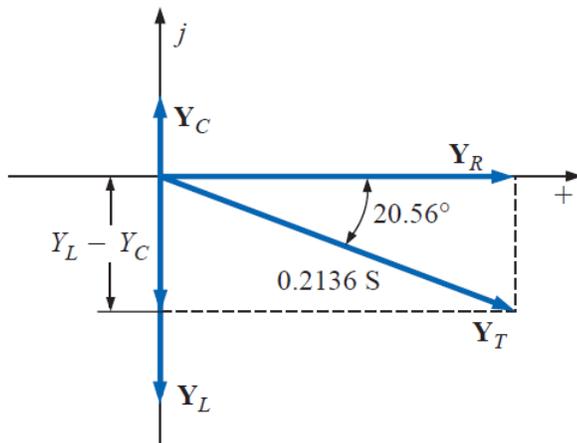



الوحدة الثامنة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

PARALLEL ac NETWORKS


موضوعات المحاضرة
الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	28


PARALLEL ac NETWORKS

1) R-L

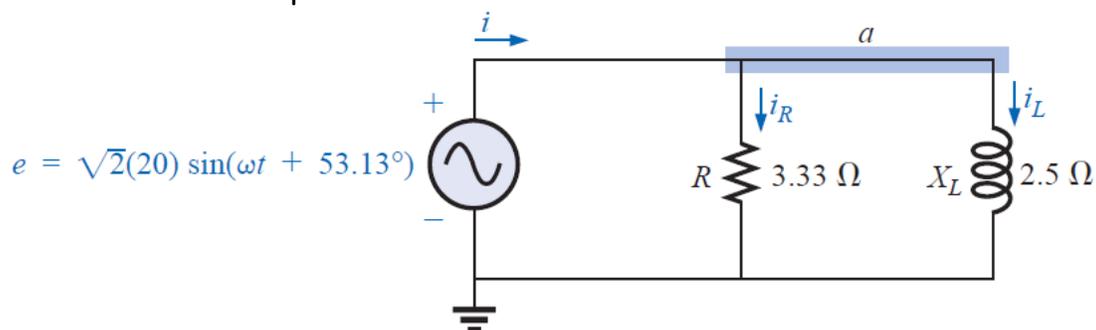EXAMPLE: find the total impedance and the current in each branch for the network.



Solutions:

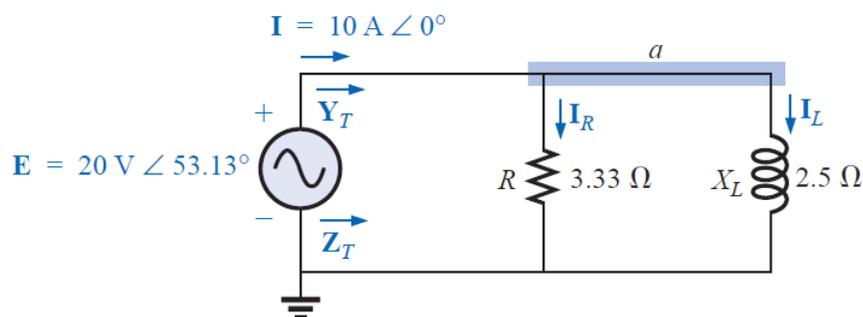

$$Y_T = Y_R + Y_L$$

$$= G \angle 0^\circ + B_L \angle -90^\circ = \frac{1}{3.33 \Omega} \angle 0^\circ + \frac{1}{2.5 \Omega} \angle -90^\circ$$

$$= 0.3 \text{ S } \angle 0^\circ + 0.4 \text{ S } \angle -90^\circ = 0.3 \text{ S} - j 0.4 \text{ S}$$


$$= \mathbf{0.5 \text{ S } \angle -53.13^\circ}$$

$$Z_T = \frac{1}{Y_T} = \frac{1}{0.5 \text{ S } \angle -53.13^\circ} = \mathbf{2 \Omega \angle 53.13^\circ}$$

Or

$$Z_T = \frac{Z_R Z_L}{Z_R + Z_L} = \frac{(3.33 \Omega \angle 0^\circ)(2.5 \Omega \angle 90^\circ)}{3.33 \Omega \angle 0^\circ + 2.5 \Omega \angle 90^\circ}$$

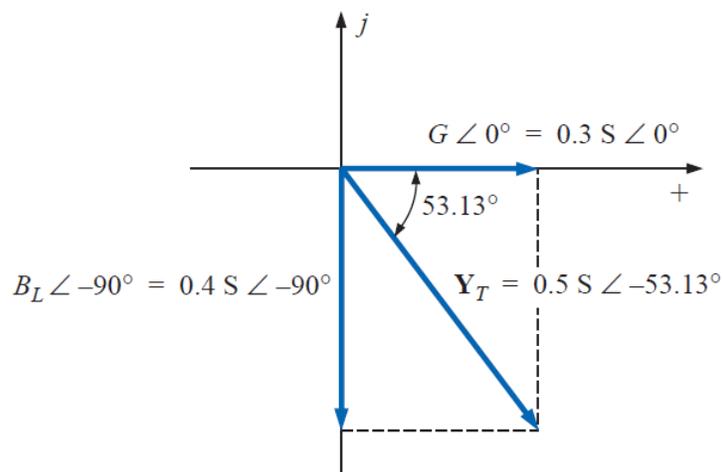
$$= \frac{8.325 \angle 90^\circ}{4.164 \angle 36.87^\circ} = \mathbf{2 \Omega \angle 53.13^\circ}$$



$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \mathbf{E}\mathbf{Y}_T = (20 \text{ V } \angle 53.13^\circ)(0.5 \text{ S } \angle -53.13^\circ) = \mathbf{10 \text{ A } } \angle 0^\circ$$


$$\begin{aligned} \mathbf{I}_R &= \frac{E \angle \theta}{R \angle 0^\circ} = (E \angle \theta)(G \angle 0^\circ) \\ &= (20 \text{ V } \angle 53.13^\circ)(0.3 \text{ S } \angle 0^\circ) = \mathbf{6 \text{ A } } \angle 53.13^\circ \end{aligned}$$
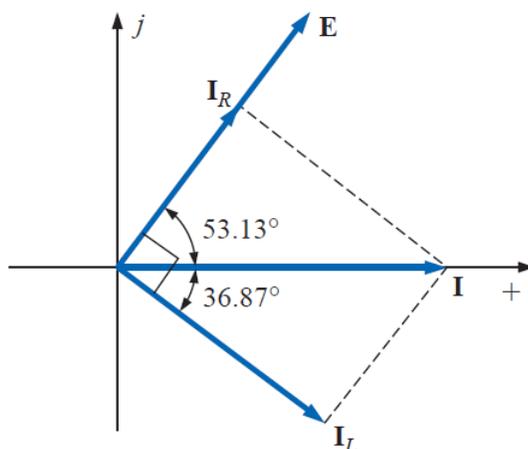
$$\begin{aligned} \mathbf{I}_L &= \frac{E \angle \theta}{X_L \angle 90^\circ} = (E \angle \theta)(B_L \angle -90^\circ) \\ &= (20 \text{ V } \angle 53.13^\circ)(0.4 \text{ S } \angle -90^\circ) \\ &= \mathbf{8 \text{ A } } \angle -36.87^\circ \end{aligned}$$



2) R-C

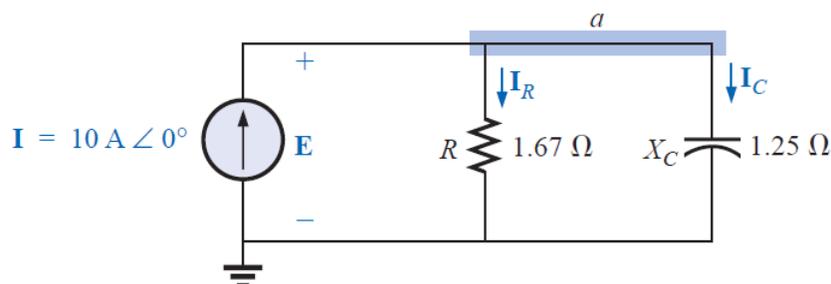EXAMPLE: find the total impedance and the current in each branch for the network.



Solutions:

$$Y_T = Y_R + Y_C = G \angle 0^\circ + B_C \angle 90^\circ = \frac{1}{1.67 \Omega} \angle 0^\circ + \frac{1}{1.25 \Omega} \angle 90^\circ$$


$$= 0.6 \text{ S} \angle 0^\circ + 0.8 \text{ S} \angle 90^\circ = 0.6 \text{ S} + j 0.8 \text{ S} = \mathbf{1.0 \text{ S} \angle 53.13^\circ}$$

$$Z_T = \frac{1}{Y_T} = \frac{1}{1.0 \text{ S} \angle 53.13^\circ} = \mathbf{1 \Omega \angle -53.13^\circ}$$

Or

$$Z_T = \frac{Z_R Z_C}{Z_R + Z_C} = \frac{(1.67 \Omega \angle 0^\circ)(1.25 \Omega \angle -90^\circ)}{1.67 \Omega \angle 0^\circ + 1.25 \Omega \angle -90^\circ}$$

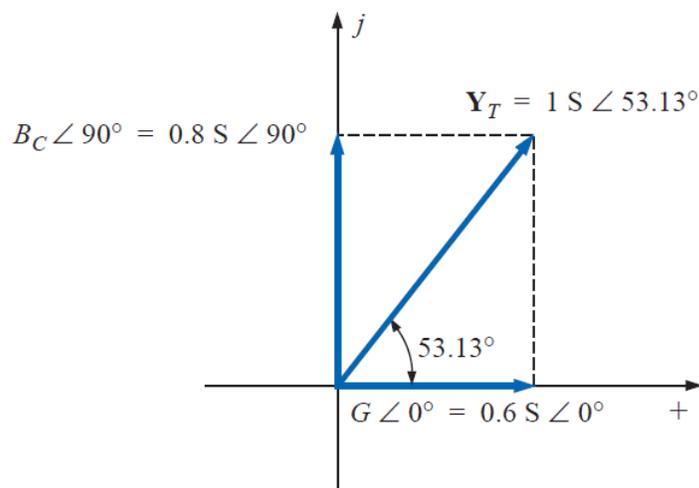
$$= \frac{2.09 \angle -90^\circ}{2.09 \angle -36.81^\circ} = \mathbf{1 \Omega \angle -53.19^\circ}$$



$$E = I Z_T = \frac{I}{Y_T} = \frac{10 \text{ A} \angle 0^\circ}{1 \text{ S} \angle 53.13^\circ} = \mathbf{10 \text{ V} \angle -53.13^\circ}$$


$$\begin{aligned} \mathbf{I}_R &= (E \angle \theta)(G \angle 0^\circ) \\ &= (10 \text{ V} \angle -53.13^\circ)(0.6 \text{ S} \angle 0^\circ) = 6 \text{ A} \angle -53.13^\circ \end{aligned}$$
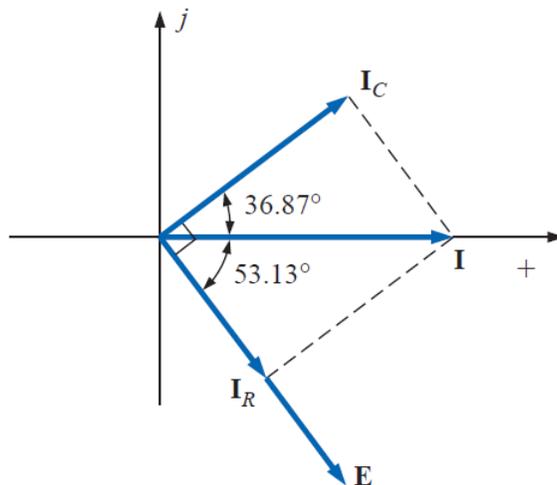
$$\begin{aligned} \mathbf{I}_C &= (E \angle \theta)(B_C \angle 90^\circ) \\ &= (10 \text{ V} \angle -53.13^\circ)(0.8 \text{ S} \angle 90^\circ) = 8 \text{ A} \angle 36.87^\circ \end{aligned}$$




3) R-L-C

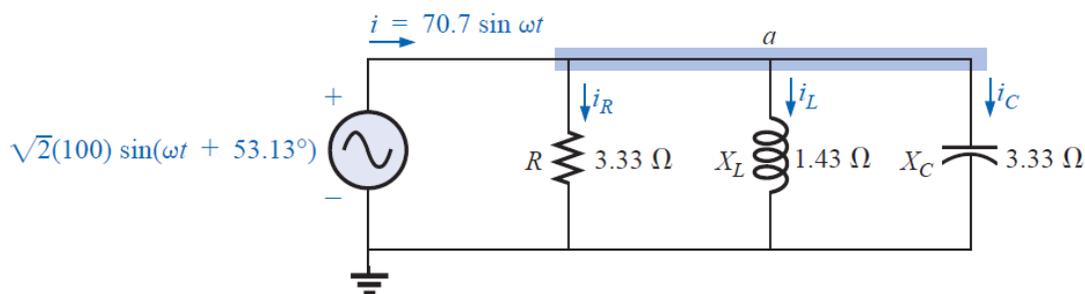EXAMPLE: find the total impedance and the current in each branch for the network.




Solutions:

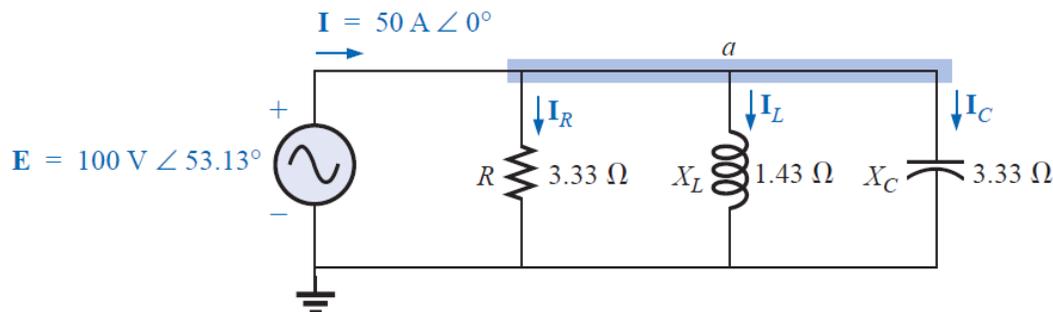

$$\begin{aligned} \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C = G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle 90^\circ \\ &= \frac{1}{3.33 \Omega} \angle 0^\circ + \frac{1}{1.43 \Omega} \angle -90^\circ + \frac{1}{3.33 \Omega} \angle 90^\circ \\ &= 0.3 \text{ S} \angle 0^\circ + 0.7 \text{ S} \angle -90^\circ + 0.3 \text{ S} \angle 90^\circ \\ &= 0.3 \text{ S} - j 0.7 \text{ S} + j 0.3 \text{ S} \\ &= 0.3 \text{ S} - j 0.4 \text{ S} = \mathbf{0.5 \text{ S} \angle -53.13^\circ} \end{aligned}$$

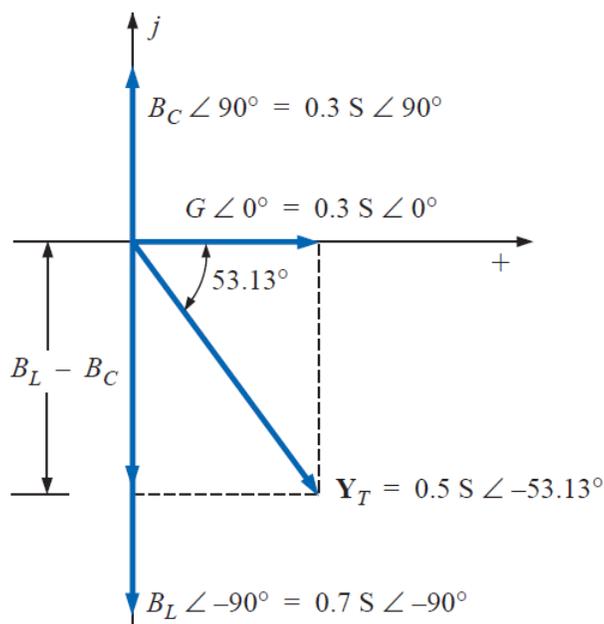
$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.5 \text{ S} \angle -53.13^\circ} = \mathbf{2 \Omega \angle 53.13^\circ}$$




$$\begin{aligned} \mathbf{I}_R &= (E \angle \theta)(G \angle 0^\circ) \\ &= (100 \text{ V} \angle 53.13^\circ)(0.3 \text{ S} \angle 0^\circ) = \mathbf{30 \text{ A} \angle 53.13^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_L &= (E \angle \theta)(B_L \angle -90^\circ) \\ &= (100 \text{ V} \angle 53.13^\circ)(0.7 \text{ S} \angle -90^\circ) = \mathbf{70 \text{ A} \angle -36.87^\circ} \end{aligned}$$
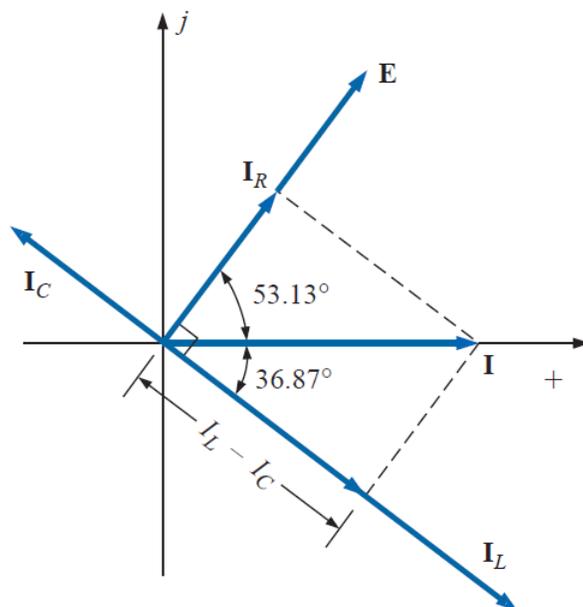
$$\begin{aligned} \mathbf{I}_C &= (E \angle \theta)(B_C \angle 90^\circ) \\ &= (100 \text{ V} \angle 53.13^\circ)(0.3 \text{ S} \angle +90^\circ) = \mathbf{30 \text{ A} \angle 143.13^\circ} \end{aligned}$$



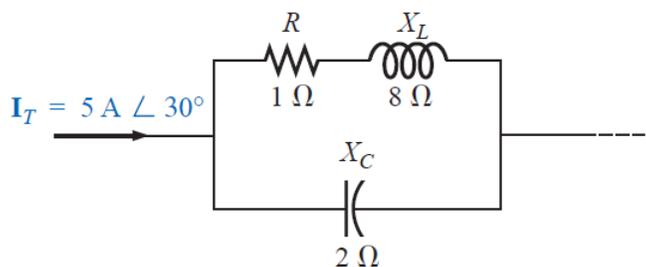EXAMPLE: Using the current divider rule, find the current through each parallel branch.



Solutions:

$$\begin{aligned} I_{R-L} &= \frac{Z_C I_T}{Z_C + Z_{R-L}} = \frac{(2 \Omega \angle -90^\circ)(5 \text{ A} \angle 30^\circ)}{-j 2 \Omega + 1 \Omega + j 8 \Omega} = \frac{10 \text{ A} \angle -60^\circ}{1 + j 6} \\ &= \frac{10 \text{ A} \angle -60^\circ}{6.083 \angle 80.54^\circ} \cong 1.644 \text{ A} \angle -140.54^\circ \end{aligned}$$



$$\begin{aligned} \mathbf{I}_C &= \frac{\mathbf{Z}_{R-L} \mathbf{I}_T}{\mathbf{Z}_{R-L} + \mathbf{Z}_C} = \frac{(1 \Omega + j 8 \Omega)(5 \text{ A } \angle 30^\circ)}{6.08 \Omega \angle 80.54^\circ} \\ &= \frac{(8.06 \angle 82.87^\circ)(5 \text{ A } \angle 30^\circ)}{6.08 \angle 80.54^\circ} = \frac{40.30 \text{ A } \angle 112.87^\circ}{6.083 \angle 80.54^\circ} \\ &= \mathbf{6.625 \text{ A } \angle 32.33^\circ} \end{aligned}$$



الوحدة التاسعة والعشرون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Series-Parallel ac Networks

موضوعات المحاضرة

Examples


الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
<ul style="list-style-type: none">● جهاز حاسوب● جهاز عرض● سبورة● اوراق واقلام	<ul style="list-style-type: none">● نشاط التعارف● محاضرة● مناقشة● سؤال وجواب	29

Series-Parallel ac Networks

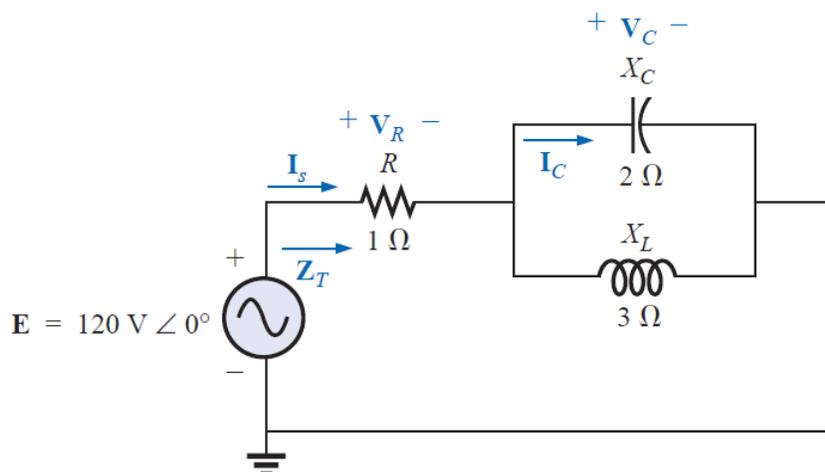
EXAMPLE: For the network

- Calculate Z_T .
- Determine I_s .
- Calculate V_R and V_C .
- Find I_C .



Solutions:

a)

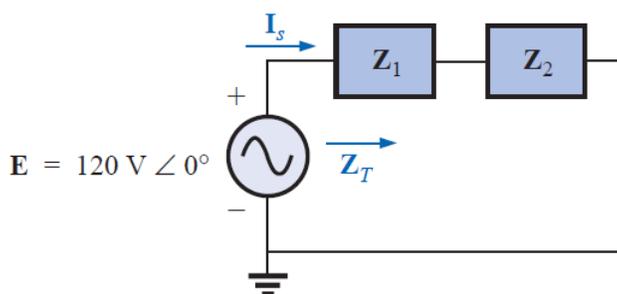

$$Z_T = Z_1 + Z_2$$

$$Z_1 = R \angle 0^\circ = 1 \Omega \angle 0^\circ$$

$$Z_2 = Z_C \parallel Z_L = \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(2 \Omega \angle -90^\circ)(3 \Omega \angle 90^\circ)}{-j2 \Omega + j3 \Omega}$$

$$= \frac{6 \Omega \angle 0^\circ}{j1} = \frac{6 \Omega \angle 0^\circ}{1 \angle 90^\circ} = 6 \Omega \angle -90^\circ$$

$$Z_T = Z_1 + Z_2 = 1 \Omega - j6 \Omega = 6.08 \Omega \angle -80.54^\circ$$

b)

$$I_s = \frac{E}{Z_T} = \frac{120 \text{ V} \angle 0^\circ}{6.08 \Omega \angle -80.54^\circ} = 19.74 \text{ A} \angle 80.54^\circ$$

c)

$$V_R = I_s Z_1 = (19.74 \text{ A} \angle 80.54^\circ)(1 \Omega \angle 0^\circ) = 19.74 \text{ V} \angle 80.54^\circ$$


$$V_C = I_s Z_2 = (19.74 \text{ A} \angle 80.54^\circ)(6 \Omega \angle -90^\circ) \\ = 118.44 \text{ V} \angle -9.46^\circ$$

d)

$$I_C = \frac{V_C}{Z_C} = \frac{118.44 \text{ V} \angle -9.46^\circ}{2 \Omega \angle -90^\circ} = 59.22 \text{ A} \angle 80.54^\circ$$

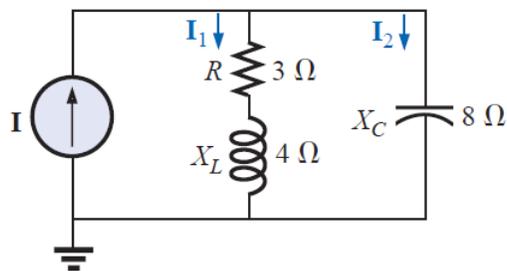
EXAMPLE: For the network

- If I is $50 \text{ A} \angle 30^\circ$, calculate I_1 using the current divider rule.
- Repeat part (a) for I_2 .
- Verify Kirchhoff's current law at one node.



Solutions:

a)

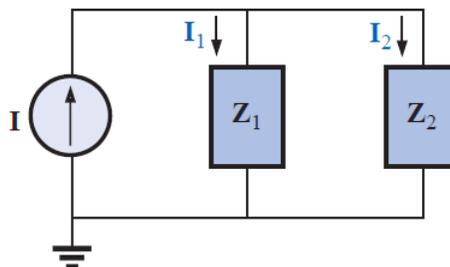

$$\mathbf{Z}_1 = R + jX_L = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ$$

$$\mathbf{Z}_2 = -jX_C = -j8 \Omega = 8 \Omega \angle -90^\circ$$

$$\begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{Z}_2 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(8 \Omega \angle -90^\circ)(50 \text{ A} \angle 30^\circ)}{(-j8 \Omega) + (3 \Omega + j4 \Omega)} = \frac{400 \angle -60^\circ}{3 - j4} \\ &= \frac{400 \angle -60^\circ}{5 \angle -53.13^\circ} = \mathbf{80 \text{ A} \angle -6.87^\circ} \end{aligned}$$

b)

$$\begin{aligned} \mathbf{I}_2 &= \frac{\mathbf{Z}_1 \mathbf{I}}{\mathbf{Z}_2 + \mathbf{Z}_1} = \frac{(5 \Omega \angle 53.13^\circ)(50 \text{ A} \angle 30^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{250 \angle 83.13^\circ}{5 \angle -53.13^\circ} \\ &= \mathbf{50 \text{ A} \angle 136.26^\circ} \end{aligned}$$

c)


$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$$

$$\begin{aligned} 50 \text{ A} \angle 30^\circ &= 80 \text{ A} \angle -6.87^\circ + 50 \text{ A} \angle 136.26^\circ \\ &= (79.43 - j9.57) + (-36.12 + j34.57) \\ &= 43.31 + j25.0 \end{aligned}$$

$$50 \text{ A} \angle 30^\circ = 50 \text{ A} \angle 30^\circ \quad (\text{checks})$$

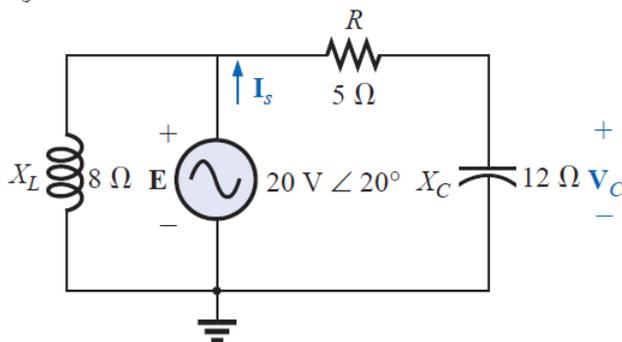
EXAMPLE: For the network

- Calculate the voltage \mathbf{V}_C using the voltage divider rule.
- Calculate the current \mathbf{I}_s .



Solutions:

a)

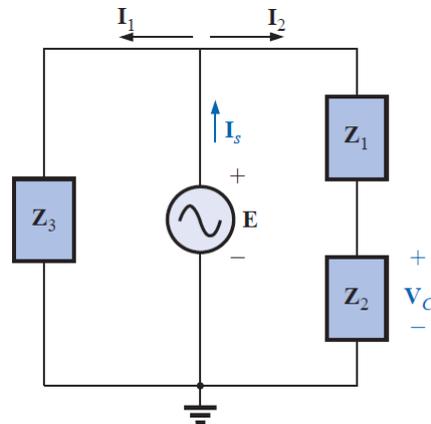

$$V_c = \frac{Z_2 E}{Z_1 + Z_2} = \frac{(12 \Omega \angle -90^\circ)(20 \text{ V} \angle 20^\circ)}{5 \Omega - j 12 \Omega} = \frac{240 \text{ V} \angle -70^\circ}{13 \angle -67.38^\circ} = 18.46 \text{ V} \angle -2.62^\circ$$

b)

$$I_1 = \frac{E}{Z_3} = \frac{20 \text{ V} \angle 20^\circ}{8 \Omega \angle 90^\circ} = 2.5 \text{ A} \angle -70^\circ$$

$$I_2 = \frac{E}{Z_1 + Z_2} = \frac{20 \text{ V} \angle 20^\circ}{13 \Omega \angle -67.38^\circ} = 1.54 \text{ A} \angle 87.38^\circ$$

$$I_s = I_1 + I_2 = 2.5 \text{ A} \angle -70^\circ + 1.54 \text{ A} \angle 87.38^\circ = (0.86 - j 2.35) + (0.07 + j 1.54)$$

$$I_s = 0.93 - j 0.81 = 1.23 \text{ A} \angle -41.05^\circ$$



الوحدة الثلاثون- الزمن: 90 دقيقة

أهداف المحاضرة

يتوقع في نهاية الجلسة أن يكون الطالب قادراً على:

Methods of Analysis (ac)

Power (ac)

APPARENT POWER

موضوعات المحاضرة


Examples

الأساليب والأنشطة والوسائل التعليمية

الوسائل التعليمية	الأساليب والأنشطة التعليمية	م
• جهاز حاسوب • جهاز عرض • سبورة • اوراق واقلام	• نشاط التعارف • محاضرة • مناقشة • سؤال وجواب	30

Methods of Analysis (ac)

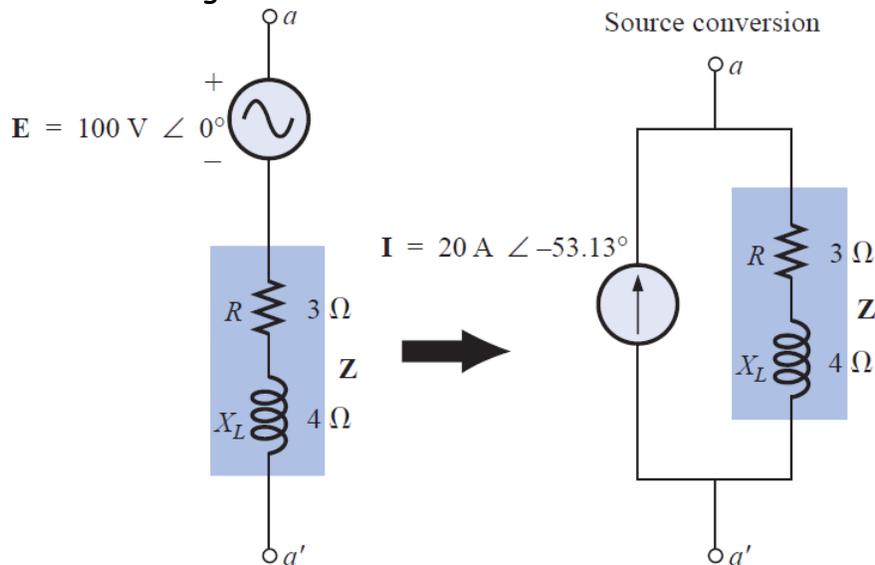
EXAMPLE: Convert the voltage source to a current source.



Solutions:

$$\begin{aligned}
 \mathbf{I} &= \frac{\mathbf{E}}{\mathbf{Z}} = \frac{100 \text{ V } \angle 0^\circ}{5 \Omega \angle 53.13^\circ} \\
 &= 20 \text{ A } \angle -53.13^\circ
 \end{aligned}$$

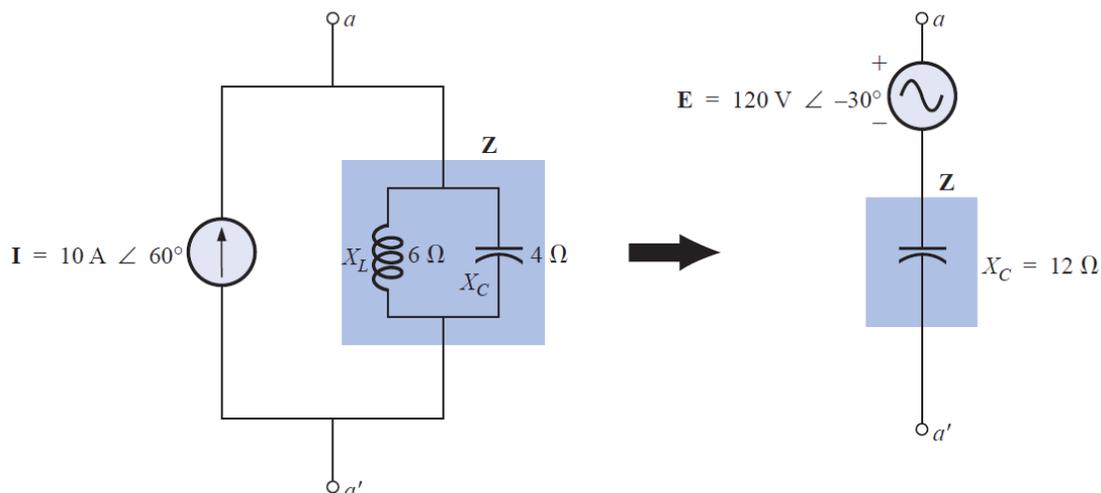
EXAMPLE: Convert the current source to a voltage source.




Solutions:

$$\begin{aligned}
 Z &= \frac{Z_C Z_L}{Z_C + Z_L} = \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-j X_C + j X_L} \\
 &= \frac{(4 \Omega \angle -90^\circ)(6 \Omega \angle 90^\circ)}{-j 4 \Omega + j 6 \Omega} = \frac{24 \Omega \angle 0^\circ}{2 \angle 90^\circ} \\
 &= 12 \Omega \angle -90^\circ \quad [\text{Fig. 17.7(b)}] \\
 E &= IZ = (10 \text{ A} \angle 60^\circ)(12 \Omega \angle -90^\circ) \\
 &= 120 \text{ V} \angle -30^\circ \quad [\text{Fig. 17.7(b)}]
 \end{aligned}$$

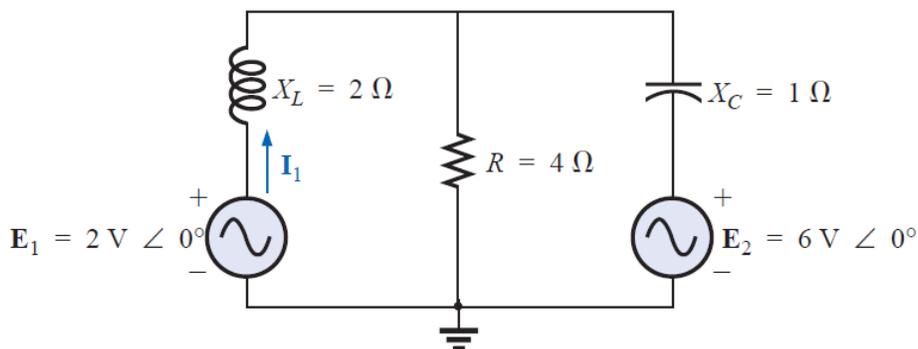EXAMPLE: Using the general approach to mesh analysis, find the current I_1 .



Solutions:

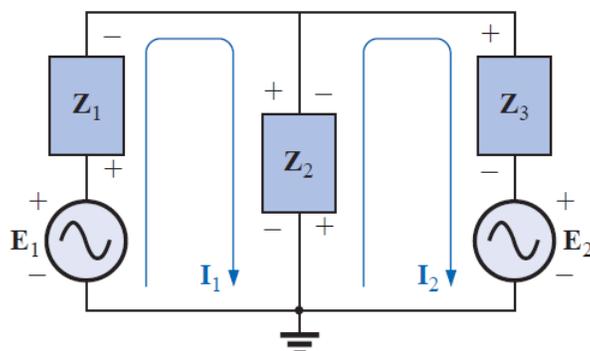

$$Z_1 = +j X_L = +j 2 \Omega \quad E_1 = 2 \text{ V } \angle 0^\circ$$

$$Z_2 = R = 4 \Omega \quad E_2 = 6 \text{ V } \angle 0^\circ$$

$$Z_3 = -j X_C = -j 1 \Omega$$

$$I_1(Z_1 + Z_2) - I_2 Z_2 = E_1$$


$$I_2(Z_2 + Z_3) - I_1 Z_2 = -E_2$$

$$\begin{array}{r} I_1(Z_1 + Z_2) - I_2 Z_2 = E_1 \\ -I_1 Z_2 + I_2(Z_2 + Z_3) = -E_2 \end{array}$$

$$\begin{aligned} I_1 &= \frac{\begin{vmatrix} E_1 & -Z_2 \\ -E_2 & Z_2 + Z_3 \end{vmatrix}}{\begin{vmatrix} Z_1 + Z_2 & -Z_2 \\ -Z_2 & Z_2 + Z_3 \end{vmatrix}} \\ &= \frac{E_1(Z_2 + Z_3) - E_2(Z_2)}{(Z_1 + Z_2)(Z_2 + Z_3) - (Z_2)^2} \\ &= \frac{(E_1 - E_2)Z_2 + E_1 Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3} \end{aligned}$$

$$\begin{aligned} I_1 &= \frac{(2 \text{ V} - 6 \text{ V})(4 \Omega) + (2 \text{ V})(-j 1 \Omega)}{(+j 2 \Omega)(4 \Omega) + (+j 2 \Omega)(-j 2 \Omega) + (4 \Omega)(-j 2 \Omega)} \\ &= \frac{-16 - j 2}{j 8 - j^2 2 - j 4} = \frac{-16 - j 2}{2 + j 4} = \frac{16.12 \text{ A } \angle -172.87^\circ}{4.47 \angle 63.43^\circ} \\ &= 3.61 \text{ A } \angle -236.30^\circ \quad \text{or} \quad 3.61 \text{ A } \angle 123.70^\circ \end{aligned}$$

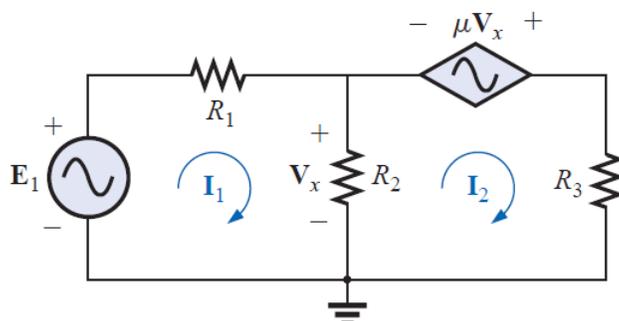EXAMPLE: Write the mesh currents for the network having a dependent voltage source.




Solutions:


$$\begin{aligned} E_1 - I_1 R_1 - R_2(I_1 - I_2) &= 0 \\ R_2(I_2 - I_1) + \mu V_x - I_2 R_3 &= 0 \end{aligned} \quad V_x = (I_1 - I_2)R_2$$

$$\begin{aligned} E_1 - I_1 R_1 - R_2(I_1 - I_2) &= 0 \\ R_2(I_2 - I_1) + \mu R_2(I_1 - I_2) - I_2 R_3 &= 0 \end{aligned}$$

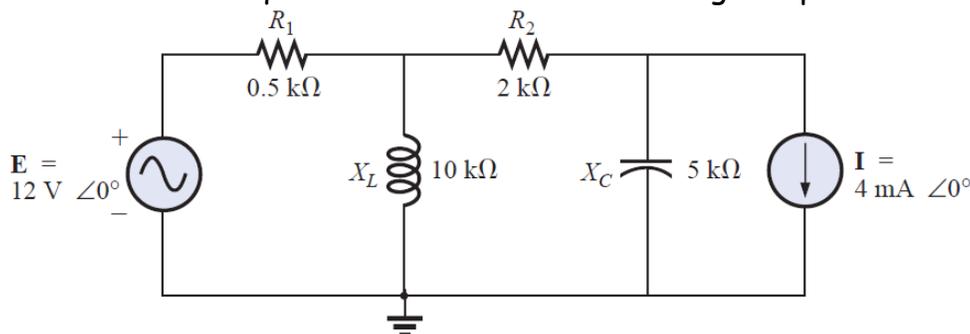EXAMPLE: Write the nodal equations for the network having a dependent current source.




Solutions:

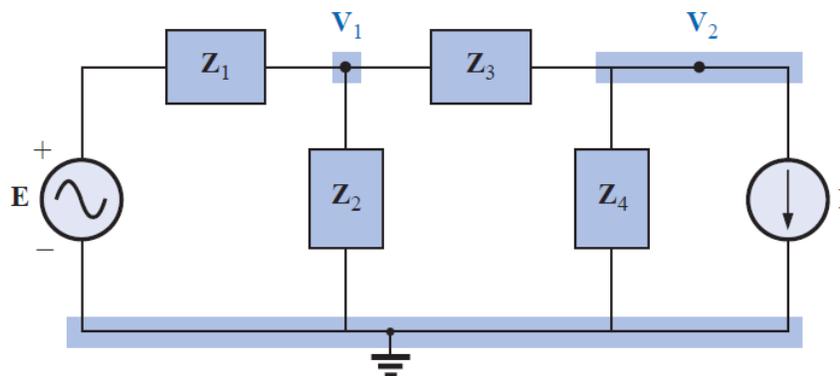


$$V_1 \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right] - V_2 \left[\frac{1}{Z_3} \right] = \frac{E_1}{Z_1}$$

$$V_2 \left[\frac{1}{Z_3} + \frac{1}{Z_4} \right] - V_1 \left[\frac{1}{Z_3} \right] = -I$$

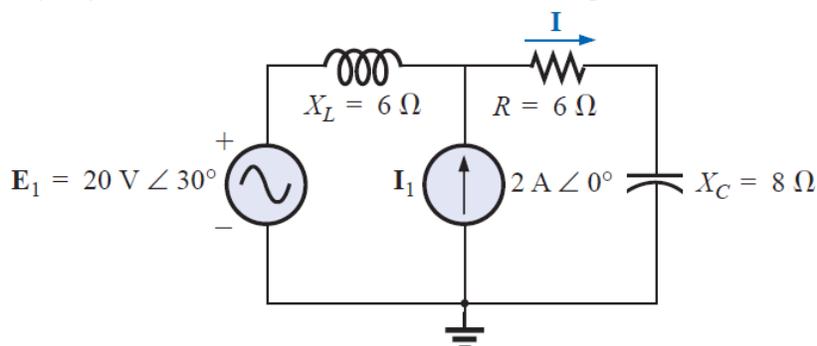
EXAMPLE: Using superposition, find the current I through the $6\text{-}\Omega$ resistor.



Solutions:

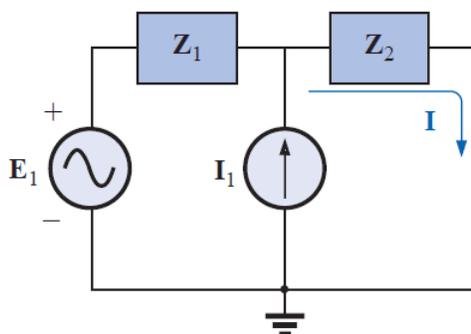

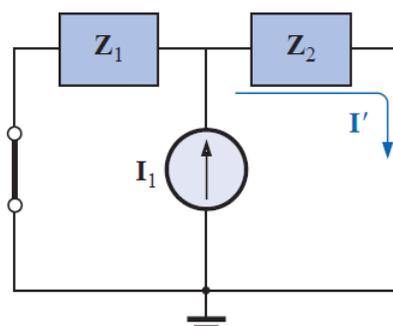
$$Z_1 = j 6 \Omega \quad Z_2 = 6 - j 8 \Omega$$



$$I' = \frac{Z_1 I_1}{Z_1 + Z_2} = \frac{(j 6 \Omega)(2 A)}{j 6 \Omega + 6 \Omega - j 8 \Omega} = \frac{j 12 A}{6 - j 2}$$

$$= \frac{12 A \angle 90^\circ}{6.32 \angle -18.43^\circ}$$


$$I' = 1.9 A \angle 108.43^\circ$$

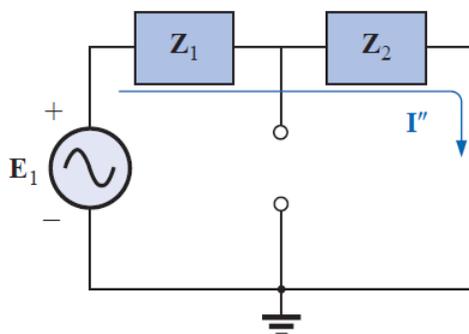


$$\begin{aligned} I'' &= \frac{E_1}{Z_T} = \frac{E_1}{Z_1 + Z_2} = \frac{20 \text{ V } \angle 30^\circ}{6.32 \Omega \angle -18.43^\circ} \\ &= 3.16 \text{ A } \angle 48.43^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I} &= \mathbf{I}' + \mathbf{I}'' \\ &= 1.9 \text{ A } \angle 108.43^\circ + 3.16 \text{ A } \angle 48.43^\circ \\ &= (-0.60 \text{ A} + j 1.80 \text{ A}) + (2.10 \text{ A} + j 2.36 \text{ A}) \\ &= 1.50 \text{ A} + j 4.16 \text{ A} \\ \mathbf{I} &= 4.42 \text{ A } \angle 70.2^\circ \end{aligned}$$

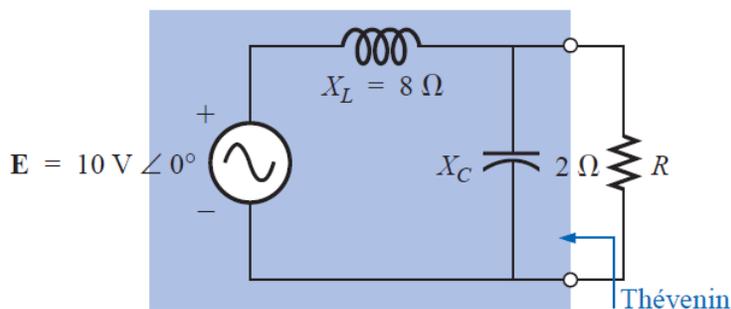
EXAMPLE: Find the Thévenin equivalent circuit for the network external to resistor R .




Solutions:

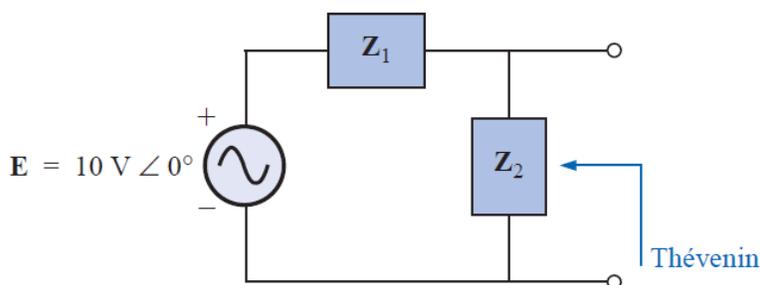

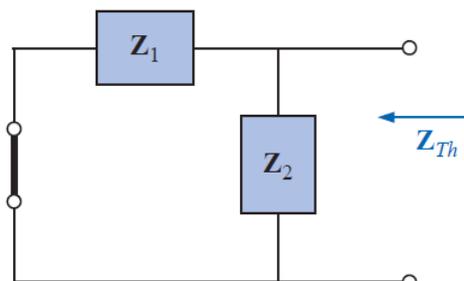
$$\mathbf{Z}_1 = jX_L = j8\ \Omega \quad \mathbf{Z}_2 = -jX_C = -j2\ \Omega$$



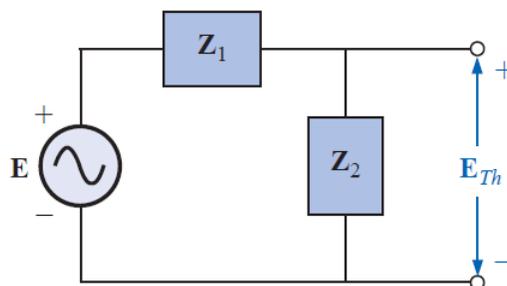
$$\begin{aligned} \mathbf{Z}_{Th} &= \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(j8\ \Omega)(-j2\ \Omega)}{j8\ \Omega - j2\ \Omega} = \frac{-j^2 16\ \Omega}{j6} = \frac{16\ \Omega}{6 \angle 90^\circ} \\ &= 2.67\ \Omega \angle -90^\circ \end{aligned}$$



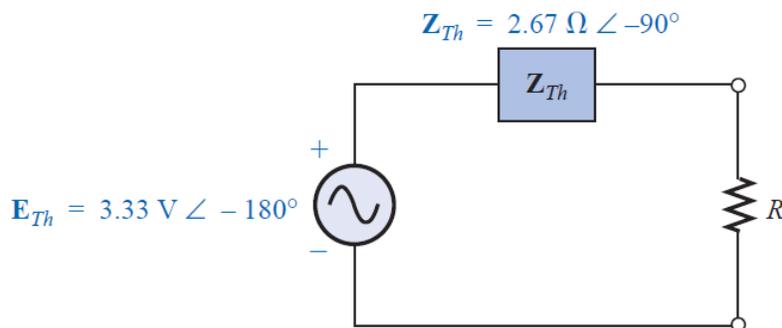
$$\begin{aligned} \mathbf{E}_{Th} &= \frac{\mathbf{Z}_2 \mathbf{E}}{\mathbf{Z}_1 + \mathbf{Z}_2} \quad (\text{voltage divider rule}) \\ &= \frac{(-j2\ \Omega)(10\ \text{V})}{j8\ \Omega - j2\ \Omega} = \frac{-j20\ \text{V}}{j6} = 3.33\ \text{V} \angle -180^\circ \end{aligned}$$




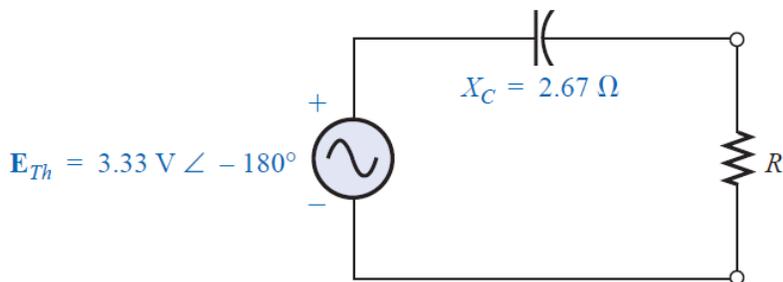

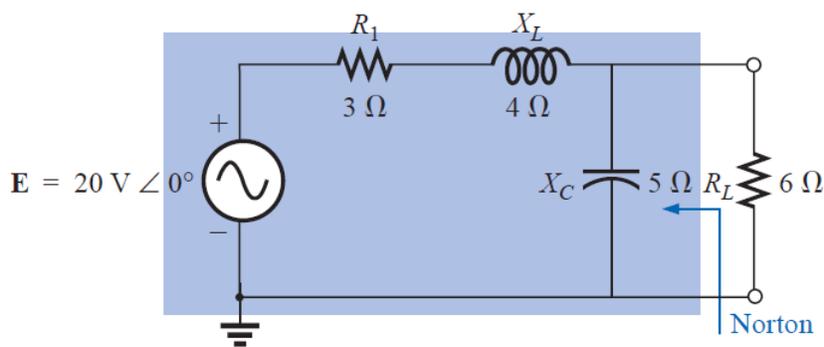EXAMPLE: Determine the Norton equivalent circuit for the network external to the 6-Ω resistor.




Solutions:

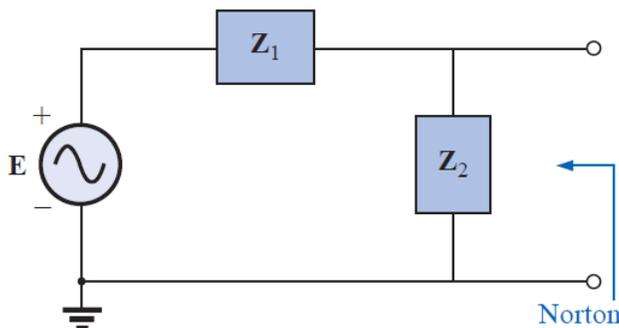


$$Z_1 = R_1 + j X_L = 3 \Omega + j 4 \Omega = 5 \Omega \angle 53.13^\circ$$


$$Z_2 = -j X_C = -j 5 \Omega$$

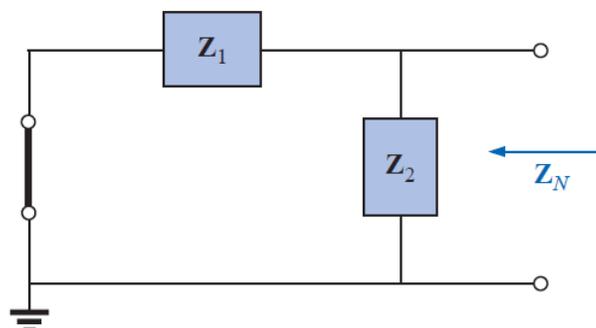

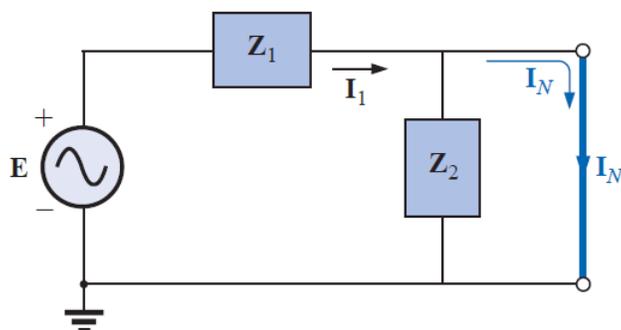
$$\begin{aligned} Z_N &= \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(5 \Omega \angle 53.13^\circ)(5 \Omega \angle -90^\circ)}{3 \Omega + j4 \Omega - j5 \Omega} = \frac{25 \Omega \angle -36.87^\circ}{3 - j1} \\ &= \frac{25 \Omega \angle -36.87^\circ}{3.16 \angle -18.43^\circ} = 7.91 \Omega \angle -18.44^\circ = 7.50 \Omega - j2.50 \Omega \end{aligned}$$


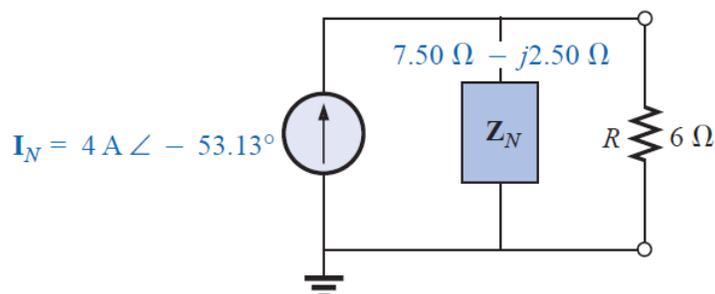
$$I_N = I_1 = \frac{E}{Z_1} = \frac{20 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 4 \text{ A} \angle -53.13^\circ$$




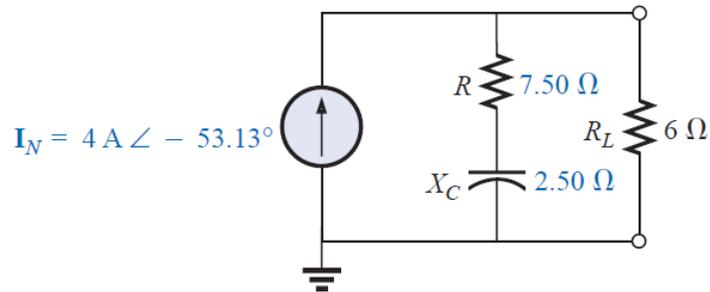

Power (ac)

AVERAGE POWER AND POWER FACTOR

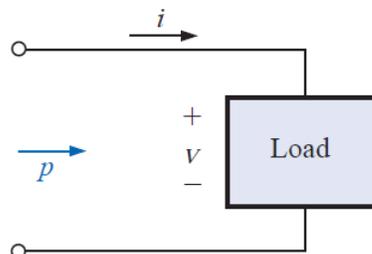The average power, or **real power** as it is sometimes called, is the power delivered to and dissipated by the load. It corresponds to the power calculations performed for dc networks.



$$p = vi$$



Since v and i are sinusoidal quantities, let us establish a general case where:

$$v = V_m \sin(\omega t + \theta)$$

$$i = I_m \sin \omega t$$

* The angle (θ) is the phase angle between v and i .

Substituting the above equations for v and i into the power equation will result in

$$p = V_m I_m \sin \omega t \sin(\omega t + \theta)$$

If we now apply a number of trigonometric identities, the following form for the power equation will result:

$$p = VI \cos \theta (1 - \cos 2\omega t) + VI \sin \theta (\sin 2\omega t)$$

* where V and I are the **rms** values.

$$V = \frac{V_m}{\sqrt{2}} \quad \text{and} \quad I = \frac{I_m}{\sqrt{2}}$$

So that the power is

$$p = \underbrace{VI \cos \theta}_{\text{Average}} - \underbrace{VI \cos \theta}_{\text{Peak}} \underbrace{\cos 2\omega t}_{2x} + \underbrace{VI \sin \theta}_{\text{Peak}} \underbrace{\sin 2\omega t}_{2x}$$

The average power equal

$$P = VI \cos \theta$$

* The magnitude of average power delivered is independent of whether v leads i or i leads v .

- for resistor $\theta = 0$ then $P = VI \cos 0 = VI$
- for Inductor v leads i by 90° , then $P = VI \cos 90 = 0$
- for Capacitor i leads v by 90° , then $P = VI \cos 90 = 0$

Power factor

The power factor is the factor that has significant control over the delivered power level.

$$\text{Power factor} = F_p = \cos \theta$$

- Capacitive networks have **leading** power factors,
- Inductive networks have **lagging** power factors.

APPARENT POWER

It is a power rating of significant usefulness in the description and analysis of sinusoidal ac networks and in the maximum rating of a number of electrical components and systems.

$$S = VI \quad (\text{volt-amperes, VA})$$



$$S = I^2 Z \quad (\text{VA})$$

$$S = \frac{V^2}{Z} \quad (\text{VA})$$


Therefore

$$P = S \cos \theta \quad (\text{W})$$

$$F_p = \cos \theta = \frac{P}{S}$$

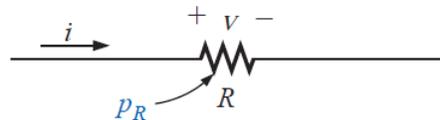1) RESISTIVE CIRCUIT

For a purely resistive circuit, v and i are in phase, and $\theta = 0^\circ$,



$$\begin{aligned} p_R &= VI \cos(0^\circ)(1 - \cos 2\omega t) + VI \sin(0^\circ) \sin 2\omega t \\ &= VI(1 - \cos 2\omega t) + 0 \end{aligned}$$


$$p_R = VI - VI \cos 2\omega t$$

The average (real) power is

$$P = VI = \frac{V_m I_m}{2} = I^2 R = \frac{V^2}{R} \quad (\text{watts, W})$$

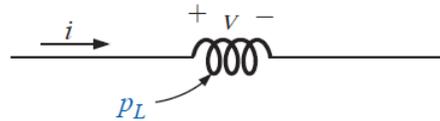2) INDUCTIVE CIRCUIT

For a purely inductive circuit, v leads i by 90° , $\theta = 90^\circ$.



$$p_L = VI \cos(90^\circ)(1 - \cos 2\omega t) + VI \sin(90^\circ)(\sin 2\omega t)$$

$$= 0 + VI \sin 2\omega t$$

$$p_L = VI \sin 2\omega t$$

The reactive power is


$$Q = VI \sin \theta \quad (\text{volt-ampere reactive, VAR})$$

$$Q_L = I^2 X_L \quad (\text{VAR})$$

$$Q_L = \frac{V^2}{X_L} \quad (\text{VAR})$$

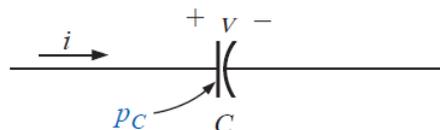3) CAPACITIVE CIRCUIT

For a purely capacitive circuit, i leads v by 90° , $\theta = -90^\circ$.



$$p_C = VI \cos(-90^\circ)(1 - \cos 2\omega t) + VI \sin(-90^\circ)(\sin 2\omega t)$$

$$= 0 - VI \sin 2\omega t$$

$$p_C = -VI \sin 2\omega t$$

The reactive power is


$$Q = VI \sin \theta \quad (\text{volt-ampere reactive, VAR})$$

$$Q_C = I^2 X_C$$

$$Q_C = \frac{V^2}{X_C}$$


THE POWER TRIANGLE

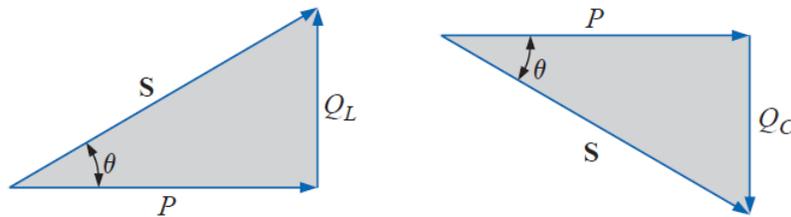The three quantities **average power (P)**, **apparent power (S)**, and **reactive power (Q)** can be related in the vector domain by



$$S = P + jQ$$
$$Q = Q_L - Q_C$$

$$S^2 = P^2 + Q^2$$

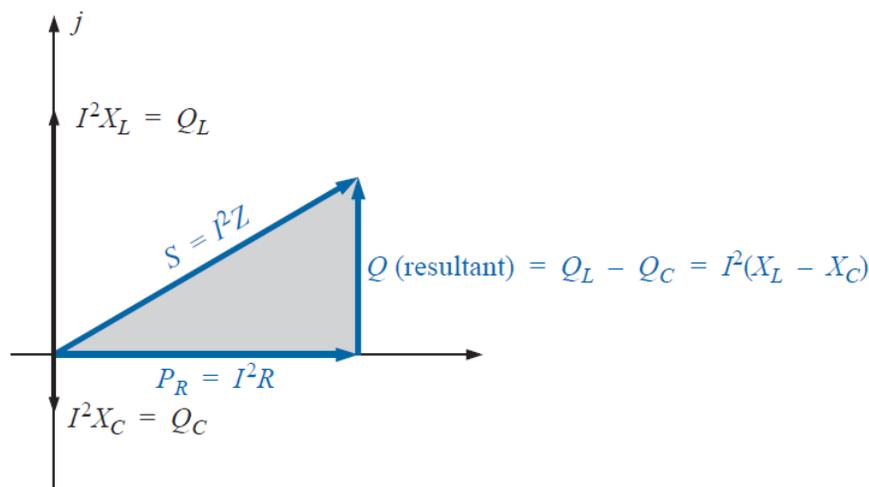


$$S = \sqrt{P^2 + Q^2}$$

$$F_p = \cos \theta = \frac{P}{S}$$

1. Find the real power and reactive power for each branch of the circuit.
2. The total real power of the system (P_T) is then the sum of the average power delivered to each branch.
3. The total reactive power (Q_T) is the difference between the reactive power of the inductive loads and that of the capacitive loads.
4. The total apparent power is $S_T = \sqrt{P_T + Q_T}$.
5. The total power factor is P_T / S_T .

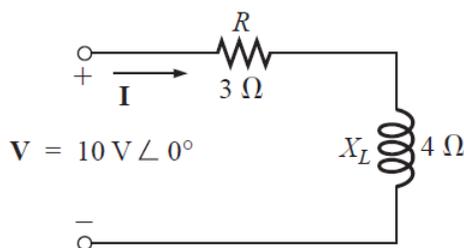EXAMPLE: Find the total number of watts, volt-amperes reactive, and volt-amperes for the network.



Solutions:

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_T} = \frac{10 \text{ V} \angle 0^\circ}{3 \Omega + j4 \Omega} = \frac{10 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 2 \text{ A} \angle -53.13^\circ$$


$$P = I^2 R = (2 \text{ A})^2 (3 \Omega) = 12 \text{ W}$$

$$Q_L = I^2 X_L = (2 \text{ A})^2 (4 \Omega) = 16 \text{ VAR (L)}$$


$$\mathbf{S} = P + j Q_L = 12 \text{ W} + j 16 \text{ VAR (L)} = 20 \text{ VA} \angle 53.13^\circ$$

Or
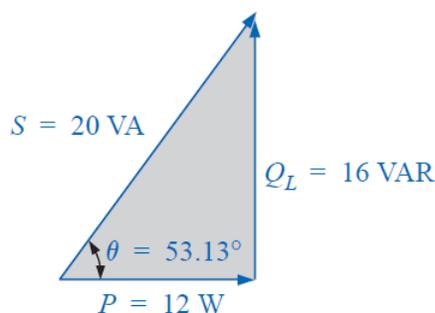
$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = (10 \text{ V} \angle 0^\circ)(2 \text{ A} \angle +53.13^\circ) = 20 \text{ VA} \angle 53.13^\circ$$



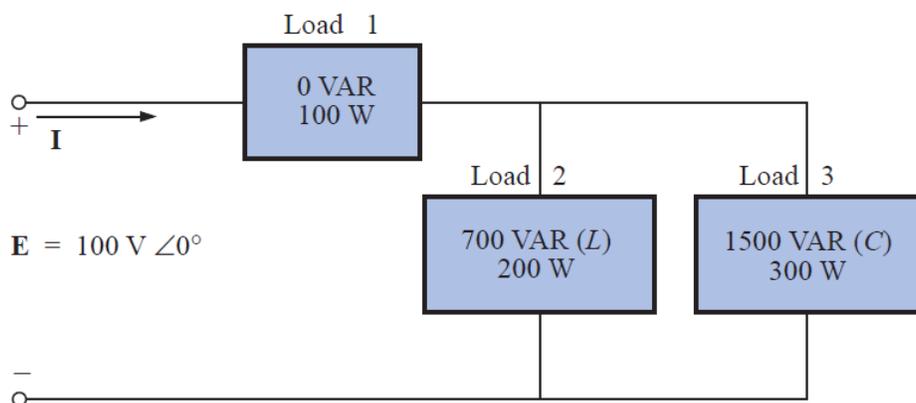EXAMPLE: Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor F_p of the network. Draw the power triangle and find the current in phasor form.




Solutions:

Load	W	VAR	VA
1	100	0	100
2	200	700 (L)	$\sqrt{(200)^2 + (700)^2} = 728.0$
3	300	1500 (C)	$\sqrt{(300)^2 + (1500)^2} = 1529.71$
	$P_T = 600$ Total power dissipated	$Q_T = 800 (C)$ Resultant reactive power of network	$S_T = \sqrt{(600)^2 + (800)^2} = 1000$ (Note that $S_T \neq$ sum of each branch: $1000 \neq 100 + 728 + 1529.71$)

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{1000 \text{ VA}} = 0.6 \text{ leading (C)}$$


$$I = 1000 \text{ VA} / 100 \text{ V} = 10 \text{ A}$$
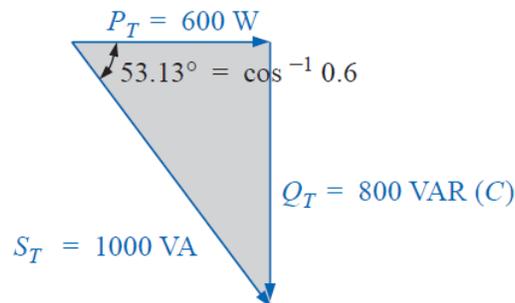
$$\mathbf{I} = 10 \text{ A} \angle +53.13^\circ$$



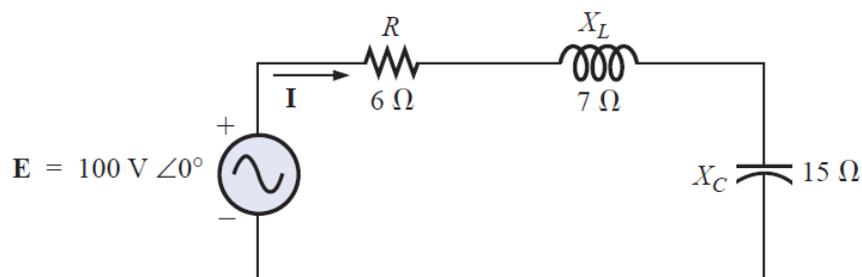EXAMPLE:

- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor F_p for the network.
- Sketch the power triangle.



Solutions:

a)

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \text{ V } \angle 0^\circ}{6 \Omega + j7 \Omega - j15 \Omega} = \frac{100 \text{ V } \angle 0^\circ}{10 \Omega \angle -53.13^\circ}$$

$$= 10 \text{ A } \angle 53.13^\circ$$

$$\mathbf{V}_R = (10 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) = 60 \text{ V } \angle 53.13^\circ$$

$$\mathbf{V}_L = (10 \text{ A } \angle 53.13^\circ)(7 \Omega \angle 90^\circ) = 70 \text{ V } \angle 143.13^\circ$$

$$\mathbf{V}_C = (10 \text{ A } \angle 53.13^\circ)(15 \Omega \angle -90^\circ) = 150 \text{ V } \angle -36.87^\circ$$

$$P_T = EI \cos \theta = (100 \text{ V})(10 \text{ A}) \cos 53.13^\circ = \mathbf{600 \text{ W}}$$

$$= I^2 R = (10 \text{ A})^2 (6 \Omega) = \mathbf{600 \text{ W}}$$

$$= \frac{V_R^2}{R} = \frac{(60 \text{ V})^2}{6} = \mathbf{600 \text{ W}}$$

$$S_T = EI = (100 \text{ V})(10 \text{ A}) = \mathbf{1000 \text{ VA}}$$

$$= I^2 Z_T = (10 \text{ A})^2 (10 \Omega) = \mathbf{1000 \text{ VA}}$$

$$= \frac{E^2}{Z_T} = \frac{(100 \text{ V})^2}{10 \Omega} = \mathbf{1000 \text{ VA}}$$

$$Q_T = EI \sin \theta = (100 \text{ V})(10 \text{ A}) \sin 53.13^\circ = \mathbf{800 \text{ VAR}}$$

$$= Q_C - Q_L$$


$$= I^2 (X_C - X_L) = (10 \text{ A})^2 (15 \Omega - 7 \Omega) = \mathbf{800 \text{ VAR}}$$

$$Q_T = \frac{V_C^2}{X_C} - \frac{V_L^2}{X_L} = \frac{(150 \text{ V})^2}{15 \Omega} - \frac{(70 \text{ V})^2}{7 \Omega}$$

$$= 1500 \text{ VAR} - 700 \text{ VAR} = \mathbf{800 \text{ VAR}}$$

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{1000 \text{ VA}} = \mathbf{0.6 \text{ leading (C)}}$$

b)

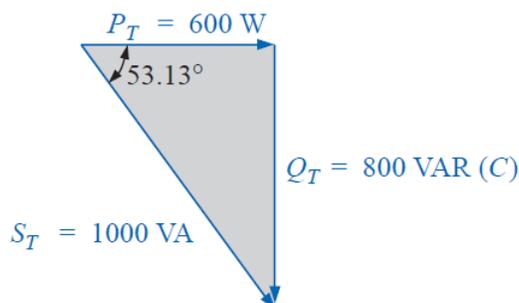

EXAMPLE: An electrical device is rated 5 kVA, 100 V at a 0.6 power-factor lag. What is the impedance of the device in rectangular coordinates?

Solutions:

$$S = EI = 5000 \text{ VA}$$


$$I = \frac{5000 \text{ VA}}{100 \text{ V}} = 50 \text{ A}$$

$$\theta = \cos^{-1} 0.6 = 53.13^\circ$$

for $\mathbf{E} = 100 \text{ V} \angle 0^\circ$,


$$\mathbf{I} = 50 \text{ A} \angle -53.13^\circ$$
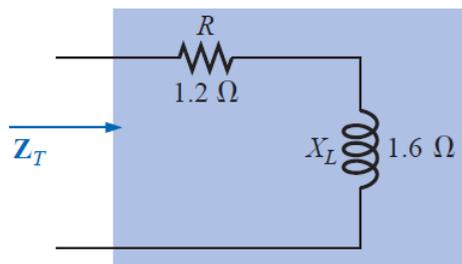
$$\mathbf{Z}_T = \frac{\mathbf{E}}{\mathbf{I}} = \frac{100 \text{ V} \angle 0^\circ}{50 \text{ A} \angle -53.13^\circ} = 2 \Omega \angle 53.13^\circ = 1.2 \Omega + j 1.6 \Omega$$



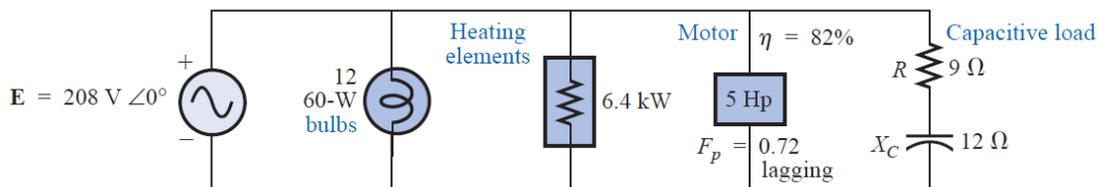EXAMPLE: For the system

- Find the average power, apparent power, reactive power, and F_p for each branch.
- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor of the system. Sketch the power triangle.
- Find the source current I .



Solutions:

a)

Bulbs:

Total dissipation of applied power

$$P_1 = 12(60 \text{ W}) = \mathbf{720 \text{ W}}$$

$$Q_1 = \mathbf{0 \text{ VAR}}$$

$$S_1 = P_1 = \mathbf{720 \text{ VA}}$$

$$F_{p1} = \mathbf{1}$$

Heating elements:

Total dissipation of applied power

$$P_2 = \mathbf{6.4 \text{ kW}}$$

$$Q_2 = \mathbf{0 \text{ VAR}}$$

$$S_2 = P_2 = \mathbf{6.4 \text{ kVA}}$$

$$F_{p2} = \mathbf{1}$$

Motor:

$$\eta = \frac{P_o}{P_i} \rightarrow P_i = \frac{P_o}{\eta} = \frac{5(746 \text{ W})}{0.82} = \mathbf{4548.78 \text{ W}} = P_3$$

$$F_p = \mathbf{0.72 \text{ lagging}}$$

$$P_3 = S_3 \cos \theta \rightarrow S_3 = \frac{P_3}{\cos \theta} = \frac{4548.78 \text{ W}}{0.72} = \mathbf{6317.75 \text{ VA}}$$

Also, $\theta = \cos^{-1} 0.72 = 43.95^\circ$, so that

$$\begin{aligned} Q_3 &= S_3 \sin \theta = (6317.75 \text{ VA})(\sin 43.95^\circ) \\ &= (6317.75 \text{ VA})(0.694) = \mathbf{4384.71 \text{ VAR (L)}} \end{aligned}$$

Capacitive load:

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}} = \frac{208 \text{ V} \angle 0^\circ}{9 \Omega - j 12 \Omega} = \frac{208 \text{ V} \angle 0^\circ}{15 \Omega \angle -53.13^\circ} = 13.87 \text{ A} \angle 53.13^\circ$$

$$P_4 = I^2 R = (13.87 \text{ A})^2 \cdot 9 \Omega = \mathbf{1731.39 \text{ W}}$$

$$Q_4 = I^2 X_C = (13.87 \text{ A})^2 \cdot 12 \Omega = \mathbf{2308.52 \text{ VAR (C)}}$$

$$S_4 = \sqrt{P_4^2 + Q_4^2} = \sqrt{(1731.39 \text{ W})^2 + (2308.52 \text{ VAR})^2} \\ = \mathbf{2885.65 \text{ VA}}$$

$$F_p = \frac{P_4}{S_4} = \frac{1731.39 \text{ W}}{2885.65 \text{ VA}} = \mathbf{0.6 \text{ leading}}$$

b)


$$P_T = P_1 + P_2 + P_3 + P_4 \\ = 720 \text{ W} + 6400 \text{ W} + 4548.78 \text{ W} + 1731.39 \text{ W} \\ = \mathbf{13,400.17 \text{ W}}$$

$$Q_T = \pm Q_1 \pm Q_2 \pm Q_3 \pm Q_4 \\ = 0 + 0 + 4384.71 \text{ VAR (L)} - 2308.52 \text{ VAR (C)} \\ = \mathbf{2076.19 \text{ VAR (L)}}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{(13,400.17 \text{ W})^2 + (2076.19 \text{ VAR})^2} \\ = 13,560.06 \text{ VA}$$

$$F_p = \frac{P_T}{S_T} = \frac{13.4 \text{ kW}}{13,560.06 \text{ VA}} = \mathbf{0.988 \text{ lagging}}$$
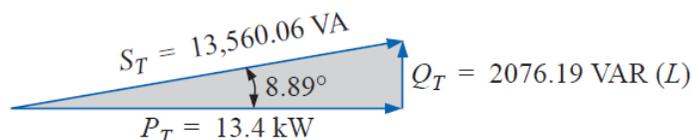
$$\theta = \cos^{-1} 0.988 = 8.89^\circ$$



c)


$$S_T = EI \rightarrow I = \frac{S_T}{E} = \frac{13,559.89 \text{ VA}}{208 \text{ V}} = 65.19 \text{ A}$$

Lagging power factor: \mathbf{E} leads \mathbf{I} by 8.89° , and


$$\mathbf{I} = 65.19 \text{ A} \angle -8.89^\circ$$

Resonance

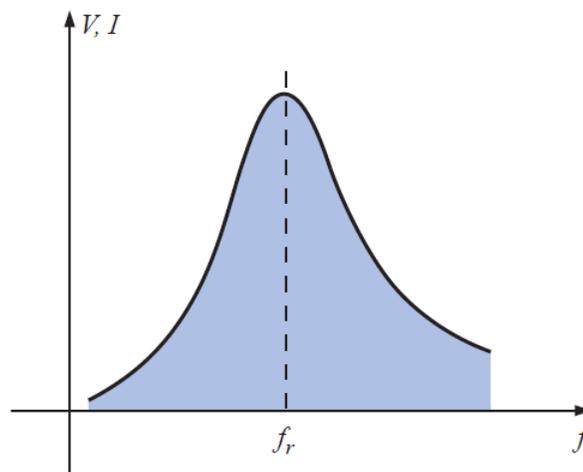The resonant circuit is a combination of R, L, and C elements having a frequency response characteristic similar to the one appearing in Figure below. Note in the figure that the response is a maximum for the frequency f_r , decreasing to the right and left of this frequency.



1-SERIES RESONANT CIRCUIT

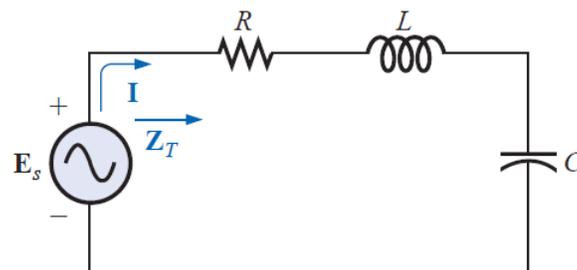

$$Z_T = R + jX_L - jX_C = R + j(X_L - X_C)$$

$$X_L = X_C$$

$$Z_{T_s} = R$$



$$\omega L = \frac{1}{\omega C} \quad \text{and} \quad \omega^2 = \frac{1}{LC}$$

$$\omega_s = \frac{1}{\sqrt{LC}}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

f = hertz (Hz)
 L = henries (H)
 C = farads (F)

$$V_{L_s} = V_{C_s}$$

$$F_p = \cos \theta = \frac{P}{S}$$

$$F_{p_s} = 1$$

THE QUALITY FACTOR (Q)

The quality factor Q of a series resonant circuit is defined as the ratio of the reactive power of either the inductor or the capacitor to the average power of the resistor at resonance; that is,

$$Q_s = \frac{\text{reactive power}}{\text{average power}}$$

$$Q_s = \frac{I^2 X_L}{I^2 R}$$

$$Q_s = \frac{X_L}{R} = \frac{\omega_s L}{R}$$

$$Q_s = \frac{\omega_s L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi}{R} \left(\frac{1}{2\pi\sqrt{LC}} \right) L$$

$$= \frac{L}{R} \left(\frac{1}{\sqrt{LC}} \right) = \left(\frac{\sqrt{L}}{\sqrt{L}} \right) \frac{L}{R\sqrt{LC}}$$


$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$V_{L_s} = Q_s E$$

$$V_{C_s} = Q_s E$$

SELECTIVITY

There is a definite range of frequencies at which the current is near its maximum value and the impedance is at a minimum. Those frequencies corresponding to 0.707 of the maximum current are called the **band frequencies**, **cutoff frequencies**, or **half-power frequencies**. They are indicated by f_1 and f_2 in Figure below. The range of frequencies between the two is referred to as the bandwidth (abbreviated BW) of the resonant circuit.

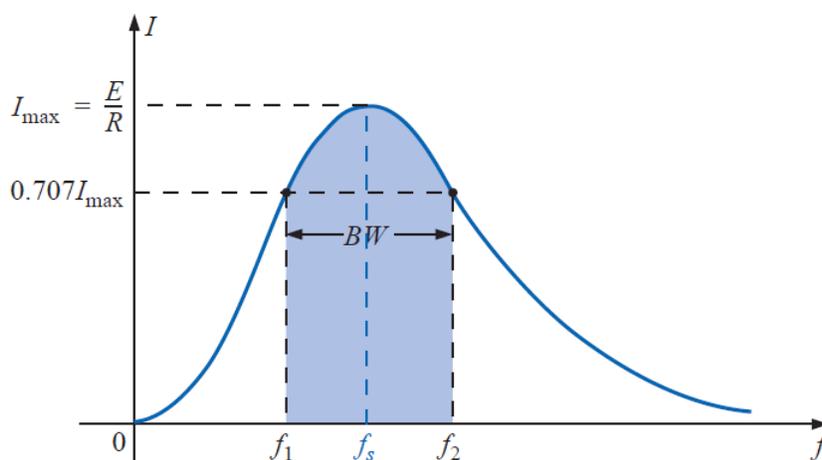


$$P_{\text{HPF}} = \frac{1}{2} P_{\text{max}}$$

$$BW = f_2 - f_1 = \frac{R}{2\pi L}$$

$$BW = \frac{f_s}{Q_s}$$

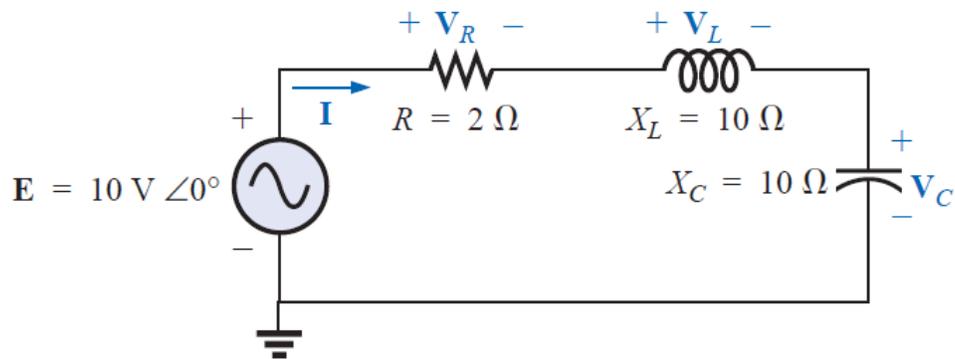EXAMPLE:

- For the series resonant circuit, find I , V_R , V_L , and V_C at resonance.
- What is the Q_s of the circuit?
- If the resonant frequency is 5000 Hz, find the bandwidth.
- What is the power dissipated in the circuit at the half-power frequencies?



Solutions:

a. $Z_{T_s} = R = 2 \Omega$

$$I = \frac{E}{Z_{T_s}} = \frac{10 \text{ V } \angle 0^\circ}{2 \Omega \angle 0^\circ} = 5 \text{ A } \angle 0^\circ$$

$$V_R = E = 10 \text{ V } \angle 0^\circ$$

$$V_L = (I \angle 0^\circ)(X_L \angle 90^\circ) = (5 \text{ A } \angle 0^\circ)(10 \Omega \angle 90^\circ) = 50 \text{ V } \angle 90^\circ$$

$$V_C = (I \angle 0^\circ)(X_C \angle -90^\circ) = (5 \text{ A } \angle 0^\circ)(10 \Omega \angle -90^\circ) = 50 \text{ V } \angle -90^\circ$$

b. $Q_s = \frac{X_L}{R} = \frac{10 \Omega}{2 \Omega} = 5$

c. $BW = f_2 - f_1 = \frac{f_s}{Q_s} = \frac{5000 \text{ Hz}}{5} = 1000 \text{ Hz}$

d. $P_{\text{HPF}} = \frac{1}{2}P_{\text{max}} = \frac{1}{2}I_{\text{max}}^2R = \left(\frac{1}{2}\right)(5 \text{ A})^2(2 \Omega) = 25 \text{ W}$

EXAMPLE: The bandwidth of a series resonant circuit is 400 Hz.

- If the resonant frequency is 4000 Hz, what is the value of Q_s ?
- If $R = 10 \Omega$, what is the value of X_L at resonance?
- Find the inductance L and capacitance C of the circuit.

Solutions:

a. $BW = \frac{f_s}{Q_s}$ or $Q_s = \frac{f_s}{BW} = \frac{4000 \text{ Hz}}{400 \text{ Hz}} = 10$

b. $Q_s = \frac{X_L}{R}$ or $X_L = Q_s R = (10)(10 \Omega) = 100 \Omega$

c. $X_L = 2\pi f_s L$ or $L = \frac{X_L}{2\pi f_s} = \frac{100 \Omega}{2\pi(4000 \text{ Hz})} = 3.98 \text{ mH}$

$$X_C = \frac{1}{2\pi f_s C} \text{ or } C = \frac{1}{2\pi f_s X_C} = \frac{1}{2\pi(4000 \text{ Hz})(100 \Omega)}$$

$$= 0.398 \mu\text{F}$$

EXAMPLE: A series R - L - C circuit has a series resonant frequency of 12,000 Hz.

- If $R = 5 \Omega$, and if X_L at resonance is 300Ω , find the bandwidth.
- Find the cutoff frequencies.

Solutions:

$$a. Q_s = \frac{X_L}{R} = \frac{300 \Omega}{5 \Omega} = 60$$


$$BW = \frac{f_s}{Q_s} = \frac{12,000 \text{ Hz}}{60} = \mathbf{200 \text{ Hz}}$$

b. Since $Q_s \geq 10$, the bandwidth is bisected by f_s . Therefore,

$$f_2 = f_s + \frac{BW}{2} = 12,000 \text{ Hz} + 100 \text{ Hz} = \mathbf{12,100 \text{ Hz}}$$

$$\text{and } f_1 = 12,000 \text{ Hz} - 100 \text{ Hz} = \mathbf{11,900 \text{ Hz}}$$

2-PARALLEL RESONANT CIRCUIT

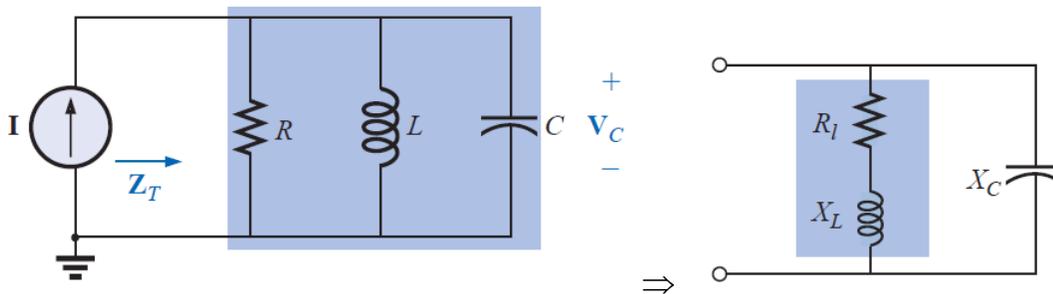

$$R_p = \frac{R_l^2 + X_L^2}{R_l}$$

$$X_{L_p} = \frac{R_l^2 + X_L^2}{X_L}$$

$$X_{L_p} = X_C$$

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_l^2 C}{L}}$$

$$f_p = f_s \sqrt{1 - \frac{R_l^2 C}{L}}$$


SELECTIVITY CURVE FOR PARALLEL RESONANT CIRCUITS

$$Q_p = \frac{X_L}{R_l} = Q_l$$

$$BW = f_2 - f_1 = \frac{f_r}{Q_p}$$

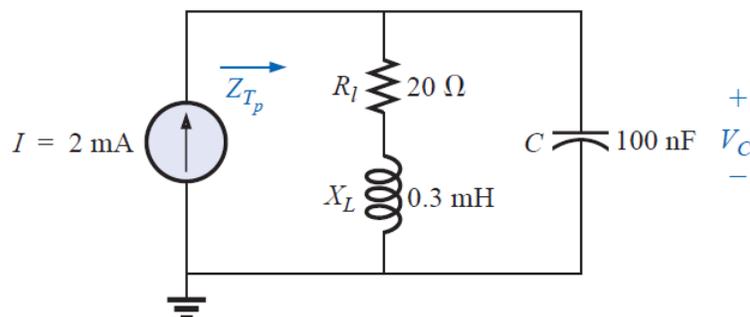EXAMPLE: For the parallel resonant circuit

- Determine f_s , and f_p , and compare their levels.
- Determine the quality factor Q_p .
- Calculate the bandwidth.



Solutions:

$$a. f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.3 \text{ mH})(100 \text{ nF})}} = 29.06 \text{ kHz}$$



$$f_p = f_s \sqrt{1 - \frac{R_l^2 C}{L}} = (29.06 \text{ kHz}) \sqrt{1 - \left[\frac{(20 \Omega)^2 (100 \text{ nF})}{0.3 \text{ mH}} \right]}$$
$$= \mathbf{27.06 \text{ kHz}}$$

b.

$$Q_p = \frac{R_s \parallel R_p}{X_{L_p}} = \frac{R_p}{X_{L_p}} = Q_l = \frac{X_L}{R_l}$$
$$= \frac{2\pi(27.06 \text{ kHz})(0.3 \text{ mH})}{20 \Omega} = \frac{51 \Omega}{20 \Omega} = \mathbf{2.55}$$

c.

$$BW = \frac{f_p}{Q_p} = \frac{27.06 \text{ kHz}}{2.55} = \mathbf{10.61 \text{ kHz}}$$