

هندسة تقنيات الاجهزة الطبية



كلية الرشيد الجامعة

## ELECTRONIC CIRCUITS AND DEVICES

### DIODE CHARACTERISTICS

(2)

مرحلة ثانية



م.م. دينا جمال

# Diode Switching Circuits

## Basic Concepts:

Diode switching circuits typically contain two or more diodes, each of which is connected to an independent voltage source. Understanding the operation of a diode switching circuit depends on determining which diodes, if any, are forward biased and which, if any, are reverse biased. The key to this determination is remembering that *a diode is forward biased only if its anode is positive with respect to its cathode* (see Fig. 2-1). One of the very important applications of diode switching circuits is logic gates.

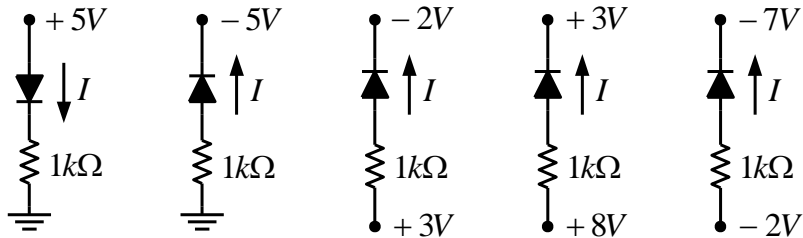



Fig. 2-1

## Logic Gates:

Diodes can be used to form logic gates, which perform some of the logic operations required in digital computers.
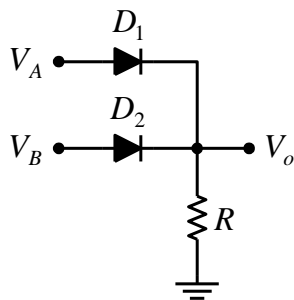
### ◀ OR Gate:

It has output when there is a signal in any input channels (see Fig. 2-2).




Input voltages		State of diodes		Output voltage
$V_A$	$V_B$	$D_1$	$D_2$	$V_o$
0	0	off	off	0
0	1	off	on	1
1	0	on	off	1
1	1	on	on	1

Fig. 2-2
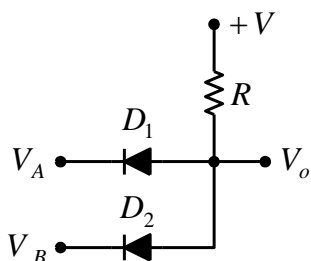
### ◀ AND Gate:

It has output only when all inputs are present (see Fig. 2-3).



Input voltages		State of diodes		Output voltage
$V_A$	$V_B$	$D_1$	$D_2$	$V_o$
0	0	on	on	0
0	1	on	off	0
1	0	off	on	0
1	1	off	off	1

Fig. 2-3

### Example 2-1:

Determine which diodes are forward biased and which are reverse biased in the circuits shown in Fig. 2-4. Assuming a 0.7-V drop across each forward-biased diode, determine the output voltage  $V_o$ .

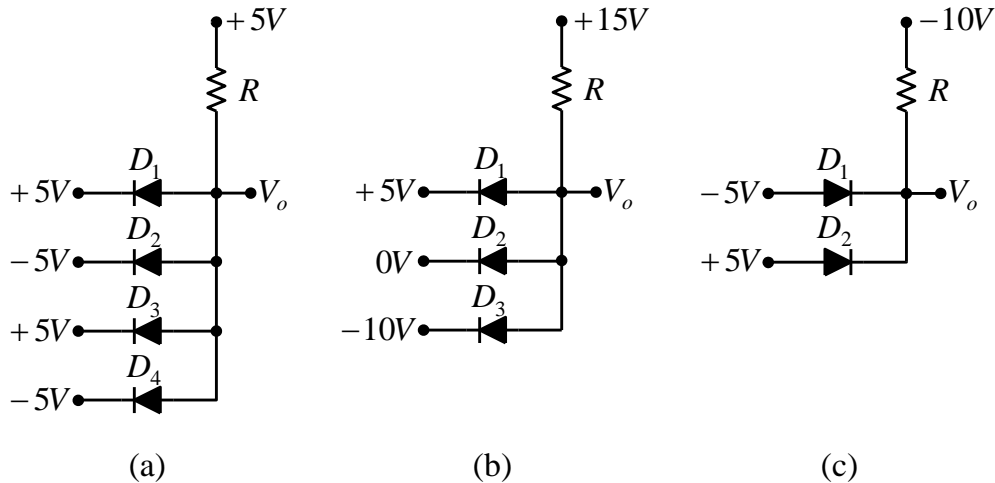


Fig. 2-4

#### Solution:

Applying a golden rule, a diode is forward biased when

$$\boxed{V^{Anode} - V^{Cathode} = V^{+ve} > V_T}, \text{ yields:}$$

In (a) the net forward-biasing voltage between supply and input for each diode is

$$\begin{aligned} D_1 \ \& \ D_3: & +5 - (+5) = 0V, \\ D_2 \ \& \ D_4: & +5 - (-5) = 10V. \end{aligned}$$

Therefore,  $D_2$  and  $D_4$  are forward biased and  $D_1$  and  $D_3$  are reverse biased.

$$V_o = -5 + 0.7 = -4.3V.$$

While in (b) the net forward-biasing voltage between supply and input for each diode is

$$\begin{aligned} D_1: & +15 - (+5) = +10V, \\ D_2: & +15 - 0 = +15V, \\ D_3: & +15 - (-10) = +25V. \end{aligned}$$

Therefore,  $D_3$  is forward biased and  $D_1$  and  $D_2$  are reverse biased.

$$V_o = -10 + 0.7 = -9.3V.$$

Finally, in (c) the net forward-biasing voltage between supply and input for each diode is

$$\begin{aligned} D_1: & -5 - (-10) = +5V, \\ D_2: & +5 - (-10) = +15V. \end{aligned}$$

Therefore,  $D_2$  is forward biased and  $D_1$  is reverse biased.

$$V_o = +5 - 0.7 = +4.3V.$$

**Exercise:**

Determine  $V_o$  and  $I$  for each circuit in Fig. 2-5. Assume that each of the diodes in these circuits has a forward voltage drop of  $0.7\text{ V}$ .

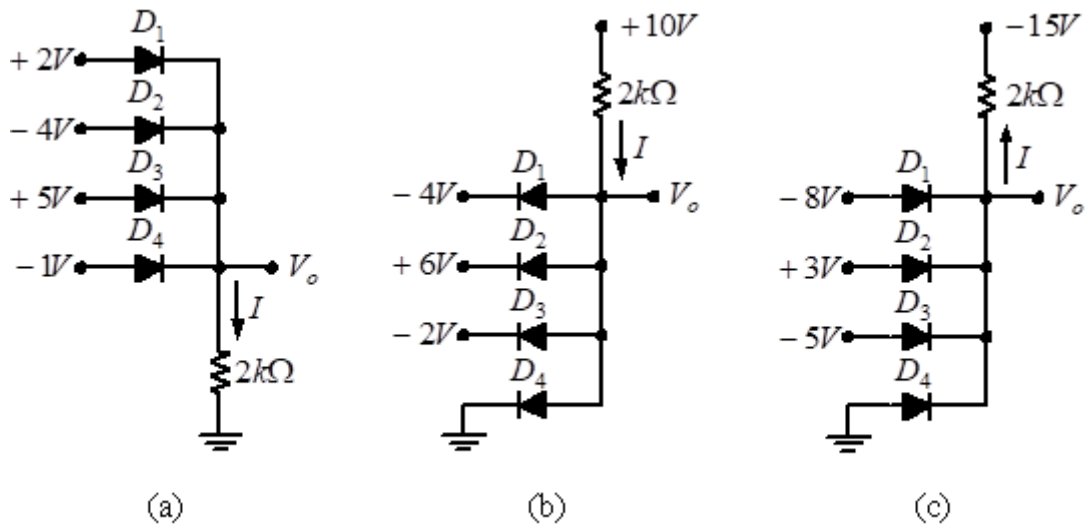


Fig. 2-5